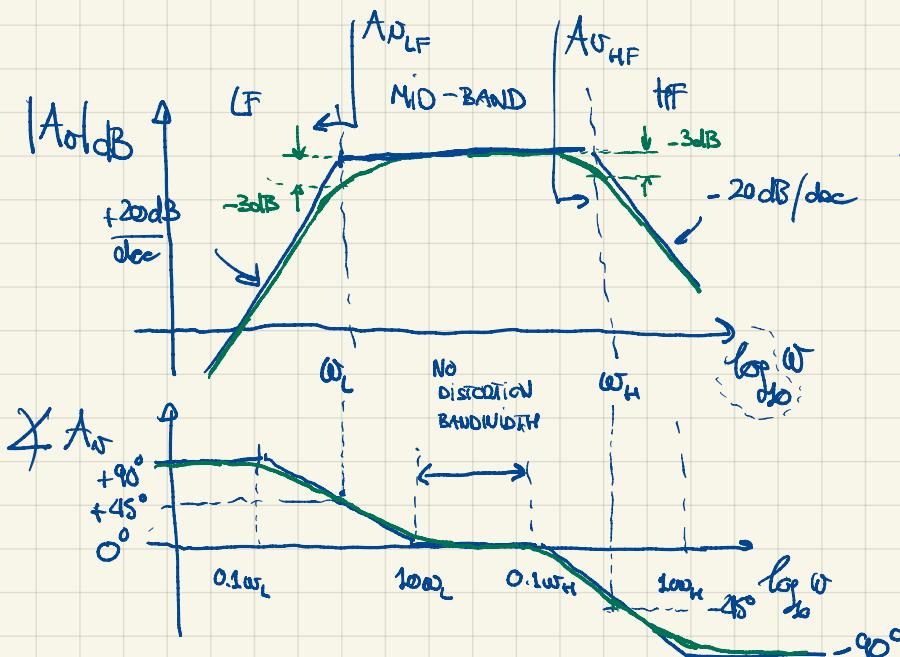


SEPTEMBER 30<sup>th</sup>, 2022

## LESSON #1

- COURSE ORGANIZATION
- QUESTION TIME → EVERY 2 MONDAYS AT 9:30 ON ZOOM

### FREQUENCY RESPONSE RECAP



$$20 \log_{10} |A(\omega)|$$

$$BW \approx \omega_H - \omega_L \approx \omega_H$$

### MINIMUM COMPLEXITY TRANSFER FUNCTION

$$A_N(s) = A_{N_{MB}} \cdot \frac{s\zeta_L}{(1+s\zeta_L)(1+s\zeta_H)} = \underbrace{A_{N_{MB}} \cdot \frac{s\zeta_L}{1+s\zeta_L}}_{A_{VLF}(s)} \cdot \underbrace{\frac{1}{1+s\zeta_H}}_{A_{VHF}(s)}$$

$$\zeta_L = \frac{1}{\omega_L} \quad \zeta_H = \frac{1}{\omega_H}$$

### LOW FREQUENCY RESPONSE


$$A_{VLF}(s) = A_{N_{MB}} \cdot \frac{s\zeta_L}{1+s\zeta_L}$$

### STEP RESPONSE ANALYSIS

$$\theta(s) = \mathcal{L}[v_i(t)] = \frac{V_i}{s}$$

$$V_o(s) = \theta(s) \cdot A_{VLF}(s) = A_{N_{MB}} \cdot \frac{\zeta_L}{1+s\zeta_L} \cdot V_i$$
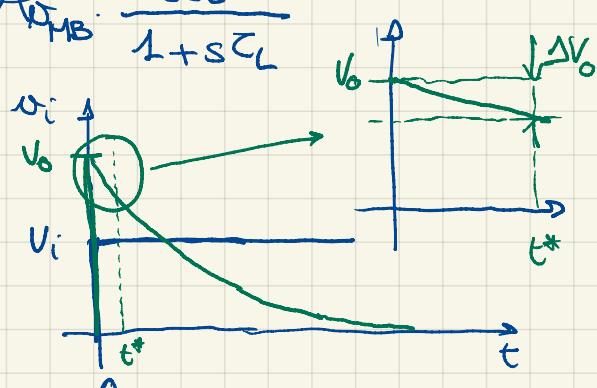
$$\mathcal{L}^{-1}[V_o(s)] = V_i \underbrace{A_{N_{MB}}}_{V_o} \cdot e^{-\frac{t}{\zeta_L}}$$




$$t^* \ll \zeta_L$$

$$V_o(t) = V_o \cdot \left(1 - \frac{t}{\tau_L} + \underbrace{\dots}_{\text{NEGIGIBLE}}\right) \approx V_o \left(1 - \frac{t}{\tau_L}\right) \quad \forall t \in [0, t^*]$$

$$\Delta V_o = V_o - V_o(t^*) = V_o - V_o + V_o \frac{t^*}{\tau_L}$$
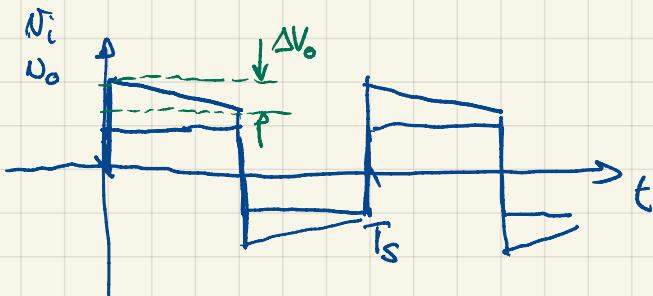
$$\frac{\Delta V_o}{V_o} = \frac{t^*}{\tau_L} \Rightarrow \boxed{\omega_L = \frac{1}{t^*} \cdot \frac{\Delta V_o}{V_o}}$$



$$T_s \ll \tau_L$$


$$t^* = \frac{T_s}{2} \Rightarrow \boxed{\omega_L = \frac{2}{T_s} \cdot \frac{\Delta V_o}{V_o}}$$

## HIGH FREQUENCY RESPONSE

$$A_{V_{HF}}(s) = \frac{1}{1 + s\tau_H}$$

STEP RESPONSE ANALYSIS

$$\Theta(s) = \frac{V_o}{s}$$

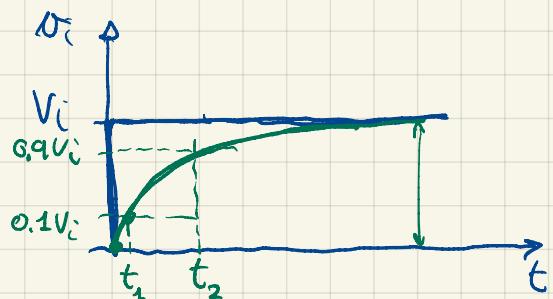

$$V_o(s) = \frac{V_i}{s(1 + s\tau_H)} = V_i \left[ \frac{1}{s} - \frac{\tau_H}{1 + s\tau_H} \right]$$

$$\mathcal{L}^{-1}[V_o(s)] = V_i \left(1 - e^{-\frac{t}{\tau_H}}\right)$$

$$t_r \triangleq t_2 - t_1$$

RISE TIME OF THE STEP RESPONSE

$$\begin{cases} V_o(t_1) = V_i \left(1 - e^{-\frac{t_1}{\tau_H}}\right) = 0.1 V_i \\ V_o(t_2) = V_i \left(1 - e^{-\frac{t_2}{\tau_H}}\right) = 0.9 V_i \end{cases}$$



$$\begin{cases} 0.9 V_i = e^{-\frac{t_2}{\tau_H}} \\ 0.1 V_i = e^{-\frac{t_1}{\tau_H}} \end{cases} \Rightarrow g = e^{\frac{t_2-t_1}{\tau_H}} = e^{\frac{t_2}{\tau_H}}$$

$$\ln(g) = \frac{t_2}{\tau_H} \quad \Rightarrow \quad \omega_H = \frac{\ln(g)}{t_2} \approx \frac{2.2}{t_2}$$

WE CAN PUT IT ALL TOGETHER AND FIND


$$V_o(s) = \frac{V_i}{s} A_{vO}(s) = V_i \frac{\tau_L}{(1+s\tau_L)(1+s\tau_H)} \cdot A_{vMB}$$
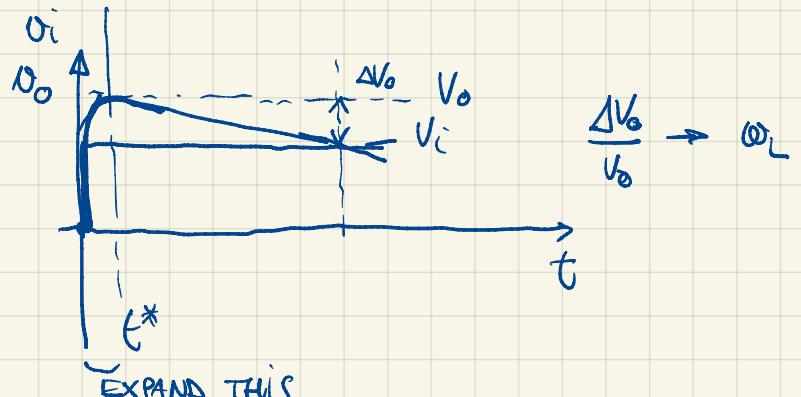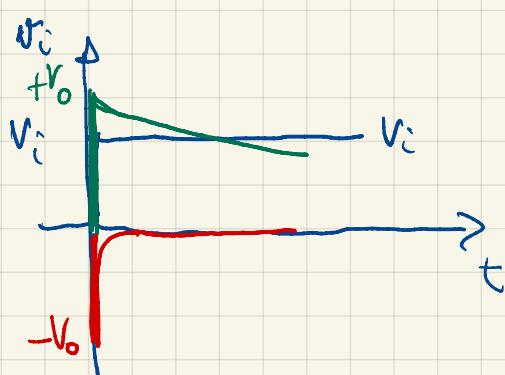
$$\mathcal{L}^{-1}[V_o(s)] = \underbrace{A_{vMB} V_i}_{V_o} \underbrace{\frac{\tau_L}{\tau_L - \tau_H}}_{\frac{1}{1 + s(\tau_L - \tau_H)}} \left( e^{-\frac{t}{\tau_L}} - e^{-\frac{t}{\tau_H}} \right)$$



IN CONCLUSION:

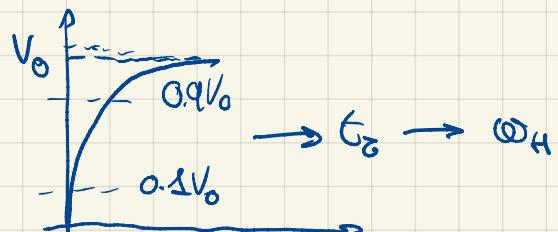BECAUSE  $\tau_L \gg \tau_H$ , FROM  
A SINGLE STEP RESPONSE



WE CAN EXTRACT VERY ACCURATE ESTIMATION OF BOTH  $\omega_L$  AND  $\omega_H$

## DISTORTION ANALYSIS

Hyp: THE AMPLIFIER IS OPERATING AS A LTI SYSTEM

$$v_i(t) = \sum_{k=1}^{+\infty} V_{ik} \sin(2\pi k f_o t + \varphi_{ik})$$

$T_0$  IS THE PERIOD OF SIGNAL  $v_i \rightarrow f_o$  IS ITS FUNDAMENTAL FREQUENCY

APPLYING SUPERPOSITION (AMPLIFIER IS LINEAR TIME INVARIANT)

$$v_o(t) = \sum_{k=1}^{+\infty} \underbrace{|A_D(j2\pi k f_o)|}_{V_{ak}} V_{ik} \sin(2\pi k f_o t + \varphi_{ik} + \Phi_{Ak})$$

IN ORDER TO HAVE NO DISTORTION

$$\left\{ \begin{array}{l} v_o(t) = A v_i(t) \\ \text{OR ELSE} \end{array} \right.$$

↑  
CONSTANT

$$v_o(t) = A v_i(t - t_A)$$

TIME SHIFT (AKA LINEAR PHASE)

WHICH MEANS

$$\left\{ \begin{array}{l} 1. |A_D(j2\pi k f_o)| = \text{CONSTANT } \forall k \\ 2. \frac{\Phi_{Ak}}{2\pi k f_o} = \text{CONSTANT } \forall k \Rightarrow \text{LINEAR PHASE RESPONSE} \end{array} \right.$$

$$\frac{\Phi_{Ak}}{2\pi k f_o} = -t_A \rightarrow \Phi_{Ak} = -2\pi k f_o t_A$$

$$\rightarrow \sin(2\pi k f_o (t - t_A) + \varphi_{ik})$$

$$\text{IN PARTICULAR, } \Phi_{Ak} = m \cdot 2\pi \quad m \in [0, 1, 2, 3, \dots]$$

GUARANTEES NO DISTORTION.

## ◊ SHORT CIRCUIT TIME CONSTANT (SCTC) METHOD


PURPOSE : DERIVING AN ESTIMATION OF  $\omega_L$  FROM THE CIRCUIT SCHEMATIC

$$A_{V_{LF}}(s) = A_{V_{MB}} \frac{N(s)}{1 + a_1 s + a_2 s^2 + \dots + a_m s^m}$$

LOW FREQUENCY RESPONSE

ORDER OF DENOMINATOR IS  $m$   
ORDER OF NUMERATOR IS  $m$

$$m = m$$

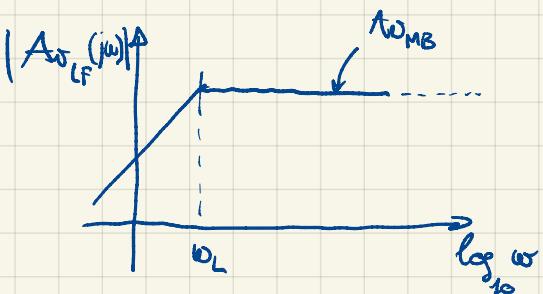

$$\lim_{s \rightarrow 0} A_{V_{LF}}(s) = \text{CONST}$$

COEFFICIENTS  $a_i$  ARE REAL NUMBERS  $\Rightarrow$  POLES ARE COMPLEX IN GENERAL ; BUT ALWAYS IN COUPLES (CONJUGATE POLES)

IN AMPLIFIERS WHERE NO FEEDBACK IS APPLIED, POLES ARE OFTEN PURELY REAL AND, IN ANY CASE, NEGATIVE REAL PART.  
INDEED ANY ELECTRONIC AMPLIFIER IS NORMALLY OPEN LOOP STABLE