

4/10/2022

◇ SHORT CIRCUIT TIME CONSTANT (SCTC) METHOD

PURPOSE: DERIVING AN ESTIMATION OF ω_L FROM THE CIRCUIT SCHEMATIC


$$A_{OL,LF}(s) = A_{OL,MB} \frac{N(s)}{1 + a_1 s + a_2 s^2 + \dots + a_m s^m} \quad \text{LOW FREQUENCY RESPONSE}$$

ORDER OF DENOMINATOR IS m

ORDER OF NUMERATOR IS m

$$m = m$$
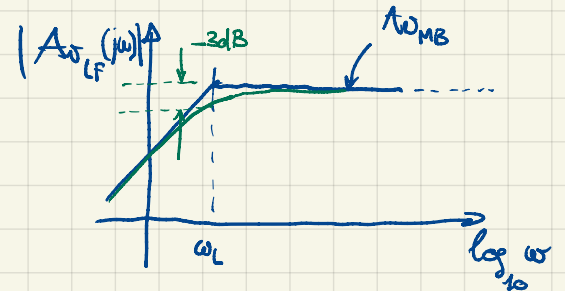
$$\lim_{s \rightarrow \infty} A_{OL,LF}(s) = \text{CONST}$$




COEFFICIENTS a_i ARE REAL NUMBERS \Rightarrow POLES ARE COMPLEX IN GENERAL, BUT ALWAYS IN COUPLES (CONJUGATE POLES)

IN AMPLIFIERS WHERE NO FEEDBACK IS APPLIED, POLES ARE OFTEN PURELY REAL AND, IN ANY CASE, NEGATIVE REAL PART. INDEED ANY ELECTRONIC AMPLIFIER IS NORMALLY OPEN LOOP STABLE

◇ Hypothesis: All poles are REAL (AND NEGATIVE)

- AN AMPLIFIER CIRCUIT WITH CAPACITORS ONLY (NO INDUCTOR) AND NO FEEDBACK HAS REAL POLES
- THE CIRCUIT HAS BEEN LINEARIZED AROUND A SPECIFIC OPERATING POINT \rightarrow FREQUENCY RESPONSE IS A SMALL SIGNAL ATTRIBUTE OF AN AMPLIFIER

LINEAR MODEL COMPONENTS

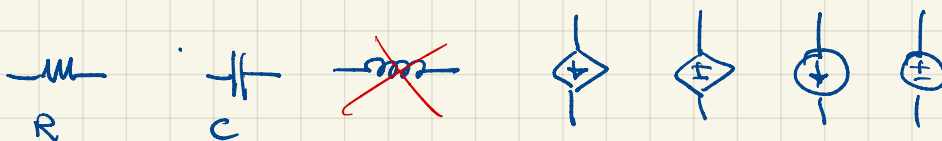

$$D(s) = 1 + a_1 s + a_2 s^2 + \dots + a_m s^m = \prod_{i=1}^m (1 + s\tau_i)$$

WITHOUT LOSS OF GENERALITY WE ASSUME THAT

$$\tau_1 < \tau_2 < \tau_3 < \dots < \tau_m$$

$$a_1 = z_1 + z_2 + \dots + z_m$$

$$a_2 = z_1 z_2 + z_1 z_3 + \dots + z_{m-1} z_m$$

$$a_{m-1} = z_1 z_2 \dots z_{m-1} + z_1 z_2 \dots z_{m-2} z_m + \dots + z_2 z_3 \dots z_{m-1} z_m$$

$$a_m = z_1 z_2 z_3 \dots z_m$$

$$\frac{a_{m-1}}{a_m} = \frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_m} = \omega_1 + \omega_2 + \dots + \omega_m$$

↑ HIGHEST FREQUENCY

a_1, a_2 AND $\frac{a_{m-1}}{a_m}$ CAN BE FOUND FROM THE CIRCUIT APPLYING THE FOLLOWING THEOREMS

FOR A LINEAR CIRCUIT WITH N INDEPENDENT CAPACITORS

THEOREM # 1

$$a_1 = \sum_{i=1}^N C_i R_i^0$$

R_i^0 : RESISTANCE SEEN FROM CAPACITOR C_i WHEN THE REMAINING ONES ARE OPEN

THEOREM # 2

$$a_2 = \sum_{i=1}^{N-1} \sum_{k=i+1}^N C_i C_k R_i^0 R_k^i = \sum_{i=1}^{N-1} \sum_{k=i+1}^N C_i C_k R_k^0 R_i^k$$

WHERE R_i^k IS THE RESISTANCE SEEN FROM CAPACITOR C_i WHEN THE REMAINING ONE ARE OPEN EXCEPT C_k THAT IS SHORTED

THEOREM # 3

$$\frac{a_{m-1}}{a_m} = \sum_{i=1}^N \frac{1}{C_i R_i^{\infty}}$$


WHERE R_i^{SC} IS THE RESISTANCE SEEN FROM CAPACITOR C_i WHEN THE REMAINING ONES ARE SHORT-CIRCUITED

◇ SCTC METHOD

- #1 LINEARISE THE AMPLIFIER CIRCUIT AROUND THE OP
- #2 TURN ALL INDEPENDENT SOURCES OFF
- #3 ELIMINATE REDUNDANT CAPACITORS TO HAVE ONLY INDEPENDENT ONES IN THE CIRCUIT
- #4 CALCULATE $\frac{a_{m-1}}{a_m}$ FROM THEOREM #3
- #5 ASSUMING A DOMINANT POLE EXISTS, ESTIMATE ω_L AS



$$\omega_L \approx \frac{a_{m-1}}{a_m} = \sum_{i=1}^N \frac{1}{C_i R_i^{SC}}$$

INDEPENDENT CAPACITORS ?

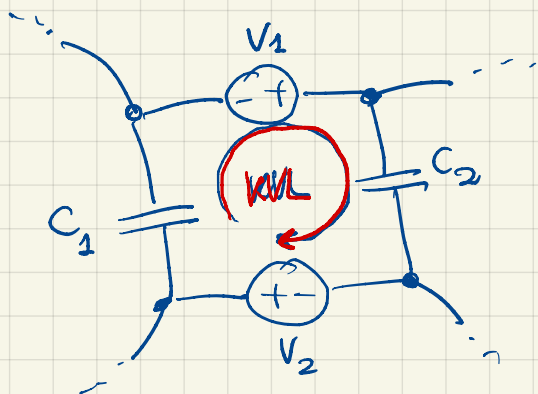


CAPACITORS IN A LOOP WITH VOLTAGE SOURCES ARE NOT INDEPENDENT!

AS A PARTICULAR CASE: $V_1 = V_2 = 0$

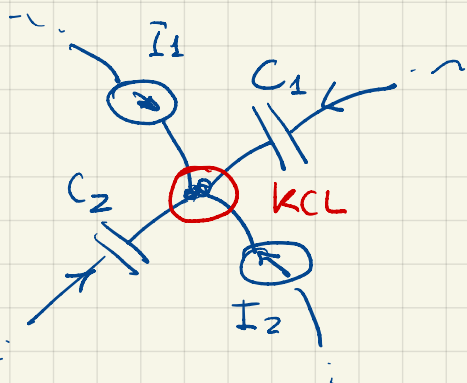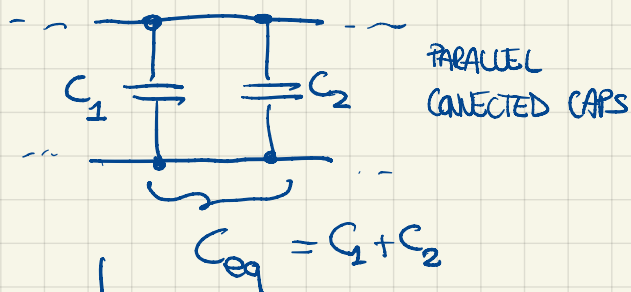

CAPACITORS IN A NODE WITH CURRENT SOURCES ARE NOT INDEPENDENT

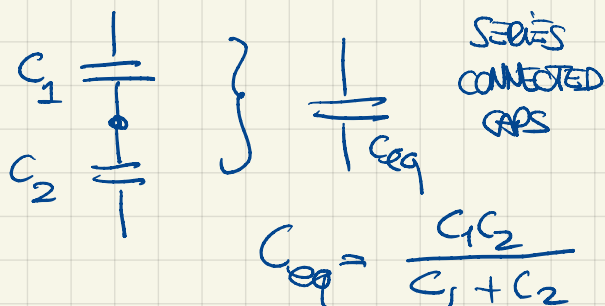AS A PARTICULAR CASE, SETTING $I_1 = I_2 = 0$



AFTER STRIPPING ALL DEPENDENT CAPACITORS OFF THE CIRCUIT

$$N = m$$

THE NUMBER OF CAPS IS EQUAL TO THE ORDER OF $D(s)$ I.E. TO THE NUMBER OF POLES.

SPECIAL CASE IS $m = N = 2$. HERE WE CAN FIND:

$$\left. \begin{aligned} a_1 &= C_1 R_1^0 + C_2 R_2^0 \\ a_2 &= C_1 C_2 R_1^0 R_2^1 = C_1 C_2 R_2^0 R_1^1 \end{aligned} \right\} \text{THESE ARE THE EXACT COEFFICIENTS OF } D(s) \text{ (FOR A LINEAR CIRCUIT)}$$

THEREFORE WE NOW KNOW $D(s) = 1 + a_1 s + a_2 s^2$
FROM WHICH WE CAN FIND P_1 AND P_2 (THE POLES OF THE NETWORK) \Rightarrow WE CAN FIND ω_L EXACTLY

BUT WE CAN ALSO CALCULATE

$$\frac{a_1}{a_2} = \frac{\cancel{C_1} R_1^0}{\cancel{C_1} \cancel{C_2} R_2^1} + \frac{\cancel{C_2} R_2^0}{\cancel{C_2} \cancel{C_1} R_1^1} = \frac{1}{\underbrace{C_2 R_2^1}_{\omega_1} + \underbrace{C_1 R_1^1}_{\omega_2}}$$

$$R_2^1 = R_2^{SC} \quad \text{AND} \quad R_1^1 = R_1^{SC}$$

SO WE HAVE DEMONSTRATED THEOREM #3, AT LEAST FOR THIS CASE

IF WE FORGET ABOUT ALL THIS AND JUST TAKE


$$\omega_L \approx \frac{a_1}{a_2} \quad \text{WE ARE APPROXIMATING THE VALUE OF } \omega_L$$

THE ESTIMATION IS ACCURATE AS LONG AS THERE IS A DOMINANT POLE, WHOSE FREQUENCY IS MUCH LARGER THAN THE REST.


CASE #1

$$\omega_1 \approx \omega_L$$

ACCURACY IS GOOD

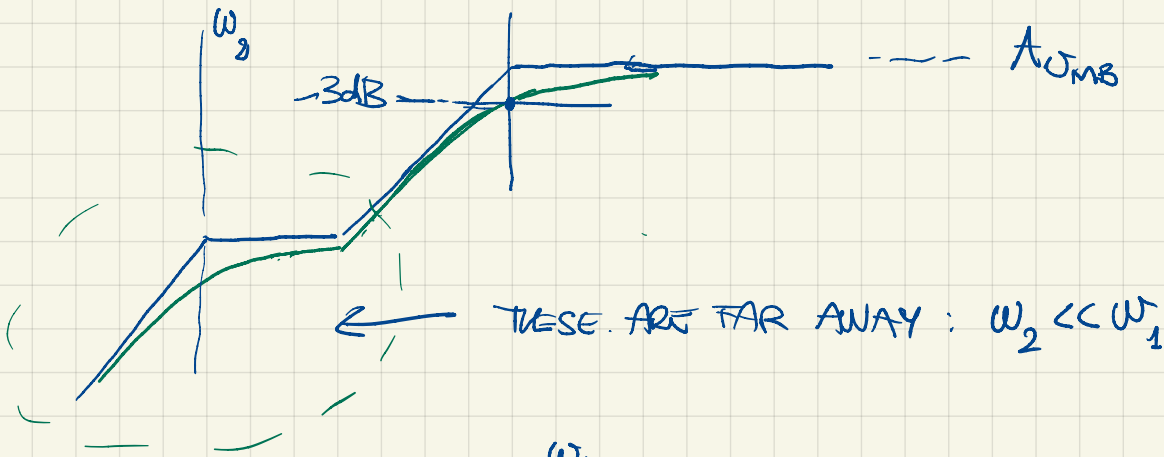

CASE #2

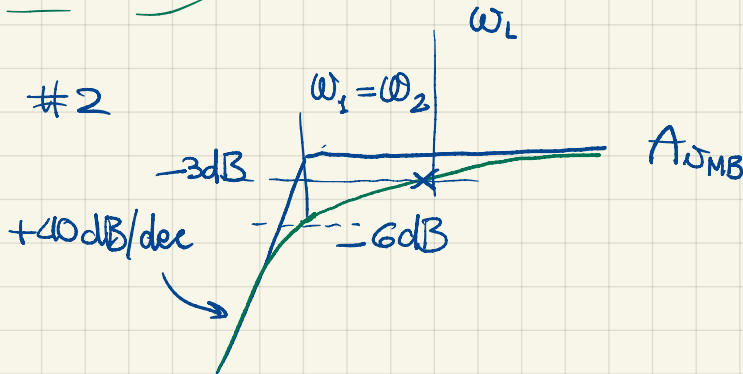


APPLYING SCTC WE WILL CONSIDER $\hat{\omega}_L = 2\omega_1$

ESTIMATION OF ω_L

QUESTION: HOW FAR IS ω_L FROM $\hat{\omega}_L$? **FIND OUT AS AN EXERCISE!**

EXAMPLE: LET'S CONSIDER A CE AMPLIFIER

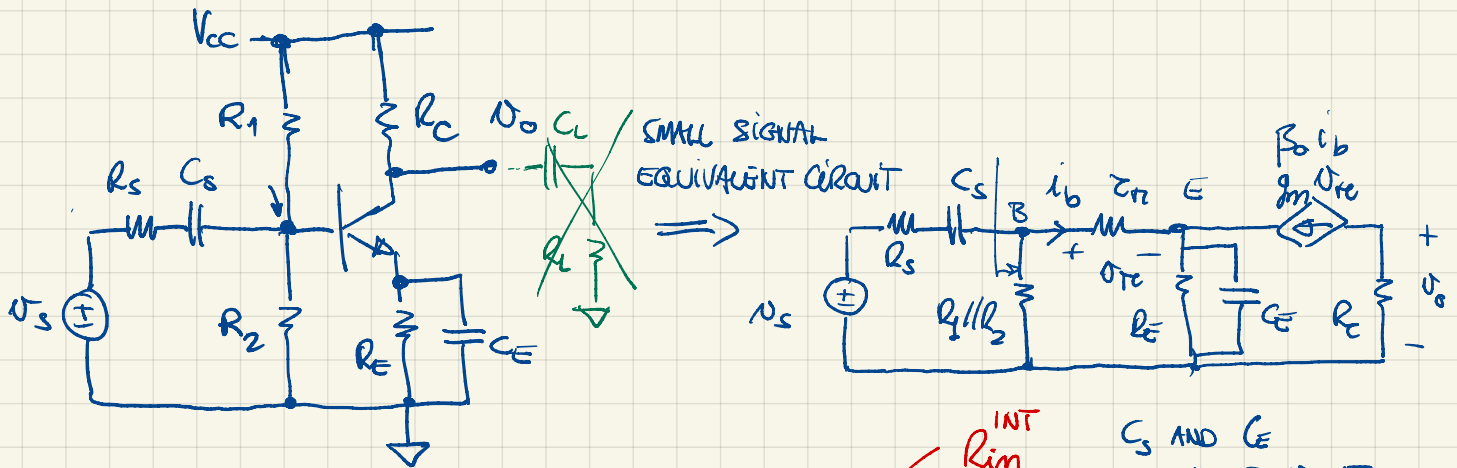

$$A_{0MB} = - \underbrace{g_m R_C}_{\text{INTRINSIC GAIN OF THE CE STAGE}} \cdot \underbrace{\alpha_i}_{\text{INPUT ATTENUATION FACTOR}} = - \frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_s + R_1 \parallel R_2 \parallel r_{\pi}} \cdot g_m R_C$$


< 1

INTRINSIC GAIN OF THE CE STAGE

INPUT ATTENUATION FACTOR

INT R_{in}

C_s AND C_E ARE INDEPENDENT

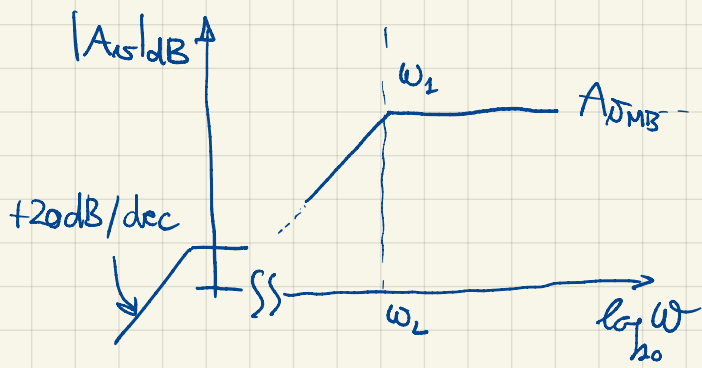

$$A_0(s) = \frac{s \zeta_0 (1 + s \zeta_z)}{1 + a_1 s + a_2 s^2} \cdot A_{\text{MIS}}$$

#1 APPROACH \leftrightarrow "BRUTE FORCE" APPROACH



TO DO AS EXERCISE

#2 APPROACH \leftarrow "EDUCATED" APPROACH



USE THEOREMS

$$a_1 =$$

USE THEOREM 1

$$a_2 =$$

USE THEOREM 2

} $\rightarrow \omega_L$

OR ELSE

$$\frac{a_1}{a_2} = \dots$$

USE THEOREM 3

$\rightarrow \omega_L$