

$$A_D(s) = \frac{s\zeta_p (1 + s\zeta_z)}{1 + a_1 s + a_2 s^2} \cdot A_{MIS}$$

$\frac{1}{RC}$

#1 APPROACH \leftrightarrow "BRUTE FORCE" APPROACH



TO DO AS EXERCISE

#2 APPROACH \leftarrow "EDUCATED" APPROACH



USE THEOREMS

$$a_1 = R_S^0 C_S + R_E^0 C_E$$

$$a_2 = C_S C_E R_E^E R_S^E$$

$$R_S^0 = R_S + R_1 \parallel R_2 \parallel R_{CE}^N$$

$$R_{CE}^N = r_{ce} + (\beta_0 + 1) R_E \propto 10^4 [\Omega]$$

$$R_E^0 = R_E \parallel R_{CC}^{OUT} \leftarrow$$

$$R_{CC}^{OUT} = \frac{R_1 \parallel R_2 + r_{ce}}{\beta_0 + 1} \propto 10^2 [\Omega] \left(\approx \frac{1}{g_m} \right)$$

$$R_S^E = R_S + R_1 \parallel R_2 \parallel R_{CE}^N$$

$$R_{CE}^N = r_{ce}$$

NOW a_1 AND a_2 ARE KNOWN \rightarrow WE CAN FIND THE ROOTS OF $1 + a_1 s + a_2 s^2 = 0$

USING SCFC

$$\frac{a_1}{a_2} = \frac{1}{C_S R_S^{SC}} + \frac{1}{C_E R_E^{SC}} \stackrel{!}{=} 10^2 \text{ (rad/s)}$$

THIS TERM TENDS TO DOMINATE

$$R_S^{SC} = R_S^E \propto 10^3 [\Omega]$$

$$R_E^{SC} = R_E \parallel \frac{R_S \parallel R_1 \parallel R_2 + r_{ce}}{\beta_0 + 1} \propto 10^2 [\Omega]$$


IF THERE IS A DOMINANT POLE

$$\omega_L \approx \frac{a_1}{a_2}$$

DESIGN CRITERIA ARE $C_E \approx \frac{1}{R_E^{SC} \omega_L}$ $C_S \approx C_E$

WHAT ABOUT THE NUMERATOR? WE NEED TO FIND ζ_0 AND ζ_z .

LET'S CONSIDER THE ADMITTANCES

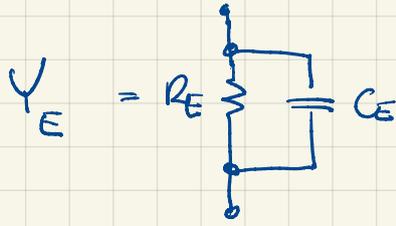

$$Y_E = sC_E + \frac{1}{R_E} \stackrel{!}{=} 0 \rightarrow s = -\frac{1}{R_E C_E}$$

IF $Y_E = 0$ THEN $i_b = 0$ ($i_b \cdot \beta_0 \cdot i_b = 0$) AND THEN $N_0 = 0$!

WE HAVE A ZERO AT $\omega_z = \frac{1}{R_E C_E} \Rightarrow \zeta_z = R_E C_E$

FINALLY, WE CAN FIND ζ_0


$$\lim_{\omega \rightarrow \infty} A_v(j\omega) = A_{v_{MS}} \cdot \frac{\zeta_0 \zeta_z}{a_2} = A_{v_{MS}} \Rightarrow$$

$$\Rightarrow \zeta_0 = \frac{a_2}{\zeta_z} = \frac{C_S C_E R_E^0 R_S^E}{R_E C_E} = C_S \cdot \frac{R_E^0}{R_E} \cdot R_S^E$$

THE ANALYSIS IS NOW COMPLETE! TO BE COMPARED WITH BRUTE FORCE APPROACH!!

LESSON #3

BASIC NETWORK ANALYSIS

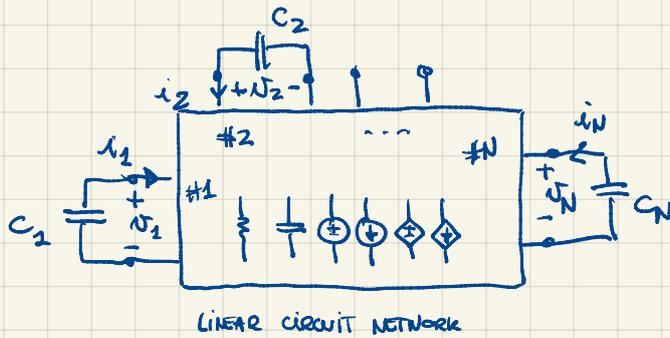

HYPOTHESIS:

1. CAPACITORS ARE THE ONLY REACTIVE COMPONENTS
2. CAPACITORS ARE ELECTRICALLY INDEPENDENT
3. THE RANK OF MATRIX $[R]$ IS FULL

N CAPACITORS $\Rightarrow m = N = n$

LET'S CONSIDER THE NETWORK MATRIX $[R]$

$$\begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{bmatrix} = \begin{bmatrix} R_{11} & R_{12} & \dots & R_{1N} \\ R_{21} & R_{22} & & \\ \vdots & & & \\ R_{2N} & & & R_{NN} \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix}$$

(1) $\vec{v} = [R] \vec{i}$

$$R_{ij} \triangleq \frac{v_i}{i_j} \Big|_{i_k=0 \text{ } \forall k \neq j}$$

$$R_{ii} = \frac{v_i}{i_i} \triangleq R_i^0$$

AND THE BOT EQUATION

$$\begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix} = - \begin{bmatrix} C_1 & C_2 & \dots & \emptyset \\ \emptyset & \dots & \dots & C_N \end{bmatrix} \begin{bmatrix} \dot{v}_1 \\ \dot{v}_2 \\ \vdots \\ \dot{v}_N \end{bmatrix}$$

(2) $\vec{i} = - [C] \cdot \dot{\vec{v}}$

(1) AND (2) YIELD $\vec{v} = - [R][C] \dot{\vec{v}}$ (3)

REWRITING (3) MULTIPLYING TIMES $[C^{-1}][G]$ $G = R^{-1}$

$$\dot{\vec{v}} = - \underbrace{[C^{-1}G]}_{\text{STATE MATRIX OF THE CIRCUIT}} \vec{v}$$

STATE MATRIX OF THE CIRCUIT

LET'S CALCULATE THE CHARACTERISTIC POLYNOMIAL OF THE NETWORK

$$\det [sI_N + C^{-1}G] = 0$$

MULTIPLYING TIMES $\det [RC] \neq 0$

$$\Leftrightarrow \det [sRC + I_N] = 0$$

LET'S SOLVE THE EQUATION (MANUALLY) FOR $N=3$

$$\det \begin{bmatrix} sR_{11}C_1 + 1 & sR_{12}C_1 & sR_{13}C_1 \\ sR_{21}C_2 & sR_{22}C_2 + 1 & sR_{23}C_2 \\ sR_{31}C_3 & sR_{32}C_3 & sR_{33}C_3 + 1 \end{bmatrix} =$$

$$= (sR_{11}C_1 + 1) \left[(sR_{22}C_2 + 1)(sR_{33}C_3 + 1) - s^2 R_{32}R_{23}C_2C_3 \right] +$$

$$- sR_{12}C_1 \left[sR_{21}C_2 (sR_{33}C_3 + 1) - s^2 R_{23}R_{31}C_2C_3 \right] +$$

$$+ sR_{13}C_1 \left[s^2 R_{21}R_{32}C_2C_3 - sR_{31}C_3 (sR_{22}C_2 + 1) \right].$$

$$a_1 = R_{11}C_1 + R_{22}C_2 + R_{33}C_3 = \sum_{i=1}^3 R_i^0 C_i \quad \text{PROOF OF THEOREM \#1}$$

$$a_2 = R_{22}R_{33}C_2C_3 + R_{11}R_{22}C_1C_2 + R_{11}R_{33}C_1C_3 - R_{32}R_{23}C_2C_3 +$$

$$- R_{12}R_{21}C_1C_2 - R_{13}R_{31}C_1C_3 =$$

$$= \sum_{i=1}^2 \sum_{j=i+1}^3 C_i C_j (R_{ii}R_{jj} - R_{ij}R_{ji}) = \sum_{i=1}^2 \sum_{j=i+1}^3 C_i C_j R_i^0 \left(R_j^0 - \frac{R_{ij}R_{ji}}{R_i^0} \right)$$

BUT WE CAN PROVE THAT

$$R_i^0 - \frac{R_{ij}R_{ji}}{R_i^0} = R_j^0$$

DEMONSTRATION: LET'S CALCULATE THE RELATION BETWEEN U_i, u_i AND U_j, u_j

$$\begin{cases} \sigma_i = R_{ii} i_i + R_{ij} i_j \\ \sigma_j = R_{jj} i_j + R_{ji} i_i \end{cases}$$

LET'S ASSUME THAT $\sigma_i \equiv 0$ (PORT i IS SHORTED!)

THEN

$$i_i = - \frac{R_{ij} i_j}{R_{ii}}$$

WHICH YIELDS

$$\sigma_j = \left(R_{jj} - \frac{R_{ij} R_{ji}}{R_{ii}} \right) i_j$$

$$\frac{\sigma_j}{i_j} \Big|_{\sigma_i=0} \triangleq R_j^i = R_{jj} - \frac{R_{ij} R_{ji}}{R_{ii}} \quad \text{c.o.d.}$$

IN THE SAME WAY, WE CAN ALSO PROVE THAT


$$R_i^j = R_i^0 - \frac{R_{ji} R_{ij}}{R_j^0}$$

FROM WHICH, IN CONCLUSION, FOLLOWS THAT

$$R_i^j R_j^0 = R_j^i \cdot R_i^0 \quad \bullet$$

PROOF OF THEOREM #2

HIGH FREQUENCY RESPONSE

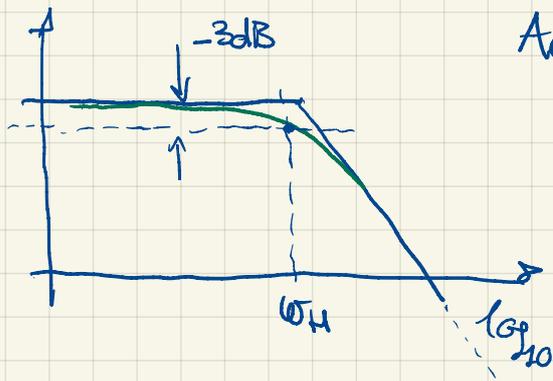

$$A_{HF}(s) = A_{N_{MB}} \frac{N(s)}{1 + a_1 s + a_2 s^2 + \dots + a_N s^N}$$

IN THIS CASE

$$N > m$$

↑
ORDER OF THE
NUMERATOR

$N - m \rightarrow$ HIGH FREQUENCY ROLL-OFF

$$N - m = \begin{cases} 1 & -20 \text{ dB/dec} \\ 2 & -40 \text{ dB/dec} \\ \vdots & \end{cases}$$

REMEMBERING THAT

$$a_1 = \tau_1 + \tau_2 + \tau_3 + \dots$$

AND ASSUMING THAT THERE IS A DOMINANT POLE THEN

$$\omega_1 \ll \omega_2 < \omega_3 < \dots < \omega_N$$

THEN $a_1 \approx \tau_1 \Rightarrow$ WE ESTIMATE $\omega_H \approx \frac{1}{a_1}$

THE SO CALLED **OCTC METHOD** CONSISTS IN ASSUMING A DOMINANT POLE AND ESTIMATING

$$\omega_{fe} \approx \frac{1}{\sum_{i=1}^N R_i^0 C_i}$$

IN THIS CASE $a_2 \approx \tau_1 \tau_2 \approx a_1 \tau_2 \Rightarrow \omega_2 \approx \frac{a_1}{a_2}$

AND THEREFORE

$$\frac{\omega_2}{\omega_1} = \frac{a_1^2}{a_2} \gg 1 \Leftrightarrow \text{WE HAVE A DOMINANT POLE}$$