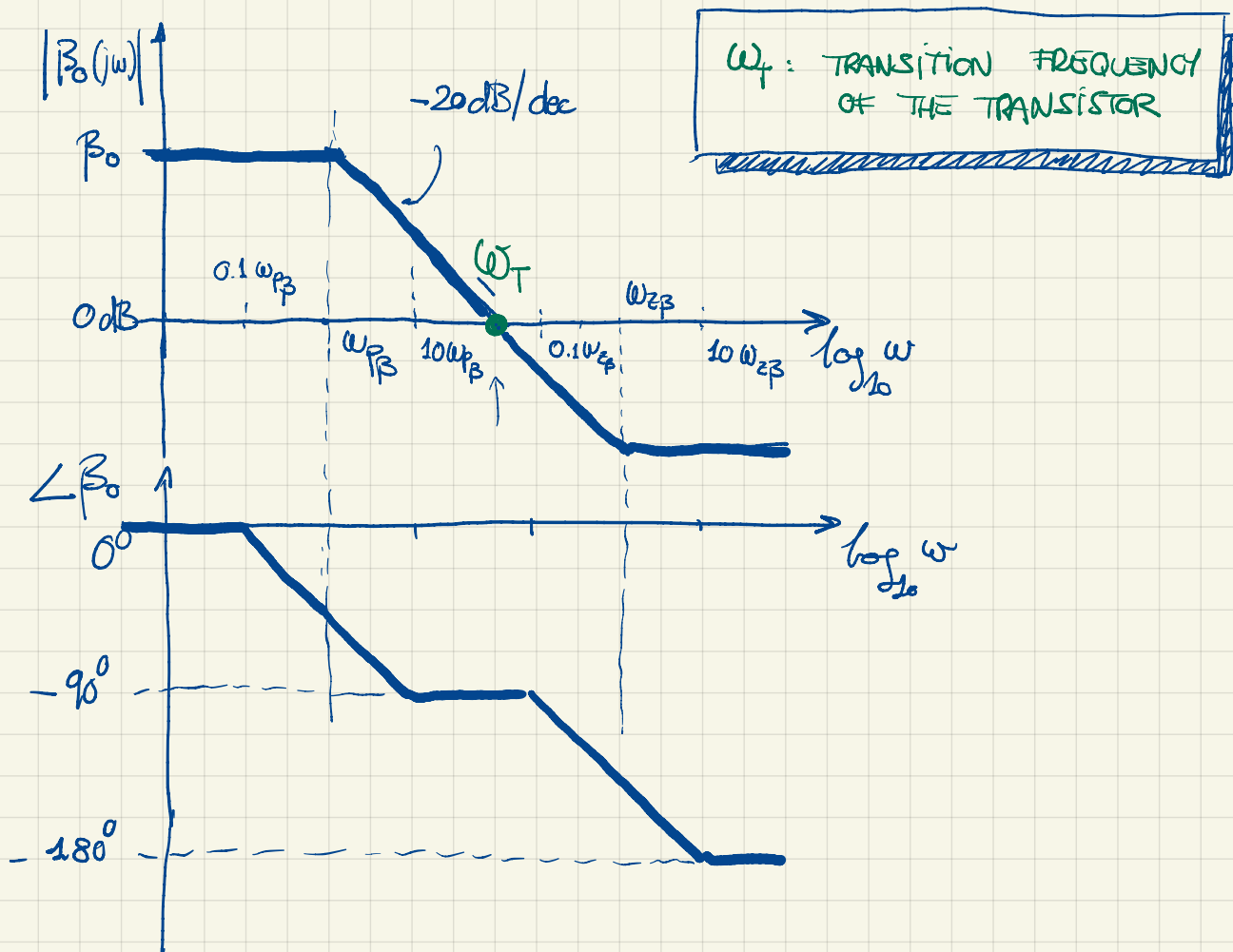


$$|\beta_0(\omega_{z\beta})| = \beta_0 \cdot \frac{\sqrt{2}}{\sqrt{1 + \left(\frac{\omega_{z\beta}}{\omega_{p\beta}}\right)^2}} = \frac{\sqrt{2}}{1 + \frac{C_{ce}}{C_{\mu}}} \ll 1$$

$\omega_{z\beta} \gg \omega_{p\beta}$



TO FIND ω_T , WE APPROXIMATE $\beta_0(s)$ LIKE:

$$\beta_0(s) = \frac{\beta_0}{1 + s/\omega_{p\beta}}$$

THE EFFECT OF THE ZERO IS NEGLIGIBLE
 ↓
 BECAUSE $\omega_{p\beta} \ll \omega_T \ll \omega_{z\beta}$

ALONG THE -20 dB/dec ASYMPTOTE, $|\beta(j\omega)| \cdot \omega$ IS CONSTANT. THEREFORE

$$\beta_0 \cdot \omega_{p\beta} = 1 \cdot \omega_T \Rightarrow \omega_T = \frac{\beta_0}{C_{ce}(C_{ce} + C_{\mu})} = \frac{g_m}{C_{ce} + C_{\mu}} \approx \frac{g_m}{C_{ce}} = \frac{1}{\tau_F}$$

FOR THE MOSFET $\omega_T = \frac{g_m}{C_{gs}}$ EXACTLY SYMMETRICAL

ω_T MOSFET $\ll \omega_T$ BJT FOR SIMILAR VOLTAGE/CURRENT RATINGS.

HF ANALYSIS OF THE CE AMPLIFIER


11/10/2022

C_S, C_L, C_E ARE RESPONSIBLE FOR THE LOW FREQUENCY RESPONSE OF THE AMPLIFIER.


IN GENERAL $\omega_L = f(C_S, C_E, C_L)$



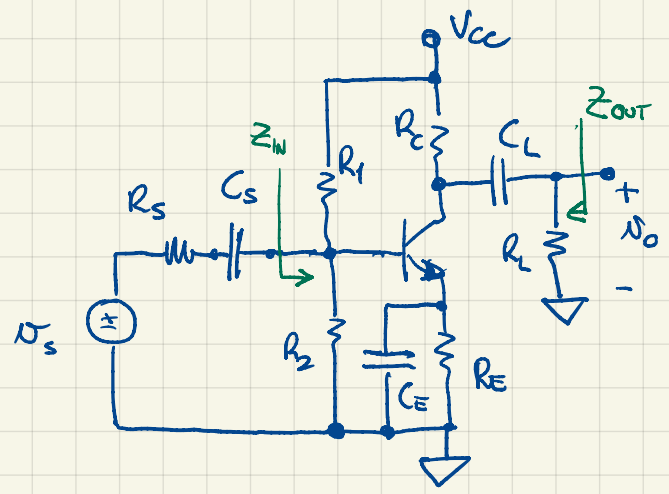THEY HAVE NO EFFECT AT HF AS THEY APPEAR TO BE LIKE SHORT CIRCUITS



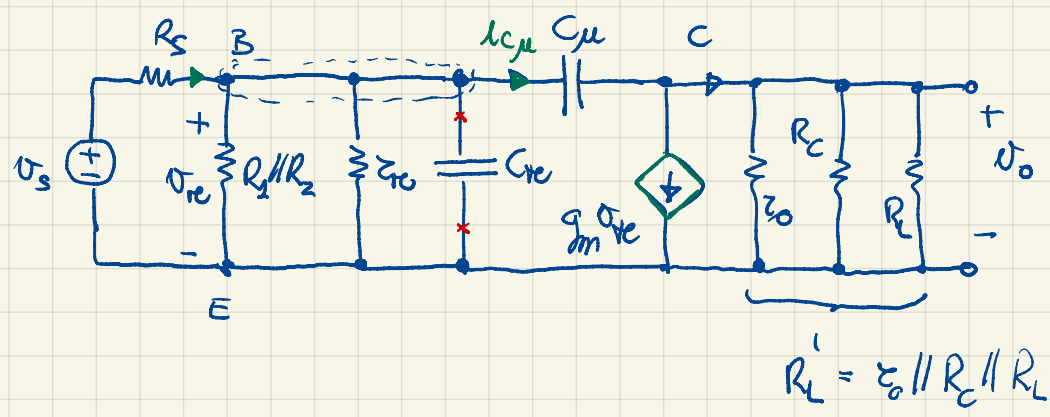LET'S DRAW THE SMALL SIGNAL EQUIVALENT CIRCUIT AT HF, WE ASSUME THE SMALL SIGNAL MODEL PARAMETERS ARE KNOWN FROM **BIAS POINT ANALYSIS** REUSE !!



$C_{ce} \in [20 \text{ pF} \div 100 \text{ pF}]$
 $C_{\mu} \in [1 \div 5 \text{ pF}]$

$$R_L' = r_o \parallel R_C \parallel R_L$$

LET'S FIND $A_{V.O.}^{HF}(s) \triangleq \frac{V_o(s)}{V_s(s)} = \frac{v_o}{v_s}$

→ BRUTE FORCE APPROACH

$$v_o = R_L' \left[sC_{\mu} (v_{ce} - v_o) - g_m v_{be} \right] \quad (1)$$

$$v_{be} = \frac{z_{in} \parallel R_1 \parallel R_2}{1 + sC_{ce} r_{ce} \parallel R_1 \parallel R_2} \cdot \left[\frac{v_s - v_{ce}}{R_s} - sC_{\mu} (v_{be} - v_o) \right] \quad (2)$$

PROCEDURE: FROM (2) WE CAN FIND $v_{be} = f(v_o)$. REPLACING v_{be} IN (1) WE CAN ELIMINATE IT AND SOLVE FOR v_o .

— "LAZY" APPROACH : USE OCTC METHOD

#1 : LET'S FIND THE MID-BAND GAIN A_{V}^{MB} CONSIDERING C_{π} AND C_{μ} OPEN


$$A_{V}^{MB} = -\alpha_{in} g_m R_L' \quad \text{WITH } \alpha_{in} = \frac{z_c \parallel R_2 \parallel R_2}{R_s + z_c \parallel R_2 \parallel R_2}$$

WE CAN ALSO WRITE α_{in} AS $\alpha_{in} = \frac{R_{in}^{\circ}}{R_s}$

LET'S CALCULATE α_1 AND α_2

$$R_{re}^{\circ} = R_s \parallel z_c \parallel R_2 \parallel R_2 \in [10^2 - 10^3 \Omega]$$
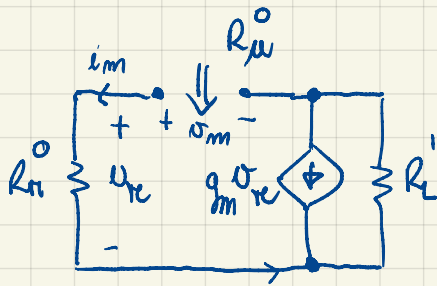
$$R_{\mu}^{\circ} = R_L' + R_{\pi}^{\circ} (1 + g_m R_L') = R_{re}^{\circ} + R_L' (1 + g_m R_{re}^{\circ}) \in [10^5 - 10^6 \Omega]$$



$$0_{in} = R_{re}^{\circ} i_{in} + R_L' (i_{in} + g_m R_{\pi}^{\circ} i_{in})$$

$$R_{\mu}^{\circ} \stackrel{\Delta}{=} \frac{0_{in}}{i_{in}} = R_{re}^{\circ} + R_L' (1 + g_m R_{\pi}^{\circ})$$

$$= R_L' + R_{\pi}^{\circ} (1 + g_m R_L')$$

MILLER MULTIPLIER

$$1 - A_{V,MAX}^{MB}$$

$$a_1 = C_{re} \cdot R_{re}^{\circ} + C_{\mu} \cdot R_{\mu}^{\circ} \propto 10^{-7}$$

$$a_2 = C_{re} C_{\mu} R_{re}^{\circ} R_{\mu}^{\circ} = C_{re} C_{\mu} R_{\mu}^{\circ} R_{re}^{\mu}$$

USING THE FIRST, BY INSPECTION

$$a_2 = C_{re} C_{\mu} R_{\pi}^{\circ} R_L' = 10^{-22} \cdot 10^3 \cdot \underbrace{10^4}_{R_L'} = 10^{-15}$$

$$R_L' \in [10^3 - 10^4]$$

VERIFICATION OF DOMINANT POLE ASSUMPTION

$$\frac{a_1^2}{a_2} \gg 1$$

$$\frac{10^{-14}}{10^{-15}} = 10$$

WITH SENSIBLE VALUES OF R_L' IT IS NORMALLY POSSIBLE TO VERIFY THE DOMINANT POLE ASSUMPTION!

ASSUMING THE ERROR TO BE SMALL IN ANY CASE

$$\omega_H \approx \frac{1}{a_1}$$

SO FAR WE HAVE FOUND THAT

$$A_{v, HF}(s) = A_{v, MB} \cdot \frac{\left(1 - s \frac{C_{\mu}}{g_m}\right)}{1 + a_1 s + a_2 s^2} \quad \begin{array}{l} m=? \quad N(s) \text{ IS UNKNOWN} \\ m=2 \quad a_1, a_2 \text{ KNOWN} \end{array}$$

CIRCUIT INSPECTION AT $s \rightarrow +\infty$ SHOWS THAT $v_o \rightarrow 0$ TRACKING v_{in} SO, IT GOES TO ZERO AS $1/sC_{\mu}$

THIS MEANS $m=1$! \Rightarrow THERE IS ONE ZERO AT THE NUMERATOR.

TO LOCATE THE ZERO, WE TAKE COLLECTOR CURRENT INTO ACCOUNT.

$$i_c = sC_{\mu}(v_{re} - v_o) - g_m v_{re} \stackrel{!}{=} 0 \quad \forall v_s$$

THE CONDITION IMPLIES $v_o \equiv 0$ AND THEREFORE THE EQUATION BECOMES


$$sC_{\mu} v_{re} - g_m v_{re} = 0 \Rightarrow \text{WE HAVE A RHP ZERO}$$

$$\text{AT } s = \frac{g_m}{C_{\mu}} \Rightarrow N(s) = 1 - s \frac{C_{\mu}}{g_m} \quad \begin{array}{l} \text{VERY HIGH} \\ \text{FREQUENCY ZERO!} \\ \rightarrow \omega_T \end{array}$$

LET'S STUDY THE INPUT IMPEDANCE OF THE AMPLIFIER, $Z_{IN}(s)$

$$Z_{IN}(s) = Z_{\pi} \parallel R_1 \parallel R_2 \parallel \frac{1}{sC_{\mu}} \parallel Z_x(s) \quad \text{TO FIND } Z_x(s):$$

$$Z_x(s) = \frac{v_{re}}{i_{in}}$$

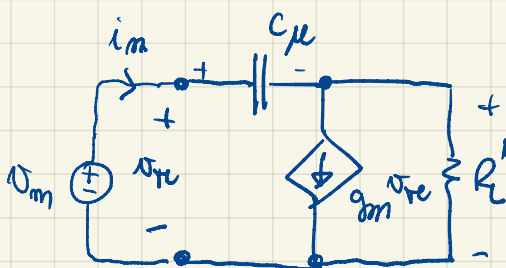

$$i_{in} \left(R'_L + \frac{1}{sC_{\mu}} \right) = v_{re} (1 + g_m R'_L)$$


$$i_{in} \cdot \frac{1}{sC_{\mu}} + R'_L (i_{in} - g_m v_{re}) = v_{re}$$

$$Z_x(s) = \frac{1 + sC_{\mu} R'_L}{(1 + g_m R'_L) sC_{\mu}}$$

$$Z_e(s) = \frac{1}{sC_{\mu}(1+g_m R_e')} + \frac{s\mu R_e'}{sC_{\mu}(1+g_m R_e')} = \frac{1}{sC_{eq}} + \underbrace{R_e' \parallel \frac{1}{g_m}}_{\approx \frac{1}{g_m}}$$

AS A RESULT, WE FOUND THAT

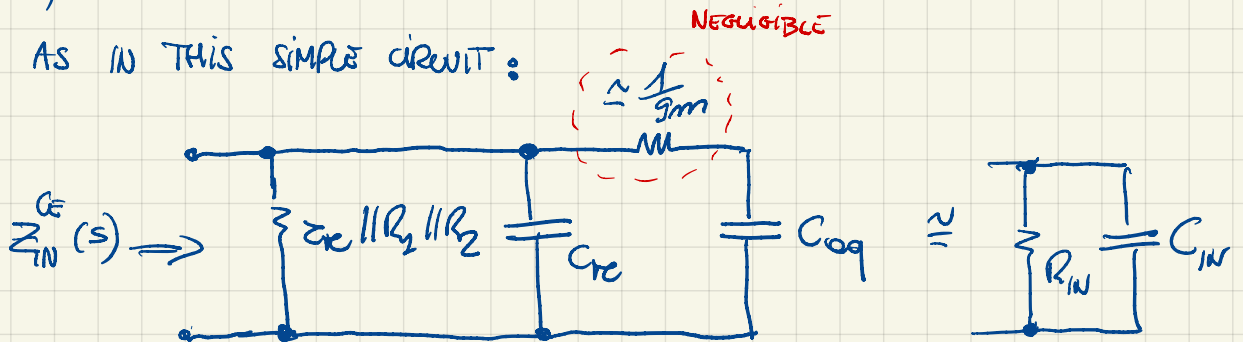$Z_{IN}(s)$ IS AS IN THIS SIMPLE CIRCUIT:



$$R_{IN} = r_{re} \parallel R_1 \parallel R_2$$

CE INPUT RESISTANCE

$$C_{IN} \approx C_{re} + \underbrace{C_{\mu}(1+g_m R_e')}_{\text{MILLER MULTIPLIER}} \leftarrow \text{MILLER EFFECT}$$

CONCLUSION: THE CE INPUT IMPEDANCE HAS A STRONG CAPACITIVE COMPONENT THAT IS DOMINATED BY C_{μ} , THROUGH **MILLER EFFECT**