
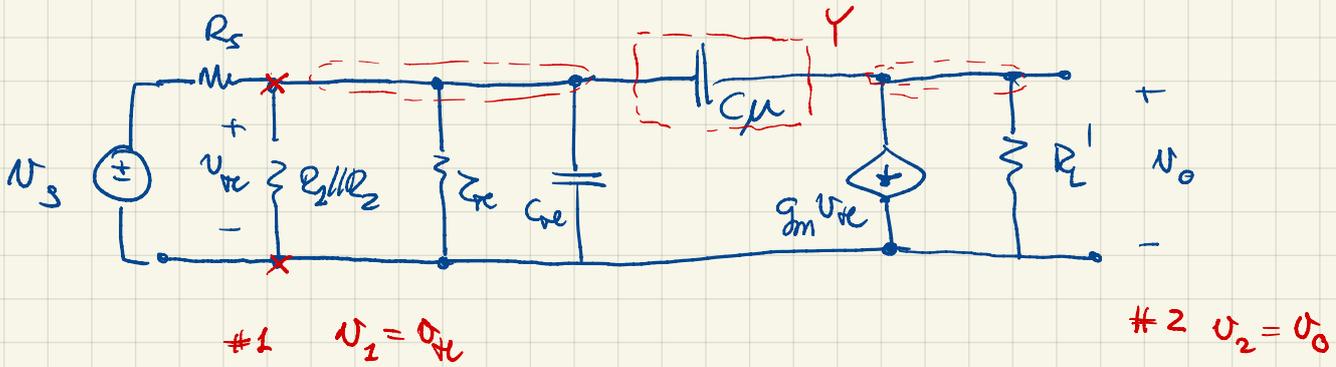


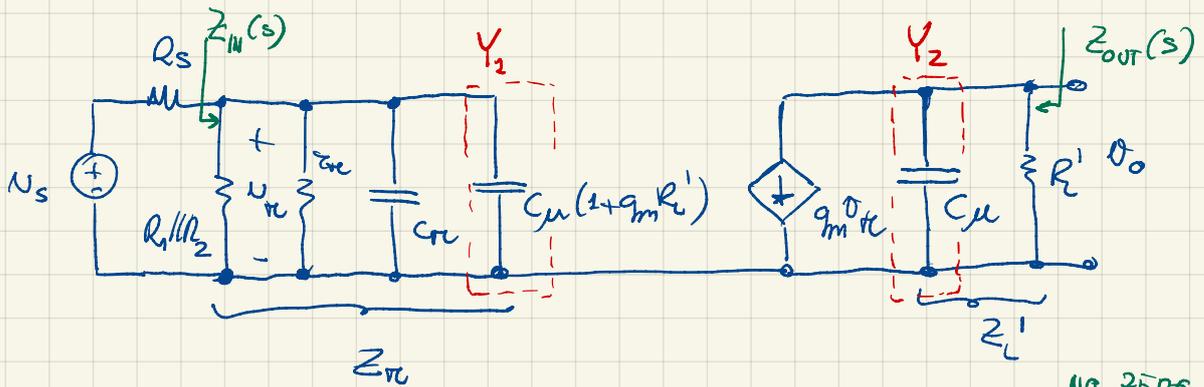LET'S REVISE THE CE AMPLIFIER USING MILLER'S THEOREM



$$G \approx \left. \frac{v_o}{v_{be}} \right|_{MS} = -g_m R_L' \quad |G| \gg 1$$

APPLYING THE THEOREM WE CAN SIMPLIFY THE CIRCUIT AS



$$A_{V, HF}(s) = -\frac{Z_{re}}{R_s + Z_{re}} \cdot g_m \cdot Z_L' = -\frac{R_{re}^0}{R_s} \cdot \frac{g_m R_L' \left(\begin{smallmatrix} \text{NO ZEROS} \\ \cdot \end{smallmatrix} \right)}{(1 + s R_{in}^0 C_{in}) \cdot (1 + s C_{\mu} R_L')}$$

$$Z_{re}(s) = \frac{R_1 // R_2 // z_{re}}{1 + s R_1 // R_2 // z_{re} C_{in}} \quad Z_L' = \frac{R_L'}{1 + s C_{\mu} R_L'}$$

$$C_{in} = C_{re} + C_{\mu} (1 + g_m R_L')$$

EXACTLY THE SAME AS IN THE ORIGINAL CIRCUIT

$$\frac{\frac{R_1 // R_2 // z_{re}}{1 + s R_1 // R_2 // z_{re} C_{in}}}{R_s + \frac{R_1 // R_2 // z_{re}}{1 + s R_1 // R_2 // z_{re} C_{in}}} = \frac{R_1 // R_2 // z_{re}}{R_s + R_1 // R_2 // z_{re} + s R_s (R_1 // R_2 // z_{re}) \cdot C_{in}}$$

$$R_{re}^0 = R_s // R_1 // R_2 // z_{re}$$

WE CAN ALSO APPLY OCTC METHOD

$$a_1^M = R_{in}^o C_N + C_{\mu} R_{\mu}^o = R_{in}^o [C_{\mu} + C_{\mu} (1 + g_m R_c')] + C_{\mu} R_c'$$

$$R_{\mu}^o = R_c' \quad R_{in}^o = R_{in}^o$$

$$a_1^M = R_{in}^o C_{\mu} + [R_{in}^o (1 + g_m R_c') + R_c'] C_{\mu} = a_1 \text{ OF THE ORIGINAL CIRCUIT (EXACT)}$$

$$\omega_H \approx \frac{1}{a_1} = \frac{1}{a_1^M}$$


IF WE CALCULATE $Z_{in}(s)$ NOW, WE EASILY FIND

$$Z_{in}(s) = Z_{re} \parallel R_1 \parallel R_2 \parallel \frac{1}{s C_{in}} \quad \text{WE LOST THE } \frac{1}{g_m} \text{ RESISTANCE IN SERIES WITH } C_{\mu}$$


FOR THE BEST, THE EXPRESSIONS ARE IDENTICAL.

N.B. MILLER'S THEOREM CANNOT BE USED TO SIMPLIFY THE CALCULATION OF $Z_{out}(s)$, BUT PROVIDES ACCURATE RESULTS FOR $\omega \ll \omega_T$ BOTH IN $A_{in}^{HF}(s)$ AND IN THE CALCULATION OF $Z_{in}(s)$

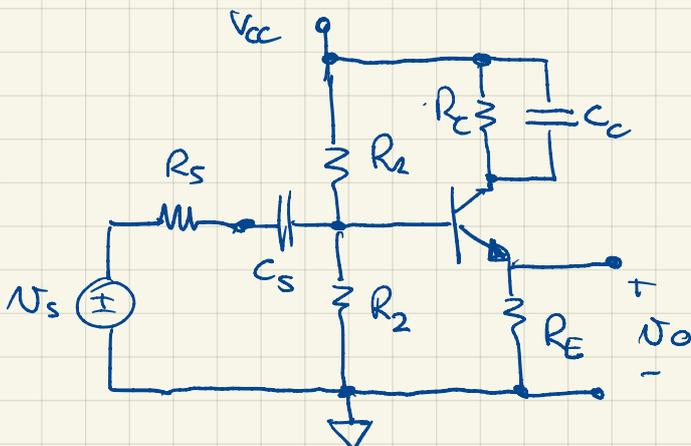HF ANALYSIS OF THE COMMON COLLECTOR AMPLIFIER



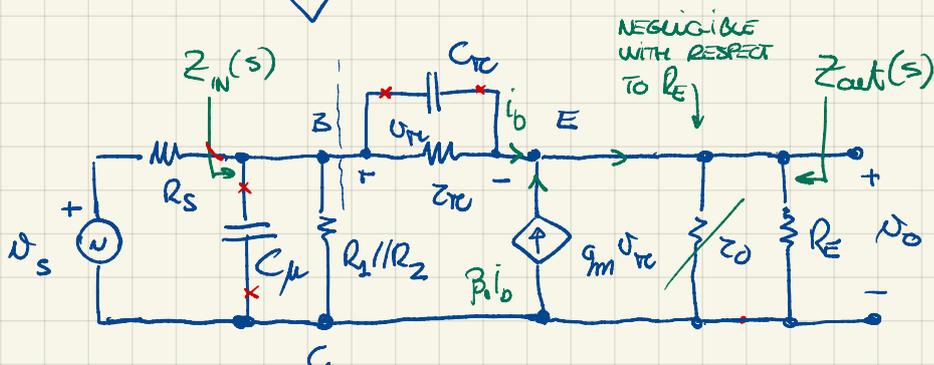IF ALL CIRCUIT PARAMETERS ARE KNOWN, WE CAN FIND THE BIAS POINT (V_{CE}, I_C) AND THE SMALL SIGNAL CIRCUIT PARAMETERS LIKE g_m, z_o, C_{μ} ...



NEGLECTABLE WITH RESPECT TO R_E

FROM WHICH WE CAN FIND:

$$A_{v}^{HF}(s)$$

$$Z_{in}(s)$$

$$Z_{out}(s)$$

1. $A_U^{HF}(s)$ USING OCTC METHOD

2 INDEPENDENT CAPACITORS $\Rightarrow m=N=2$

$$A_U^{HF}(s) = A_U^{MB} \cdot \frac{1 + s \frac{C_{re}}{g_m}}{1 + a_1 s + a_2 s^2}$$

CIRCUIT INSPECTION SHOWS $v_o \rightarrow 0$ AS $\omega \rightarrow \infty$ LIKE $\frac{1}{s} \Rightarrow$ THERE MUST BE A ZERO AT THE NUMERATOR $\Rightarrow m=1$.

TO FIND THE ZERO WE NEED TO FIND A CONDITION ON s SUCH THAT

$$v_o \equiv 0 \quad \forall v_s$$

THIS IS FOUND TO BE

$$\cancel{v_{re}} \cdot \left(s C_{re} + \frac{1}{r_e} \right) + g_m \cancel{v_{re}} = 0$$

$$s = - \left(g_m + \frac{1}{r_e} \right) \cdot \frac{1}{C_{re}} = - \frac{\beta_0 + 1}{r_e C_{re}} \approx - \frac{g_m}{C_{re}} = -\omega_T$$


SO, WE HAVE A NEGATIVE REAL PART ZERO AT $\omega_z \approx \omega_T$

$$A_U^{MB} = \frac{R_{in}^{INT} // R_1 // R_2}{R_s + R_{in}^{INT} // R_1 // R_2} \cdot \frac{(\beta_0 + 1) R_E}{r_e + (\beta_0 + 1) R_E} \approx 1$$

LET'S FIND THE DENOMINATOR COEFFICIENTS

$$a_1 = R_{T0}^o C_{re} + R_{\mu}^o C_{\mu} \quad \propto 10^{-10} \cdot 10^2 + 10^{-11} \cdot 10^4 \quad 10 \text{ ns}$$
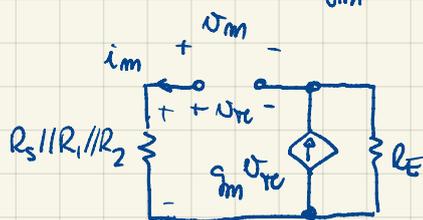
$$R_{re}^o = r_e // \frac{R_E + R_s // R_1 // R_2}{1 + g_m R_E} \quad \propto 10^2 \quad [\Omega]$$



$$v_{re} = R_s // R_1 // R_2 i_{in} + R_E (i_{in} - g_m v_{re})$$

$$\frac{v_{re}}{i_{in}} = \frac{R_E + R_s // R_1 // R_2}{1 + g_m R_E}$$

$$R_{\mu}^o = R_s // R_1 // R_2 // R_{in}^{INT} \quad \propto 10^1 \quad [\Omega]$$

IF WE CAN ASSUME A DOMINANT POLE EXISTS THEN

$$\omega_H \approx \frac{1}{\alpha_1} \gg 100 \text{ Mrad/s}$$

NORMALLY, THE CC STAGE HAS LARGER BANDWIDTH WITH RESPECT TO COMMON EMITTER STAGES.


$$\alpha_2 = C_{\pi} C_{\mu} R_{\pi}^0 R_{\mu}^{\pi} = C_{\pi} C_{\mu} R_{\pi}^0 \cdot R_1 // R_2 // R_s // R_E \propto 10^{-17}$$

$\begin{matrix} 10^{-10} & 10^{-11} & 10^2 & 10^2 \end{matrix}$

$$\frac{\alpha_1^2}{\alpha_2} = \frac{10^{-16}}{10^{-17}} = 10 \quad \text{THERE IS A DOMINANT POLE!}$$

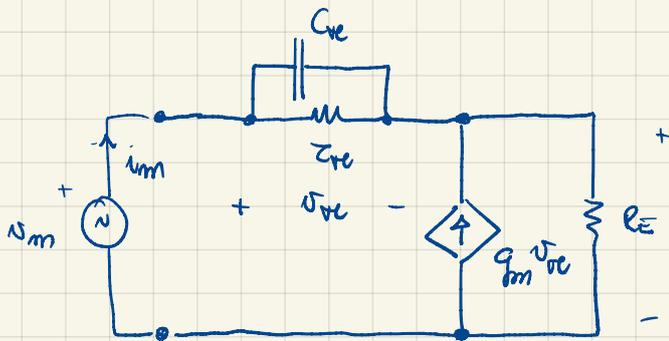2. LET'S DISCUSS $Z_{IN}(s)$ NOW

BY INSPECTION, WE SEE THAT $Z_{IN}(s) = R_B // \frac{1}{sC_{\mu}} // Z_{X}(s)$ WHERE $Z_{X}(s)$ CAN BE FOUND LIKE THIS:



$$v_{\pi} = Z_{\pi} i_{tm}$$

$$v_{tm} = v_{\pi} + R_E (i_{tm} + g_m Z_{\pi} i_{tm})$$


$$Z_X(s) = \frac{v_{tm}}{i_{tm}} = Z_{\pi} + R_E (1 + g_m Z_{\pi}) = R_E + Z_{\pi}(s) \cdot (1 + g_m R_E)$$

$$Z_X(s) = R_E + \frac{Z_{\pi} (1 + g_m R_E)}{1 + s C_{\pi} Z_{\pi}} = \frac{R_E + s C_{\pi} Z_{\pi} R_E + Z_{\pi} + \beta_0 R_E}{1 + s C_{\pi} Z_{\pi}} =$$

$$= R_{im}^{INT} \cdot \frac{1 + s C_{\pi} \frac{Z_{\pi} // R_E (\beta_0 + 1)}{\beta_0 + 1}}{1 + s Z_{\pi} C_{\pi}} = R_{im}^{INT} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \Rightarrow$$

$$\omega_z = \frac{\beta_0 + 1}{C_{\pi} (Z_{ce} \parallel R_E (\beta_0 + 1))} \approx \omega_T \quad \omega_p = \frac{1}{Z_{ce} C_{\mu}}$$

$$\omega_z \gg \omega_p$$

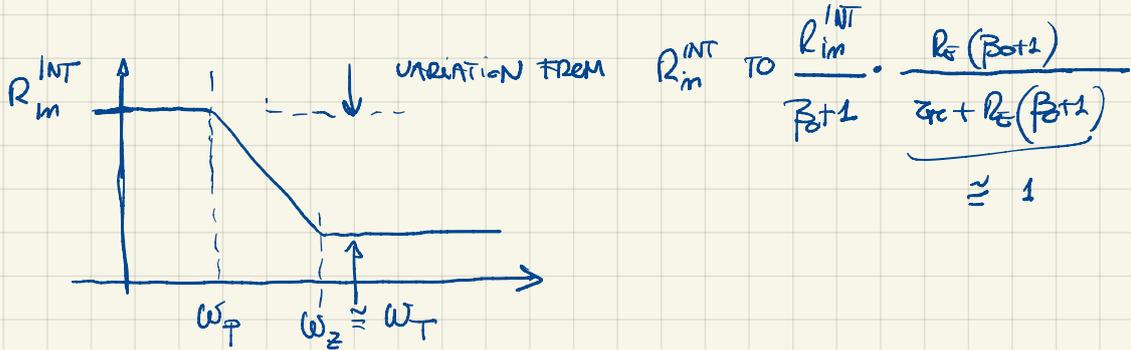

IN THE LAST FORM, $Z_{ce}(s)$ IS REVEALED TO BE OF THIS TYPE:

$$Z_{ce}(s) = R_m^{INT} \parallel \frac{1}{s C_{ce}'} \quad \text{WITH } C_{ce}' \ll C_{\mu}$$

INDEED @ $\omega \ll \omega_T$ WE CAN WRITE

$$Z_{ce}(s) \approx \frac{R_m^{INT}}{1 + s C_{ce}' Z_{ce}} = \frac{R_m^{INT}}{1 + s C_{ce}' R_m^{INT}} \quad \text{WITH } C_{ce}' = C_{ce} \cdot \frac{Z_{ce}}{R_m^{INT}} < C_{\mu}$$

TYPICALLY \downarrow


FINALLY, THE INPUT IMPEDANCE IS FOUND TO BE:

$$Z_{in}(s) = R_B \parallel R_m^{INT} \parallel \frac{1}{s(C_{ce}' + C_{\mu})} \approx R_B \parallel R_m^{INT} \parallel \frac{1}{s C_{\mu}}$$

CONCLUSION: THE CC INPUT IMPEDANCE IS RESISTIVE-CAPACITIVE.
THE INPUT CAPACITANCE IS $C_{in} \approx C_{\mu}$ (SMALL)

3. LET'S CONSIDER NOW THE OUTPUT IMPEDANCE

$$Z_{out}(s) = R_E \parallel Z_y(s)$$

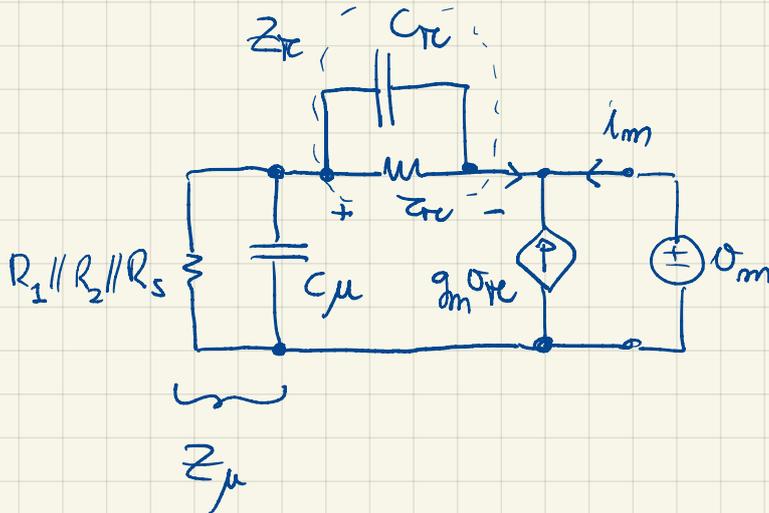

$$\begin{cases} i_{tm} = - \left(g_m v_{re} + i_{z_{re}} \right) = - v_{re} \left(g_m + \frac{1}{z_{re}} \right) \\ v_{re} = - \frac{z_{re}}{z_{re} + z_{\mu}} v_{tm} \end{cases}$$

$$\begin{aligned} \frac{i_{tm}}{v_{tm}} &= \frac{1 + g_m z_{re}}{z_{re} + z_{\mu}} = \frac{1 + g_m \frac{z_{re}}{1 + s C_{\mu} z_{re}}}{\frac{z_{re}}{1 + s C_{\mu} z_{re}} + \frac{R_1 \parallel R_2 \parallel R_s}{1 + s C_{\mu} R_1 \parallel R_2 \parallel R_s}} \\ &= \frac{1 + \beta_0 + s C_{re} z_{re}}{1 + s C_{re} z_{re}} \\ &= \frac{z_{re} + R_1 \parallel R_2 \parallel R_s + s(C_{re} + C_{\mu})(z_{re} \cdot R_1 \parallel R_2 \parallel R_s)}{(1 + s C_{re} z_{re})(1 + s C_{\mu} R_1 \parallel R_2 \parallel R_s)} \end{aligned}$$

$$Z_y(s) = \frac{z_{re} + R_1 \parallel R_2 \parallel R_s + s(C_{re} + C_{\mu})(z_{re} \cdot R_1 \parallel R_2 \parallel R_s)}{(1 + \beta_0 + s C_{re} z_{re})(1 + s C_{\mu} R_1 \parallel R_2 \parallel R_s)}$$

$$Z_y(s) = \underbrace{\frac{z_{re} + R_1 \parallel R_2 \parallel R_s}{1 + \beta_0}}_{R_{out}^{INT} \approx \frac{1}{g_m}} \cdot \frac{1 + s(C_{re} + C_{\mu}) \cdot z_{re} \parallel R_1 \parallel R_2 \parallel R_s}{(1 + s C_{\mu} R_1 \parallel R_2 \parallel R_s) \underbrace{\left(1 + s C_{re} \frac{z_{re}}{1 + \beta_0}\right)}_{\approx 1/\omega_T}}$$

$$Z_y(s) = R_{\text{OUT}}^{\text{INT}} \cdot \frac{1 + \frac{s}{\omega_z}}{\left(1 + \frac{s}{\omega_{P_1}}\right) \left(1 + \frac{s}{\omega_{P_2}}\right)}$$

IT IS POSSIBLE THAT $\omega_z < \omega_{P_1} < \omega_{P_2} \approx \omega_T$

INDUCTIVE REGION!

