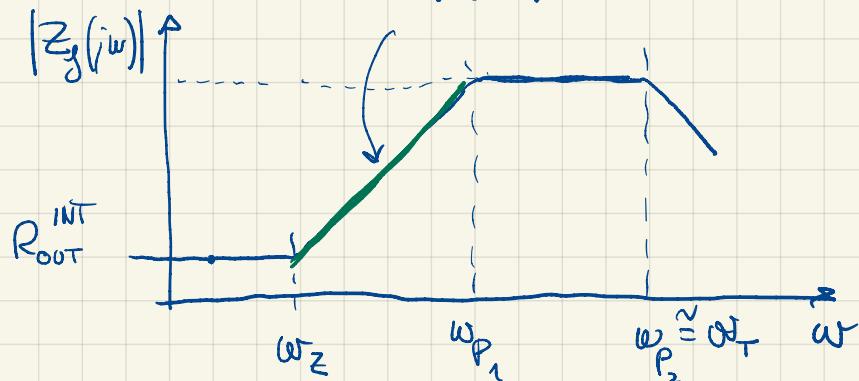


$$Z_g(s) = R_{out}^{int} \cdot \frac{1 + \frac{s}{\omega_z}}{\left(1 + \frac{s}{\omega_{p_1}}\right)\left(1 + \frac{s}{\omega_{p_2}}\right)}$$


IT IS POSSIBLE THAT $\omega_z < \omega_{p_1} < \omega_{p_2} \approx \omega_T$

INDUCTIVE REGION !




IN THE INDUCTIVE REGION


$$\omega < \omega_{p_1}$$

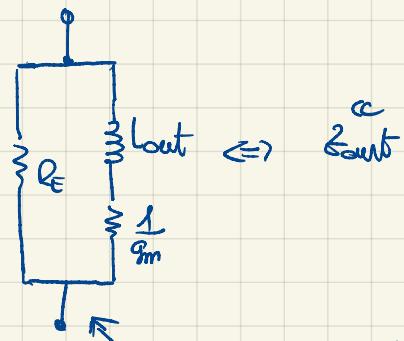

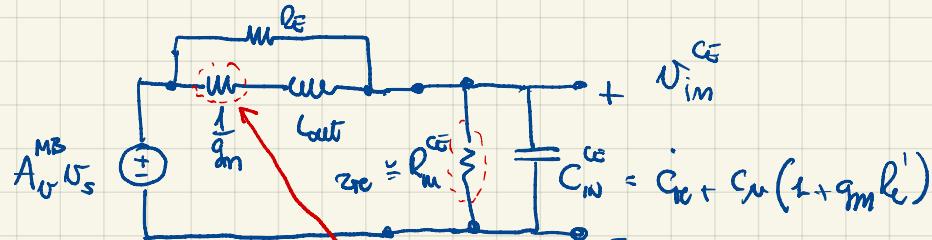THIS CAN BE A PROBLEM FOR CC. + C.E.
STAGES (BUFFERED COMMON Emitter).



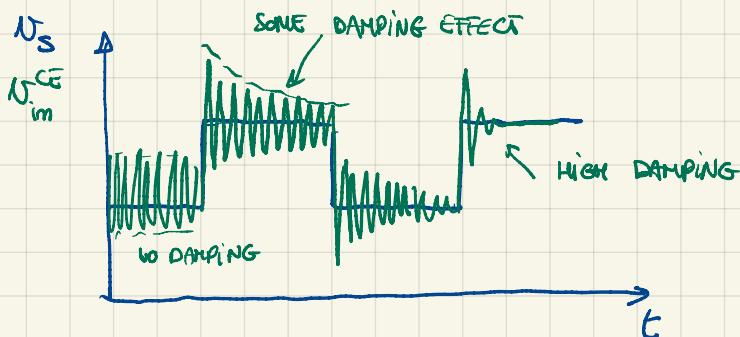EQUIVALENT THEVENIN
MODEL OF C.C. STAGE DAMPING $\xi \propto \frac{1}{g_m}, \frac{1}{r_o}$ IS RELATIVELY SMALL



$$\omega_R \approx \frac{1}{\sqrt{L_{out} C_{in}^{CE}}}$$


EQUIVALENT CIRCUIT
REPRESENTING THE
CC AMPLIFIER OUTPUT
IMPEDANCE FOR
 $\omega < \omega_{p_1}$

FREQUENCY RESPONSE OF MULTI-STAGE AMPLIFIER

1. BUFFERED CE STAGE ($CC + CF$)

2. CASCODE STAGE ($CE + CB$)

1.

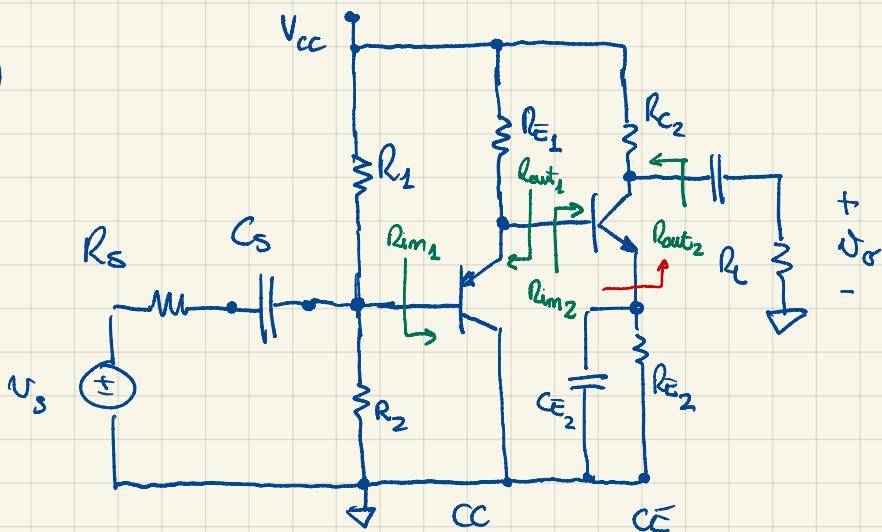

To do list

FIND THE BIAS POINTS

$$Q_1: (V_{CE1}, I_{C1})$$


$$Q_2: (V_{CE2}, I_{C2})$$

VERIFY THE BIAS POINTS FALL INTO THE FORWARD ACTIVE REGION

CALCULATE (OR FIND) THE SMALL CIRCUIT PARAMETERS
 $Z_R, g_m, C_{o2}, Z_o, \dots$

SOLVE THE SMALL SIGNAL CIRCUIT TO FIND:

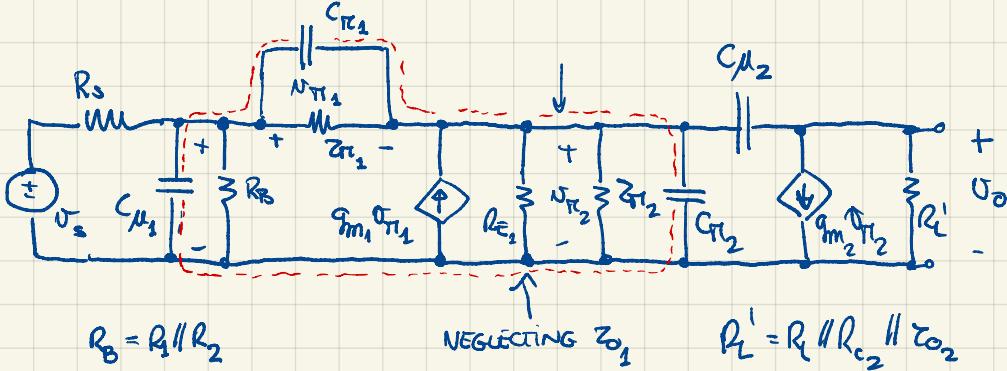NB
 $A_V, Z_{in}, Z_{out}, \omega_L, \omega_H$



$$R_{in1} = R_{in_{CC}}^{\text{INT}} = Z_{T1} + (\beta_0 + 1) R_{E1} // \underline{(R_{in2})} \quad \text{LOADING EFFECT!}$$

$$R_{out1} = R_{out_{CC}}^{\text{INT}} = R_{E1} // \frac{R_s // R_B + Z_{T1}}{\underbrace{\beta_0 + 1}_{\approx 1/g_m1}} \approx \frac{1}{g_m1}$$

$$R_{in2} = R_{in_{CE}}^{\text{INT}} = Z_{T2}$$

$$R_{out2} = R_{out_{CE}}^{\text{INT}} = R_{C2} // Z_{o2} \quad \text{LOADING EFFECT}$$

$$A_{v5}^{\text{MB}} = \frac{V_o}{V_s} = -g_{m2}^{-1} \cdot \frac{(\beta_0 + 1) R_{E2} // \underline{(R_{in2})}}{Z_{T1} + (\beta_0 + 1) R_{E1} // \underline{(R_{in2})}} \cdot \frac{R_B // R_{in2}}{R_s + R_B // R_{in2}}$$

$\omega_L \rightarrow$ USE OF SCLC METHOD UNDER DOMINANT POLE ASSUMPTION.

$$\omega_L \approx \frac{1}{C_s R_s^{\text{sc}}} + \frac{1}{C_{E_2} R_{E_2}^{\text{sc}}} + \frac{1}{C_L R_L^{\text{sc}}}$$

$$R_s^{\text{sc}} = R_s + R_B // R_{\text{out},1} \quad \text{LARGE } 10^5 \Omega$$

$$R_{E_2}^{\text{sc}} = R_{E_2} // \frac{R_{E_2} + R_{\text{out},2}}{\beta_{E_2} + 1} \approx R_{E_2} // \frac{1}{q_{m_2}} \quad \text{SMALL} \quad \leftarrow \text{DOMINANT } 10^1 \Omega$$

$$R_L^{\text{sc}} = R_L + R_{\text{out},2} \quad \text{MEDIUM } 10^3 \Omega$$

• ω_H USING OCTC METHOD AND DOMINANT PAE ASSUMPTION

$$\omega_H \approx \frac{1}{C_{T_1} R_{T_1}^0 + C_{U_1} R_{U_1}^0 + C_{T_2} R_{T_2}^0 + C_{U_2} R_{U_2}^0} = \frac{1}{\frac{1}{\omega_{H_1}} + \frac{1}{\omega_{H_2}}}$$


a_{11} WITH LOADING EFFECTS a_{12} WITH LOADING EFFECT

$$\omega_H < \min \{ \omega_{H_1}, \omega_{H_2} \} \quad \text{BUT} \quad \omega_H > \omega_{H_{CE}} \quad \text{UNLOADED !}$$

LET'S SEE WHY !

$$R_{T_1}^0 = r_{T_1} // \frac{R_s // R_B + R_{E_1} // (R_{\text{out},2})}{1 + q_{m_1} (R_{E_1} // (R_{\text{out},2}))}$$

LOADING EFFECT

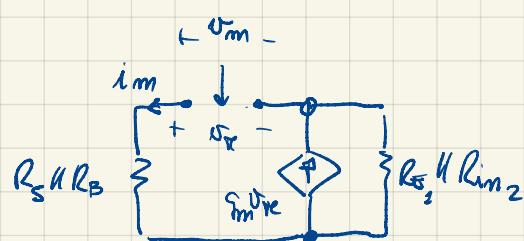

$$v_m = (R_s // R_B) i_m + R_{E_1} // R_{\text{out},2} (i_m - q_m v_m)$$

$$R_{U_1}^0 = R_s // R_B // R_{\text{out},1} = R_s // R_B // [r_{U_1} + (\beta_{U_1} + 1) R_{E_1} // R_{\text{out},2}]$$

LOADING EFFECT

THE LOADING EFFECT OF THE C.E. STAGE OVER THE C.C. STAGE IS NOT STRONG BECAUSE TYPICALLY $\beta_U > \beta_E$!!

$$a_{11} \approx a_1^{\text{CC}} \quad \text{WITH NO LOAD}$$

LOADING EFFECT MAKES $R_{T_2}^0$ SMALL

$$R_{T_2}^0 = r_{T_2} // R_{\text{out},1} \approx r_{T_2} // \frac{1}{q_{m_1}} \quad \text{SMALL !}$$

$$R_{U_2}^0 = R_{T_2}^0 + R_L \cdot (1 + q_{m_2} R_{T_2}^0) = R_L + \frac{R_{T_2}^0}{R_{T_2}^0} (1 + q_{m_2} R_L)$$

THANKS TO THE LOADING EFFECTS $\alpha_{12} \ll \alpha_1^{CE}$ AS THE MILLER MULTIPLIER IS STRONGLY REDUCED.

AS A RESULT $\omega_{H_2} \gg \omega_H^{CE} \Rightarrow \omega_H > \omega_H^{CE}$!!

THE BUFFER STAGE ALLOWS TO MAKE THIS AMPLIFIER BANDWIDTH **LARGER**.

N.B. DO NOT FORGET THE POTENTIAL RESONANCE BETWEEN Z_{out}^{CC} AND Z_{in}^{CE}

ADDITIONAL DETAILS: $M = 3$ EVEN IF $N = 4$ AT HIGH FREQUENCY, BECAUSE WE HAVE A LOOP INVOLVING $C_{T1}, C_{\mu 1}, C_{T2}$.

- BESIDES, N_0 GOES TO ZERO LIKE $\frac{1}{s}$ AS $s \rightarrow \infty$ WHICH MEANS $m = 2$.
NOTICE THE CAPACITIVE VOLTAGE DIVIDER MADE UP BY C_{T1} AND C_{T2} !
- THE TWO ZEROS CAN BE FOUND AS IN THE SINGLE STAGE CE AND CC AMPLIFIER.