

THANKS TO THE LOADING EFFECTS $a_{12} \ll a_1^{CE}$ AS THE MILLER MULTIPLIER IS STRONGLY REDUCED.

AS A RESULT $\omega_{H2} \gg \omega_H^{CE} \Rightarrow \omega_H > \omega_H^{CE} !!$

THE BUFFER STAGE ALLOWS TO MAKE THIS AMPLIFIER BANDWIDTH **LARGER**.


N.B. **DO NOT FORGET THE POTENTIAL RESONANCE BETWEEN Z_{out}^{CC} AND Z_{in}^{CE}**

ADDITIONAL DETAILS: $m = 3$ EVEN IF $N = 4$ AT HIGH FREQUENCY, BECAUSE WE HAVE **A LOOP INVOLVING $C_{\pi 1}, C_{\mu 1}, C_{\pi 2}$** .


- BESIDES, N_0 GOES TO ZERO LIKE $\frac{1}{s}$ AS $s \rightarrow \infty$ WHICH MEANS $m = 2$.
- NOTICE THE CAPACITIVE VOLTAGE DIVIDER MADE UP BY $C_{\pi 1}$ AND $C_{\pi 2}$** !

- THE TWO ZEROS CAN BE FOUND AS IN THE SINGLE STAGE CE AND CC AMPLIFIER.

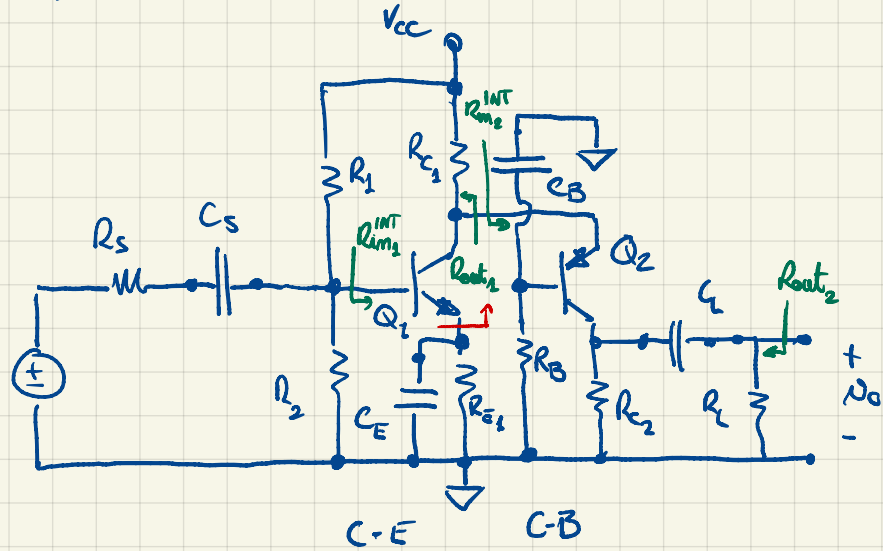◇ FREQUENCY RESPONSE OF THE CASCODE (CE-CB) AMPLIFIER



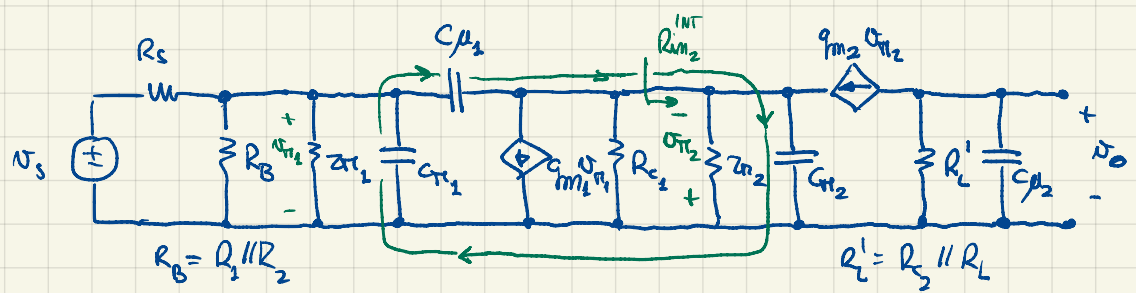- $Q_1 (I_{C1}, V_{CE1}), Q_2 (I_{C2}, V_{CE2})$
- CHECK F.A.R. BIAS
- DETERMINE SMALL SIGNAL PARAMETERS $g_{m1,2}, z_{rc,1,2}, C_{\mu,1,2}, C_{\pi,1,2} \dots$
- DRAW THE SMALL SIGNAL EQUIVALENT CIRCUIT



$N = 4$ BUT WE HAVE A LOOP $\Rightarrow m = 3$

$m = 1$ AS $N_0 \rightarrow 0$ AS FAST AS $\frac{1}{s}$ DUE TO $C_{\mu 2}$ AND $C_{\pi 1}$ (INDEPENDENTLY).

$$R_{in1}^{INT} = Z_{T1}$$

$$R_{out1} = R_{C1} \parallel Z_{O1} \approx R_{C1}$$

$$R_{in2}^{INT} = Z_{T2} \parallel \frac{1}{g_{m2}} = \frac{Z_{T2}}{\beta_2 + 1} \approx \frac{1}{g_{m2}}$$

$$R_{out2} \approx R_L'$$

$$A_v^{MB} = -g_{m2} R_L' \cdot \underbrace{g_{m1} (R_{C1} \parallel R_{in2}^{INT})}_{\text{CE GAIN WITH LOADING EFFECT}} \cdot \underbrace{\frac{R_{in1}^{INT} \parallel R_B}{R_{in1}^{INT} \parallel R_B + R_S}}_{\alpha_i} \approx -\alpha_i \cdot g_{m1} R_L'$$

THE CASCODE STAGE HAS ALMOST THE SAME GAIN OF A CE STAGE WITH THE SAME LOAD.

2. SCTC METHOD AND DOMINANT POLE ASSUMPTION

$$\omega_L \approx \frac{1}{R_S^x C_S} + \frac{1}{R_E^x C_E} + \frac{1}{R_B^x C_B} + \frac{1}{R_L^{sc} C_L}$$

$$R_S^x = R_S + R_B \parallel R_{in1}^{INT}$$

$$R_E^x = R_{E1} \parallel \frac{Z_{T1} + R_S \parallel R_B}{\beta_2 + 1} \approx R_{E1} \parallel \frac{1}{g_{m1}} \approx \frac{1}{g_{m1}}$$

← MOST IMPORTANT FOR THE DESIGN OF ω_L

$$R_B^x = R_B \parallel [Z_{T2} + (\beta_2 + 1) R_{out2}]$$

$$R_L^{sc} = R_{C2} + R_L$$

3. OCTC METHOD AND DOMINANT POLE ASSUMPTION

$$\omega_H \approx \frac{1}{\underbrace{R_{\pi 1}^0 C_{\pi 1} + R_{\mu 1}^0 C_{\mu 1}}_{\frac{1}{a_{11}}} + \underbrace{R_{\pi 2}^0 C_{\pi 2} + R_{\mu 2}^0 C_{\mu 2}}_{\frac{1}{a_{12}}}} = \frac{1}{\frac{1}{\omega_{H1}} + \frac{1}{\omega_{H2}}}$$

THE LOADING EFFECT STRONGLY REDUCES THE MILLER'S MULTIPLIER

$$R_{\pi 1}^0 = Z_{T1} \parallel R_B \parallel R_S$$


$$R_{\mu 1}^0 = R_{\pi 1}^0 + R_S \parallel R_{in2}^{INT} (1 + g_{m1} R_{\pi 1}^0) = R_{C1} \parallel R_{in2}^{INT} + R_{\pi 1}^0 (1 + g_{m1} R_{C1} \parallel R_{in2}^{INT})$$

$$R_{\pi 2}^0 = R_{out1} \parallel R_{in2}^{INT} \approx R_{in2}^{INT}$$


$$R_{\mu 2}^0 = R_L'$$

CB IS NOT AFFECTED (ALMOST) BY THIS CE STAGE

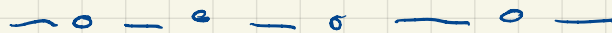
CONCLUSION: BY REDUCING THE MILLER EFFECT ON THE CE STAGE THE CASCODE AMPLIFIER HAS A **MUCH WIDER BANDWIDTH** THAN A SIMPLE CE OF EQUAL GAIN.



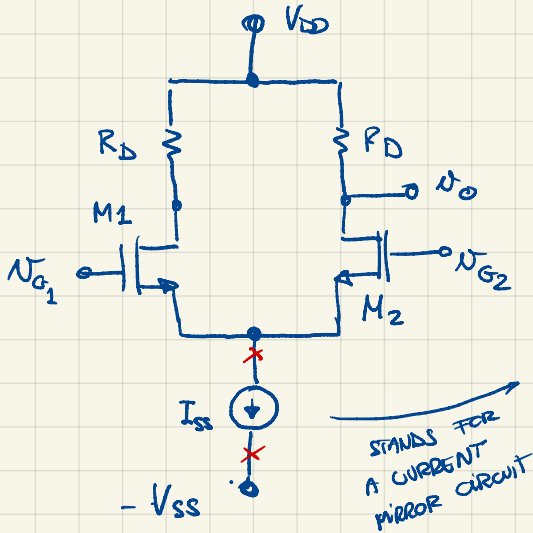◇ **FREQUENCY RESPONSE OF A MOSTET BASED DIFFERENTIAL STAGE**



STANDS FOR A CURRENT MIRROR CIRCUIT

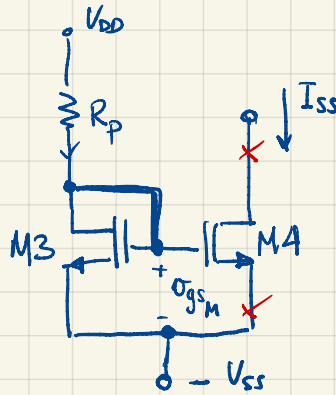

THE CURRENT MIRROR DEVICES ARE MUCH LARGER (TYPICALLY) THAN THE AMPLIFIER'S

THE PURPOSE OF THIS CURRENT MIRROR IS TO BIAS THE DIFFERENTIAL STAGE SO THAT WHEN $V_{G1} = V_{G2} = 0$ THEN

$$I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

Hyp: THE CIRCUIT IS PERFECTLY SYMMETRICAL


SMALL SIGNAL ANALYSIS IS **TWOFOLD**

- **DM ANALYSIS** $V_{g1} = \frac{V_{odm}}{2}$ $V_{g2} = -\frac{V_{odm}}{2}$
- **CM ANALYSIS** $V_{g1} = V_{g2} = V_{cm}$


WHERE

$$\begin{cases} V_{odm} = V_{g1} - V_{g2} \\ V_{cm} = \frac{V_{g1} + V_{g2}}{2} \end{cases} \Leftrightarrow \begin{cases} V_{g1} = V_{cm} + \frac{V_{odm}}{2} \\ V_{g2} = V_{cm} - \frac{V_{odm}}{2} \end{cases}$$

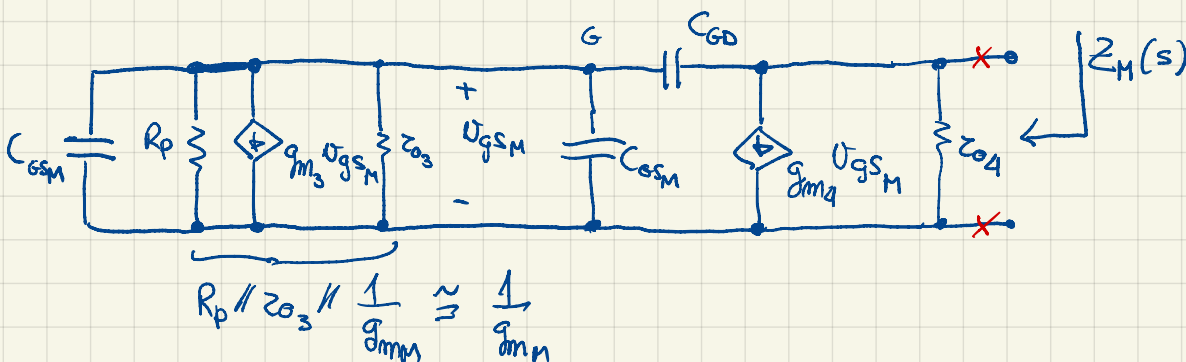LET'S ANALYZE THE CURRENT MIRROR FIRST, ASSUMING $g_{m3} = g_{m4} = g_{mm}$



$$Z_M(s) = z_{o4} \parallel Z_y(s)$$

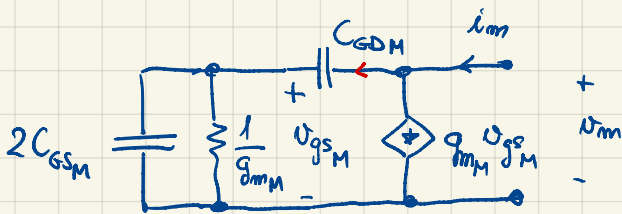

$$C_{GDM} \gg C_{GD}$$

$$C_{GSM} \gg C_{GS}$$


$$v_{gsM} = v_{nm} \cdot \frac{\frac{1}{g_{mM} + 2sC_{GSM}}}{\frac{1}{g_{mM} + 2sC_{GSM}} + \frac{1}{sC_{GDM}}} = v_{nm} \cdot \frac{sC_{GDM}}{g_{mM} + 2sC_{GSM} + sC_{GDM}}$$

$$i_{nm} = g_{mM} \cdot v_{gsM} + (v_{nm} - v_{gsM}) sC_{GDM} =$$


$$= v_{nm} \cdot \left[\frac{(g_{mM} - sC_{GDM}) sC_{GDM}}{g_{mM} + s(C_{GDM} + 2C_{GSM})} + sC_{GDM} \right] =$$

$$= v_{nm} \cdot \frac{sC_{GDM} (g_{mM} - \cancel{sC_{GDM}} + g_{mM} + \cancel{sC_{GDM}} + 2sC_{GSM})}{g_{mM} + s(C_{GDM} + 2C_{GSM})}$$
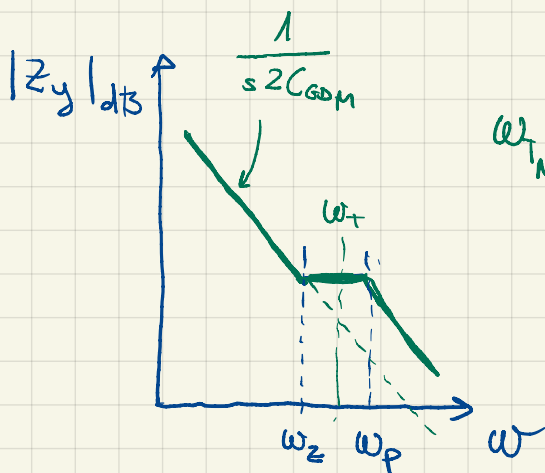
$$\frac{v_{nm}}{i_{nm}} \triangleq Z_y(s) = \frac{1 + s \frac{C_{GDM} + 2C_{GSM}}{g_{mM}}}{2sC_{GDM} \left(1 + \frac{sC_{GSM}}{g_{mM}} \right)} = \frac{1 + \frac{s}{\omega_z}}{s 2C_{GDM} \left(1 + \frac{s}{\omega_p} \right)}$$


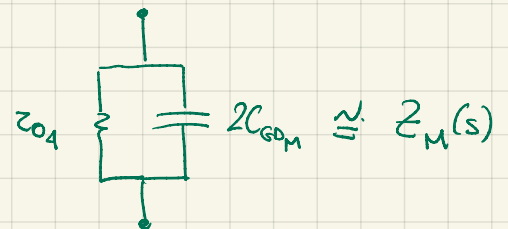
$$\omega_{TM} = \frac{g_{mM}}{C_{GSM} + C_{GDM}}$$



$$Z_M(s) \approx z_{o4} \parallel \frac{1}{s 2C_{GDM}} = \frac{z_{o4}}{1 + s 2z_{o4} C_{GDM}}$$

BECAUSE $\omega_z < \omega_T < \omega_p$, ω_z IS CLOSE TO ω_T AND SO IS ω_p , WE CAN NEGLECT THE ZERO-POLE COUPLE AND APPROXIMATE Z_M AS IN HERE