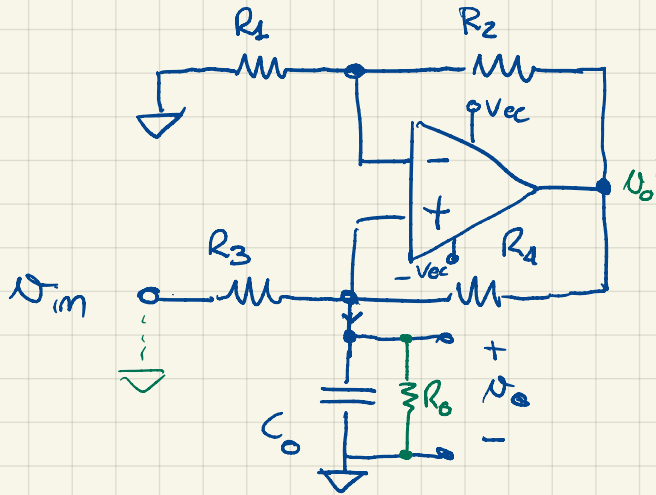


8/11/2022

FEEDBACK IN ELECTRONIC AMPLIFIERS

IN ELECTRONICS WE USE BOTH NEGATIVE AND POSITIVE FEEDBACK



EXAMPLE: NON INVERTING INTEGRATOR

Hyp: OPAMP IS IDEAL

$$R_1 = R_3$$

$$R_2 = R_4$$

AS A RESULT (PROOF AS EXERCISE)

$$v_o = v_{im} \cdot \frac{1}{sC_0R_1}$$


PROBLEM:

@ BC $v_- = \frac{R_1}{R_1 + R_2} v_o' = v_+ \Rightarrow$ POTENTIAL STABILITY ISSUE

SOLUTION:

BY APPLYING R_0 (LARGE) WE MAKE NEGATIVE FEEDBACK STRONGER THAN THE POSITIVE ONE

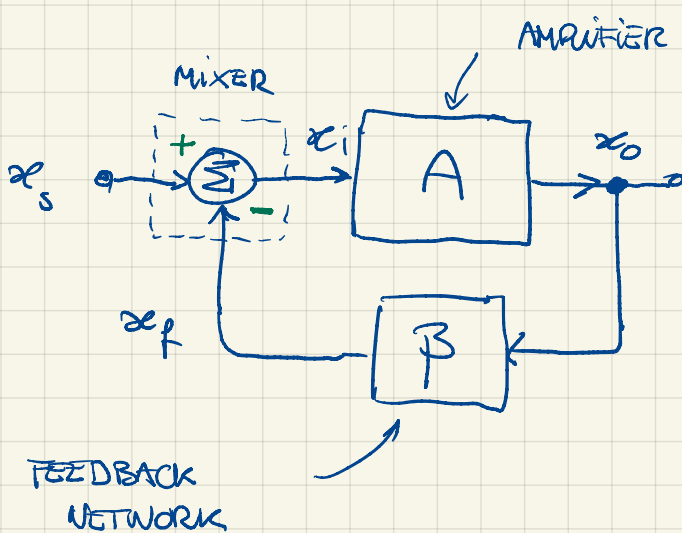THIS MODEL OF A FEEDBACK AMPLIFIER CAN BE THE USUAL ONE, BASED ON BLOCK DIAGRAMS



HIDDEN ASSUMPTIONS

BLOCKS ARE UNICATERAL
ELECTRONIC CIRCUITS ARE NOT UNICATERAL (IN GENERAL)

THERE ARE NO LOADING EFFECTS (A DOES NOT CHANGE WHEN WE CONNECT IT TO B)

EXAMPLES

1. A is a CE STAGE
2. A is a CC STAGE

ALL ELECTRONICS CIRCUITS SHOW SOME DEGREE OF LOADING EFFECT \Rightarrow A DOES CHANGE WHEN CONNECTED TO B


1. CE SMALL SIGNAL MODEL



$$A = \frac{v_o}{v_i} = -g_m R_L$$

IS THIS AMPLIFIER UNILATERAL? **YES**: NO EFFECT OF v_o OVER v_i

2. CC SMALL SIGNAL MODEL

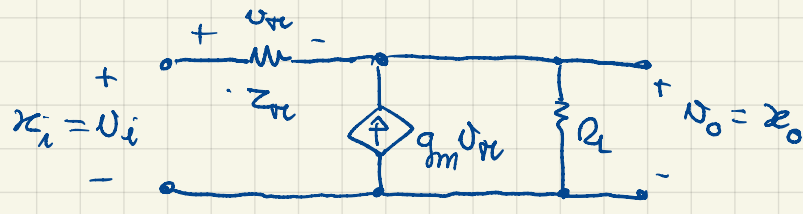


$$A = \frac{v_o}{v_i} \approx 1$$

IS THIS AMPLIFIER UNILATERAL? **NO**: v_o HAS EFFECTS OVER THE INPUT PART

WHAT ABOUT THE FEEDBACK NETWORK?

AS AN EXAMPLE: RESISTIVE T-NETWORK

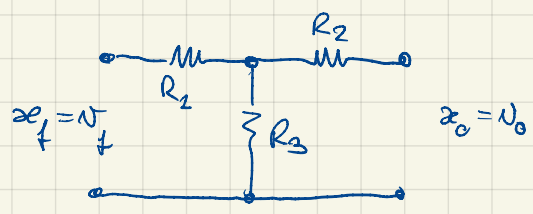

β -NETWORKS ARE PASSIVE (MOST OFTEN)



THEY ARE ALWAYS BILATERAL.

IN ADDITION, LOADING EFFECTS ARE ALWAYS FOUND.

ASSUMING THAT A HAS BEEN CALCULATED TAKING INTO ACCOUNT THE LOADING EFFECT **AND** THAT THE BILATERALITY EFFECTS ARE NEGLIGIBLE, WE CAN APPLY THE USUAL BLOCK DIAGRAM ALGEBRA AND FIND

$$A_F = \frac{x_o}{x_i} = \frac{A}{1 + A\beta}$$

WHERE $A\beta = T$ IS THE **LOOP GAIN**

THE LOOP GAIN DEFINES THE STABILITY PROPERTIES OF THE CLOSED LOOP AMPLIFIER

THE QUANTITY $|1 + T|$ IS CALLED THE **AMOUNT OF FEEDBACK**


TO TELL POSITIVE FEEDBACK FROM NEGATIVE FEEDBACK WE CHECK THE RELATION BETWEEN A AND A_F

IF $|A_F| > |A|$ WE HAVE POSITIVE FEEDBACK $\Leftrightarrow |1+T| < 1$

IF $|A_F| < |A|$ WE HAVE NEGATIVE FEEDBACK $\Leftrightarrow |1+T| > 1$

STABILITY IS ASSESSED BY THE NYQUIST CRITERION (REVISE)

EXAMPLE

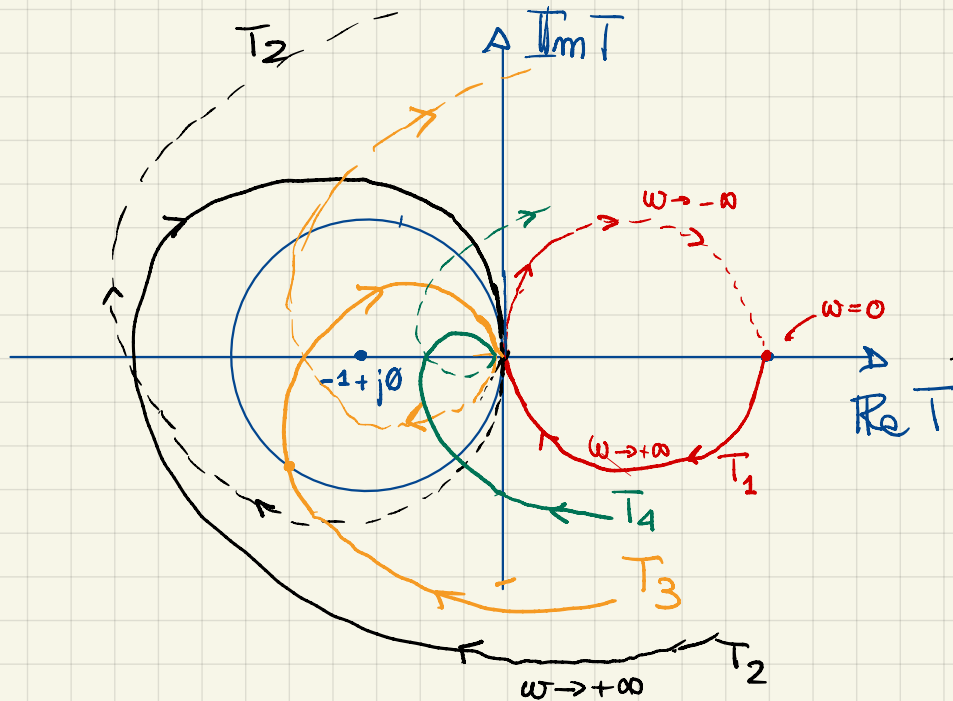

NOTE: WE CAN SAFELY ASSUME BOTH A AND β DO NOT HAVE RHP POLES SO WE CAN TEST THE NUMBER OF CLOSED LOOP RHP POLES COUNTING THE NUMBER OF CLOCKWISE ENCIRCLEMENTS OF $-1 + j0$

T_1 IS A NEGATIVE FEEDBACK **STABLE** AMPLIFIER. (NO ENCIRCLEMENTS)

T_2 IS A $u \ u \ u \ u$ **UNSTABLE** $u \ u$ (2 ENCIRCLEMENTS)

T_3 IS A POSITIVE FEEDBACK **UNSTABLE** $u \ u$ (2 ENCIRCLEMENTS)

T_4 IS A $u \ u \ u \ u$ **STABLE** $u \ u$ (NO ENCIRCLEMENT)

ALL THAT SAID, WE ARE VERY MUCH INTERESTED IN USING NEGATIVE FEEDBACK, THANKS TO ITS PROPERTIES.

PROPERTIES OF NEGATIVE FEEDBACK

1. DE-SENSITIVENESS

$$\frac{dA_F}{dA} = \frac{1 + \beta A - \beta A}{(1 + \beta A)^2} = \frac{1}{(1 + T)^2} = \frac{1}{A} \cdot A_F \cdot \frac{1}{1 + T}$$

$$\frac{dA_F}{A_F} = \frac{dA}{A} \cdot \frac{1}{1 + T}$$

↑ ↑
THE REASON IS THAT

THE RELATIVE VARIATION OF A_F IS SMALLER
THE RELATIVE VARIATION OF A WHEN


$|1 + T| > 1 \Rightarrow$ NEGATIVE FEEDBACK MAKES
THE AMPLIFIER LESS SENSITIVE
TO ANY SORT OF PARAMETRIC
VARIATIONS

$$A_F = \frac{A}{1 + \beta A} \approx \frac{1}{\beta}$$

$|1 + T| \gg 1$

DOES NOT DEPEND ON THE AMPLIFIER
PARAMETERS BUT ONLY ON THE FEEDBACK
NETWORK WHICH IS EASIER TO MAKE
INSENSITIVE

2. LINEARIZATION

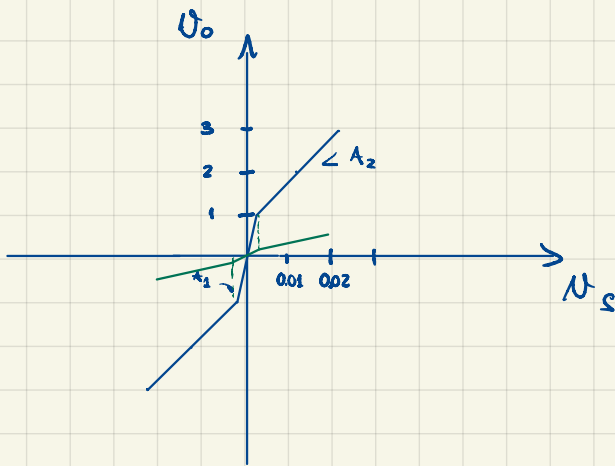

THE NON LINEARITY OF
THE TRANSFER-CHARACTERISTIC
IS REDUCED IF WE
APPLY NEGATIVE FEEDBACK

$$A_1 = 1000 \quad \text{FOR } |U_s| < 0.001 \text{ [p.u.]}$$

$$A_2 = 100 \quad \text{ELSEWHERE}$$

APPLYING NEGATIVE FEEDBACK WITH $\beta = 0.1$ (EXAMPLE) THEN

$$A_{F1} = \frac{1000}{1 + 100} \approx 9.9$$

$$A_{F1} \approx A_{F2} \quad \text{EVEN IF } A_2 \ll A_1 \quad !!$$

$$A_{F2} = \frac{100}{1 + 10} \approx 9.1$$

WE HAVE LINEARIZED THE TRANS-
CHARACTERISTIC.

3. BANDWIDTH WIDENING


$$A = \frac{A_{MB}}{1 + \frac{s}{\omega_p}} \longrightarrow A_F = \frac{\frac{A_{MB}}{1 + \frac{s}{\omega_p}}}{1 + \frac{\beta A_{MB}}{1 + \frac{s}{\omega_p}}}$$

WE CAN RE-ARRANGE A_F

$$A_F = \frac{A_{MB}}{1 + \beta A_{MB} + \frac{s}{\omega_p}} = \underbrace{\frac{A_{MB}}{1 + \beta A_{MB}}}_{A_{FMB}} \cdot \frac{1}{1 + \frac{s}{\omega_p(1 + \beta A_{MB})}}$$

IF FEEDBACK IS NEGATIVE, THE MID-BAND GAIN DROPS BY A FACTOR $1 + T_{MB}$, BUT THE POLE MOVES FURTHER TO THE RIGHT BY THE SAME FACTOR

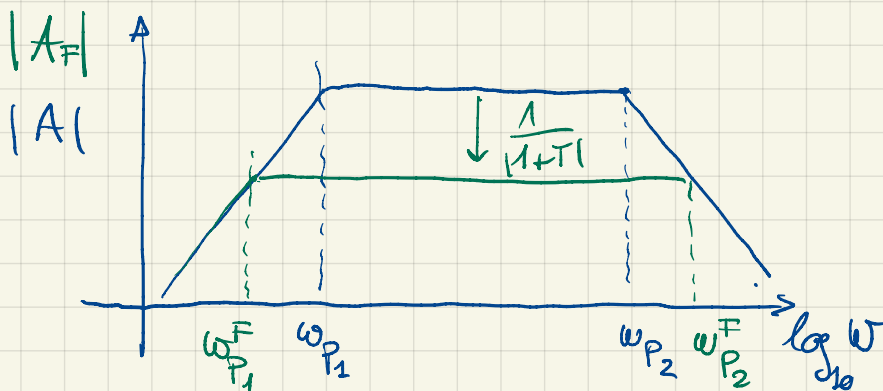EXERCISE: VERIFY THE SAME HAPPENS TO A LOW FREQUENCY POLE



$$\omega_{P2}^F = \omega_{P2} |1 + T|$$

$$\omega_{P1}^F = \frac{\omega_{P1}}{|1 + T|}$$

THE FEEDBACK AMPLIFIER BANDWIDTH IS WIDENED WITH RESPECT TO THE ORIGINAL ONE!