
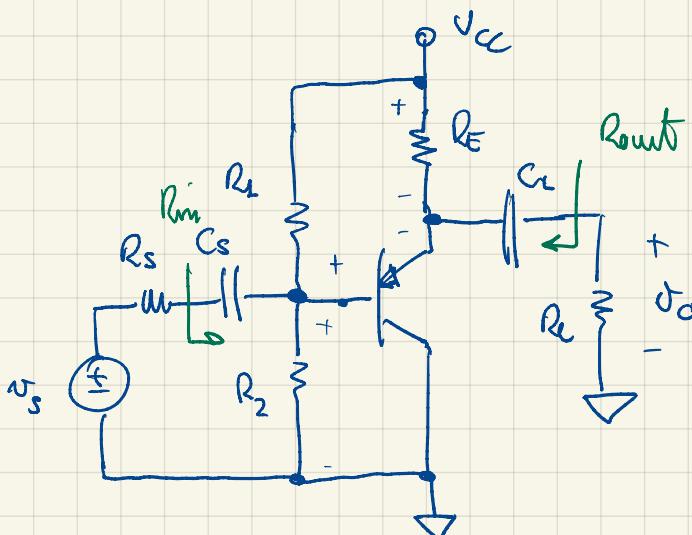


## EXAMPLE: CC AMPLIFIER

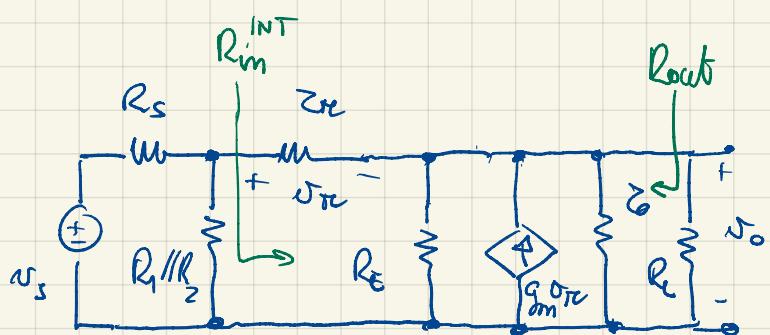

SMALL SIGNAL EQUIVALENT CIRCUIT



THE SMALL SIGNAL EQUIVALENT CIRCUIT CAN BE "EASILY" SOLVED:

$$A_{\text{D}} \triangleq \frac{u_o}{u_s} = \frac{(B_0 + 1) R_L \parallel R_E \parallel z_o}{z_o + (B_0 + 1) R_L \parallel R_s \parallel z_o} \cdot \frac{R_1 \parallel R_2 \parallel R_m^{\text{INT}}}{R_s + R_1 \parallel R_2 \parallel R_m^{\text{INT}}} = \dots$$

$$\dots = \frac{(B_0 + 1) R_L \parallel R_E \parallel z_o}{R_s \parallel R_1 \parallel R_2 + R_m^{\text{INT}}} \cdot \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2}$$


$$R_m^{\text{INT}} = R_1 \parallel R_2 \parallel R_m^{\text{INT}}$$

PROVE THIS AS AN EXERCISE !!

$$R_{\text{out}} = z_o \parallel R_E \parallel \frac{z_o + R_1 \parallel R_2 \parallel R_s}{B_0 + 1}$$

WE CAN DERIVE THE SAME RESULT APPLYING FEED BACK THEORY

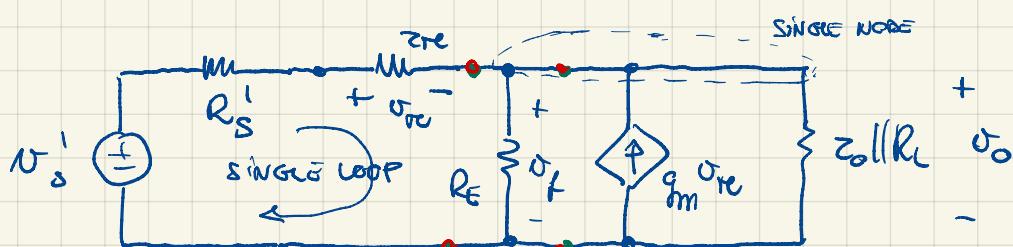
FIRST, WE CAN SIMPLIFY THE INPUT SIDE USING THEVENIN'S THEOREM:




$$u_s' = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} u_s$$

$$R_s^1 = R_1 \parallel R_2 \parallel R_s$$

B-NETWORK

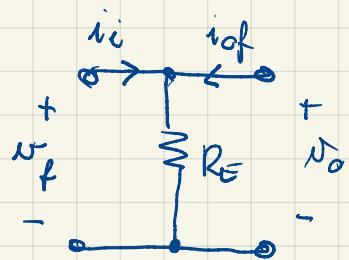

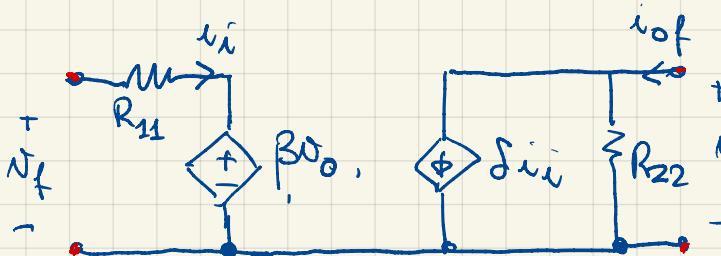TWO TWO PORT EQUIVALENT MODEL OF THE  $\beta$ -NETWORK IS: THAT OF A VOLTAGE AMPLIFIER (SERIES-SHUNT) :




$$R_{21} \stackrel{\Delta}{=} \frac{U_f}{i_i} \Big|_{U_o=0} = \emptyset$$

$$\beta = \frac{U_f}{U_o} \Big|_{i_i=0} = 1$$

$$R_{22} = \frac{U_o}{i_o} \Big|_{i_i=0} = R_E$$


$$\delta = \frac{i_o}{i_i} \Big|_{U_o=0} = -1$$

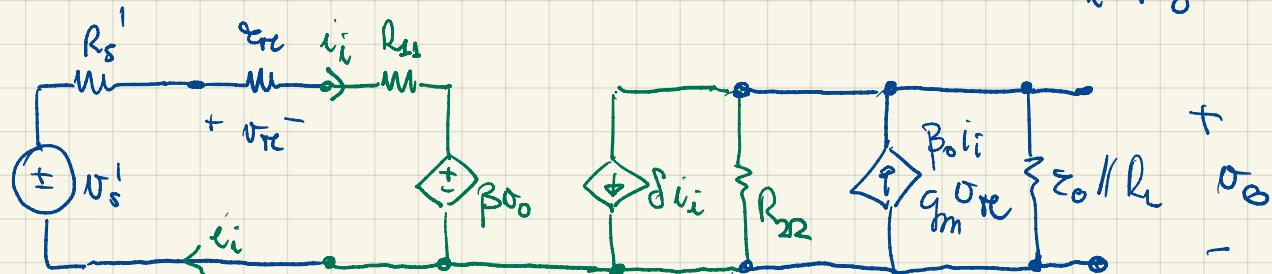LET'S REPLACE  $R_E$  WITH THE COMPLEMENT TWO-PORT MODEL OF THE PHYSICAL  $\beta$ -NETWORK.



$$U_R = z_r \cdot i_i \Rightarrow q_m U_R = q_m z_r \cdot i_i = \beta_0 i_i \Rightarrow (\beta_0 - \delta) i_i = (\beta_0 + 1) i_i$$

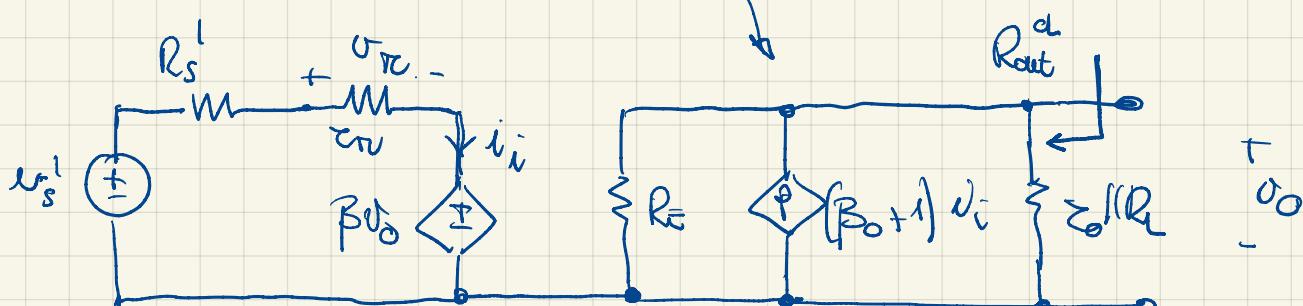WE CAN MERGE  
THE TWO CONTROLLED  
CURRENT SOURCES



FROM THIS CIRCUIT WE CAN FIND OPEN LOOP PARAMETERS BY SETTING  $\beta = 0$

$$A_{V^d} = \frac{U_o}{U_s^1} = \frac{(\beta_0 + 1) R_E \parallel Z_o \parallel R_L}{R_s^1 + z_r}$$

$$R_{in}^d = R_s^1 + z_r$$

$$R_{out}^d = Z_o \parallel R_L \parallel R_E$$

THESE RESULTS  
ARE EXACT AS  
 $\delta$  HAS BEEN  
TAKEN INTO  
ACCOUNT, NOT  
NEGLECTED.

WE CAN NOW DETERMINE THE CLOSED LOOP PARAMETERS

$$A_{v^F}^F = \frac{A_v^a}{1 + \beta A_v^a} = \frac{(\beta_0 + 1) z_{OL} R_E || R_L}{z_{RE} + R_s^I}, \quad \frac{z_{RE} + R_s^I}{R_s^I + z_{RE} + (\beta_0 + 1) z_{OL} R_E || R_L}$$

$$= \frac{(\beta_0 + 1) z_{OL} R_E || R_L}{R_s^I + z_{RE} + (\beta_0 + 1) z_{OL} R_E || R_L} \triangleq \frac{V_o}{V_s} \quad \text{BUT WE ARE INTERESTED IN FINDING } \frac{V_o}{V_s} \rightarrow$$

$$A_{v^F} = \frac{V_o}{V_s} = \underbrace{\frac{V_o}{V_s}}_{A_v^F} \cdot \frac{V_s^I}{V_s} = A_v^F \cdot \frac{R_2 || R_1}{R_s^I + R_2 || R_1}$$

k<sub>s</sub> : INPUT SCALING FACTOR

WHICH IS EXACTLY EQUAL TO THE ONE AS FOUND DIRECTLY ON THIS CIRCUIT (VERIFY AS AN EXERCISE). SIMILARLY:

$$R_{in}^F = R_{in}^{OL} \left( 1 + \beta A_{v^F} \right) = (R_s^I + z_{RE}) \cdot \left( 1 + \frac{(\beta_0 + 1) z_{OL} R_E || R_L}{z_{RE} + R_s^I} \right) =$$

$$= R_s^I + z_{RE} + (\beta_0 + 1) z_{OL} R_E || R_L$$

WE HAVE A SERIES MIXING SO WE CAN DISASSEMBLE R<sub>in</sub><sup>F</sup> AND FIND

$$R_{in} = \underbrace{(R_{in}^F - R_s^I)}_{\text{CLOSED LOOP INPUT RESISTANCE MEASURED AT THE BASE SECTION}} || R_1 || R_2 = R_{in}^{INT} || R_1 || R_2$$

WHICH MATCHES THE ONE FOUND IN THE ORIGINAL CIRCUIT

LET'S CALCULATE THE OUTPUT RESISTANCE


$$R_{out}^F = \frac{R_{out}^a}{1 + \frac{(\beta_0 + 1) z_{OL} R_E || R_L}{z_{RE} + R_s^I}} = \frac{R_{out}^a (z_{RE} + R_s^I)}{R_s^I + z_{RE} + (\beta_0 + 1) R_{out}^a} = R_{out}^a || \frac{R_s^I + z_{RE}}{\beta_0 + 1}$$

AT THE OUTPUT, INSTEAD, WE HAVE A SHUNT STRUCTURE. THEREFORE

$$R_{out} = \frac{1}{\frac{1}{R_{out}^F} - \frac{1}{R_L}} = z_o || R_E || \frac{R_s^I + z_{RE}}{\beta_0 + 1}$$

WHICH MATCHES THE ONE FOUND ON THE ORIGINAL CIRCUIT (VERIFY AS AN EXERCISE)

LET'S CONSIDER NOW THE CURRENT AMPLIFIER

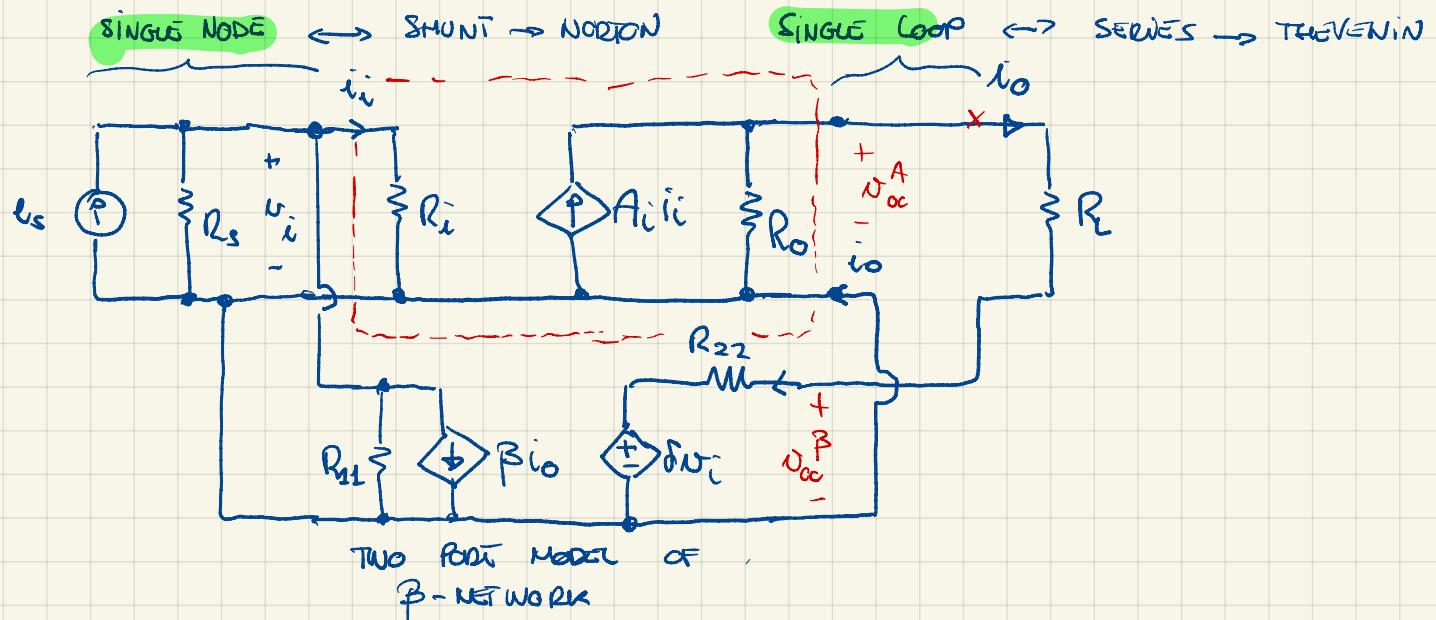

LET'S DISCUSS THE UNILATERALITY ISSUE BY COMPARING OPEN CIRCUIT VOLTAGES

$$v_{oc}^A = R_o \cdot A_i \cdot i_i = R_o A_i i_s \cdot \frac{R_s \parallel R_{11}}{R_i + R_s \parallel R_{11}} = R_o A_i d_i i_s$$

$$v_{oc}^\beta = \delta v_i = \delta \cdot R_s \parallel R_{11} \parallel R_i \cdot i_s$$

$$\frac{v_{oc}^A}{v_{oc}^\beta} = R_o A_i \frac{R_s \parallel R_{11} \parallel R_i}{R_i} \cdot \frac{1}{\delta R_s \parallel R_{11} \parallel R_i} = \frac{R_o}{R_i} \cdot \frac{A_i}{\delta} \gg 1$$


IDEALLY WE WOULD LIKE TO HAVE

$\beta$ -NET IS PASSIVE  $\Rightarrow |\delta| \leq 1$

$$\delta < A_i \cdot \frac{R_s}{R_i} \xrightarrow{\text{large}} \frac{R_s}{R_i} \gg 1$$

THIS INEQUALITY IS MOST LIKELY WELL VERIFIED IN PRACTICAL CASES.

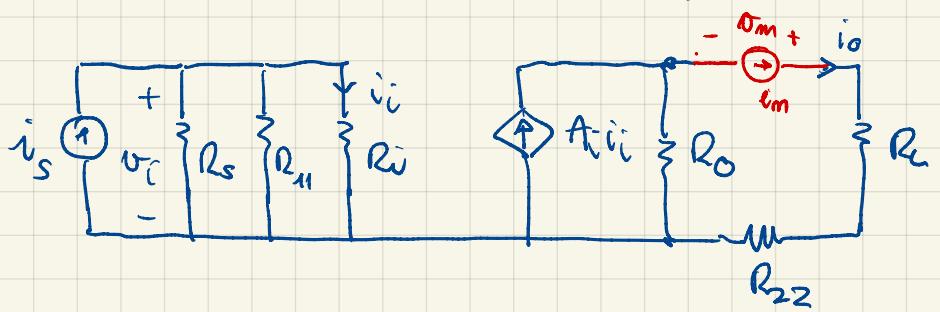NOW WE CAN FIND THE AMPLIFIER PARAMETERS IN OPEN LOOP CONDITIONS THAT IS FOR  $\beta = 0$  AND  $\delta \approx 0$ .



$$A_i^a = \frac{i_o}{i_s} = \underbrace{\frac{R_s || R_{11}}{R_s || R_{11} + R_i}}_{\alpha_i} \cdot A_i \cdot \frac{R_o}{R_o + R_{22} + R_L} = \alpha_i A_i \alpha_o$$

$$R_{im}^a = R_s || R_{11} || R_i$$

$$R_{out}^{OL} = R_L + R_{22} + R_o$$

$$i_s = \emptyset \Rightarrow i_i = \emptyset \Rightarrow A_i \cdot i_i = \emptyset$$

LET'S CONSIDER THE CLOSED LOOP CONFIGURATION  $\beta \neq 0 \quad \delta \neq \emptyset$

$$A_i^F \stackrel{\text{def}}{=} \frac{i_o}{i_s} = \frac{A_i^{OL}}{1 + \beta A_i^{OL}} \quad \text{AS INDICATED IN SUMMARY TABLE}$$

$$\begin{cases} i_i = (i_s - \beta i_o) \alpha_i \\ i_o = \alpha_o \cdot A_i \cdot i_i \end{cases} \Leftrightarrow i_o = \alpha_o A_i (i_s - \beta i_o) \alpha_i \Leftrightarrow$$

$$\Leftrightarrow i_o (1 + \beta A_i^{OL}) = A_i^a \cdot i_s \Rightarrow \frac{i_o}{i_s} = \dots$$

$$R_{im}^F = \frac{R_{im}^{OL}}{1 + \beta A_i^{OL}} \quad \text{AS INDICATED IN SUMMARY TABLE}$$

$$v_i = (i_s - \beta i_o) R_{im}^{OL} = i_s \left(1 - \frac{\beta A_i^a}{1 + \beta A_i^a}\right) \cdot R_{im}^{OL} \Rightarrow \frac{v_i}{i_s} = \dots$$

$$R_{out}^F = R_{out}^{OL} \cdot (1 + \beta A_i^a) \quad \text{AS IN SUMMARY TABLE}$$

$$\left\{ \begin{array}{l} -V_m + (R_t + R_{22})i_m + R_o(i_m - A_i i_i) = 0 \\ i_i^c = -\beta i_m \cdot \alpha_i \end{array} \right.$$

$$-V_m + (R_t + R_{22})i_m + R_o i_m + \beta A_i R_o \alpha_i i_m = 0$$

$$\frac{V_m}{i_m} = R_t + R_{22} + R_o + \alpha_i A_i \beta R_o = \underbrace{(R_t + R_{22} + R_o)}_R \underbrace{\left(1 + A_i \alpha_i K_o \beta\right)}_{BA_i^{\text{OL}}} \Rightarrow \dots$$

WE HAVE THUS PROVEN ROW 2 AND 3 OF THE SUMMARY TABLE. PROVE ROW 1 AND 4 AS AN EXERCISE.