


$$\begin{cases} -v_{em} + (R_L + R_{22})i_{em} + R_o(i_{em} - A_v i_i) = 0 \\ i_i = -\beta i_{em} \cdot \alpha_i \end{cases}$$

$$-v_{em} + (R_L + R_{22})i_{em} + R_o i_{em} + \beta A_i R_o \alpha_i i_{em} = 0$$

$$\frac{v_{em}}{i_{em}} = R_L + R_{22} + R_o + \alpha_i A_i \beta R_o = \underbrace{(R_L + R_{22} + R_o)}_{R_{out}} \underbrace{(1 + A_i \alpha_i \beta)}_{\beta A_i^{cl}} \Rightarrow \dots$$

WE HAVE THUS PROVEN ROW 2 AND 3 OF THE SUMMARY TABLE. PROVE ROW 1 AND 4 AS AN EXERCISE.

### EXERCISE #1: CB AMPLIFIER

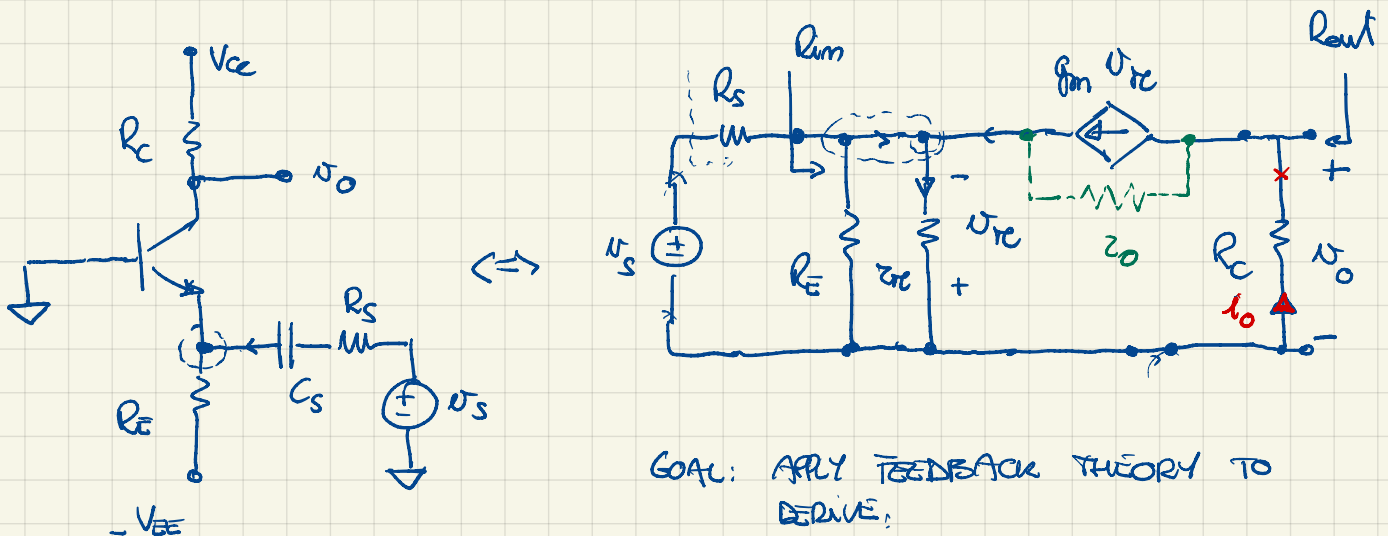

GOAL: APPLY FEEDBACK THEORY TO DERIVE:

$$A_v \triangleq \frac{v_o}{v_s}, \quad R_{in}, \quad R_{out}$$


1. IDENTIFY THE AMPLIFIER'S TOPOLOGY
2. IDENTIFY  $\beta$ -NETWORK
3. BUILD THE 2-PORT MODEL OF  $\beta$ -NETWORK
4. REPLACE THE  $\beta$ -NETWORK WITH THE 2-PORT MODEL
5. SOLVE CIRCUIT IN OPEN LOOP CONDITIONS  $\beta=0 \quad \delta \approx 0$
6. DERIVE CLOSED LOOP QUANTITIES APPLYING THEORY
7. "ADJUST" RESULTS TO FIND TARGET QUANTITIES

$$A_{vT} = g_m R_C \cdot \frac{R_L \parallel R_o \parallel \frac{1}{g_m}}{R_s + R_s \parallel R_o \parallel \frac{1}{g_m}}$$

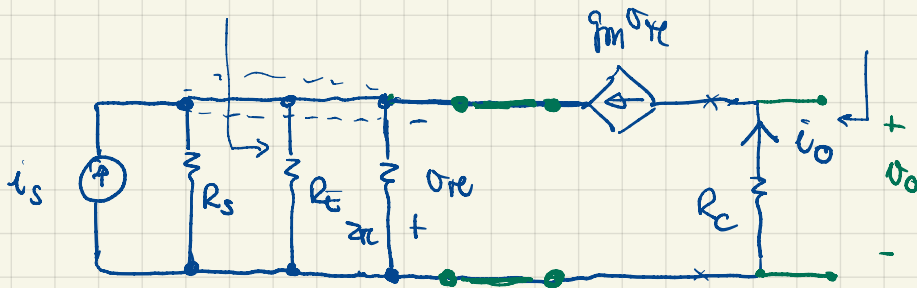1. CIRCUIT INSPECTION SHOWS THE CIRCUIT IS PROBING CURRENT.


INPUT MIXING IS AGAIN CURRENT TYPE (SHORTING  $v_{re}$  KILLS FEEDBACK)

CONCLUSION: CB STAGE CAN BE CONSIDERED A CASE OF CURRENT AMPLIFIER.




$i_s = \frac{v_s}{R_s}$  NORTON'S THEOREM

2.  $\beta$ -NETWORK IN THE CIRCUIT

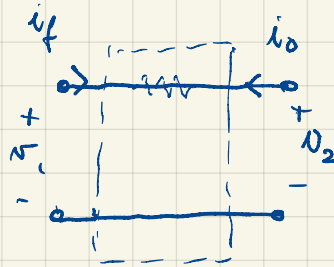

3. 2-PORT MODEL

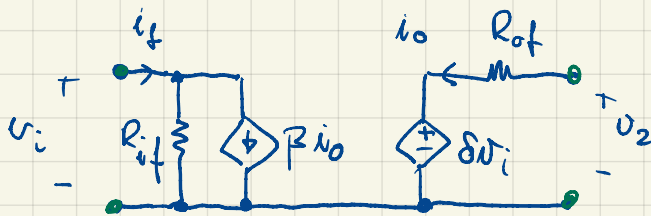

$R_{if} \triangleq \frac{v_i}{i_i} \Big|_{i_o=0} = +\infty$

$\beta \triangleq \frac{i_i}{i_o} \Big|_{v_i=0} = -1$


$R_{of} \triangleq \frac{v_o}{i_o} \Big|_{v_i=0} = \emptyset$

$\delta \triangleq \frac{v_o}{v_i} \Big|_{i_o=0} = +1$

$R_{11} = R_{if}$

$R_{22} = R_{of}$

4.

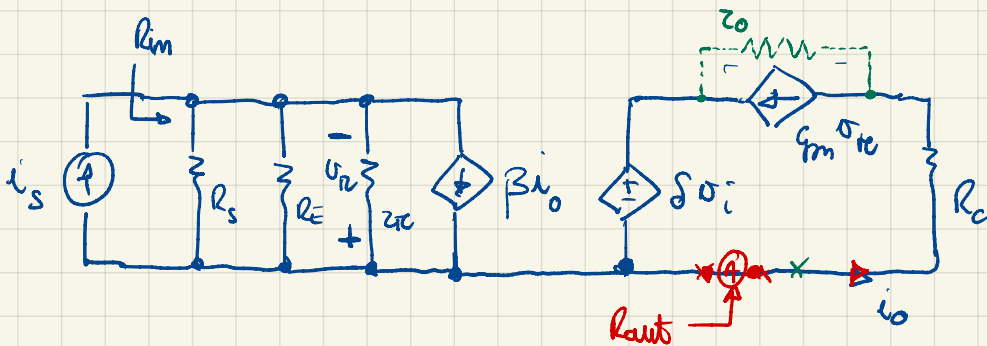

OPTIONAL: DISCUSSION OF UNICATERALITY

OPEN CIRCUIT VOLTAGE

$|g_m z_o \frac{v_{re}}{v_i}| \gg |delta \frac{v_{re}}{v_i}|$   
 $\uparrow$   
 $10^{-2} \cdot 10^5 \gg 1$

AGAIN WE CAN MAKE A VERY SMALL ERROR NEGLECTING  $\delta$

5. STUDY OPEN LOOP AMPLIFIER  $\beta \approx 0$   $\delta \approx 0$

$$A_a \triangleq \frac{i_o}{i_s} = -g_m \cdot R_s \parallel R_E \parallel r_{re} = -g_m R_{in}^{ol}$$

$$i_o = g_m v_{re} = -g_m (R_s \parallel R_E \parallel r_{re}) \cdot i_s$$

$$R_{in}^{ol} = R_s \parallel R_E \parallel r_{re}$$

$$R_{out}^{ol} = +\infty \quad (\text{IN PRACTICE IT WILL BE } r_o + R_c)$$

## 6. APPLY FEEDBACK THEORY TO DERIVE CLOSED LOOP QUANTITIES

$$A_F = \frac{A_a}{1 + \beta A_a} = \frac{-g_m R_{in}^{ol}}{1 - 1 \cdot (-g_m R_{in}^{ol})} = -\frac{g_m R_{in}^{ol}}{1 + g_m R_{in}^{ol}} = -g_m \cdot \left( \frac{1}{g_m} \parallel R_{in}^{ol} \right)$$

$$R_{in}^F = \frac{R_{in}^{ol}}{1 + \beta A_a} = \frac{R_{in}^{ol}}{1 + g_m R_{in}^{ol}}$$

$$R_{out}^F = R_{out}^{ol} (1 + g_m R_{in}^{ol})$$

## 7. ADAPTION OF RESULTS TO FIND TARGET QUANTITIES

$$A_{v0} = \frac{v_o}{v_s} = \frac{v_o}{i_o} \cdot \frac{i_o}{i_s} \cdot \frac{i_s}{v_s} = -R_c A_F \cdot \frac{1}{R_s} = -g_m R_c \cdot \frac{\frac{1}{g_m} \parallel R_s \parallel R_E \parallel r_{re}}{R_s} =$$

$$= -g_m R_c \frac{\frac{1}{g_m} \parallel r_{re} \parallel R_E}{R_s + \frac{1}{g_m} \parallel r_{re} \parallel R_E}$$

THIS IS THE SAME RESULT WE CAN GET BY DIRECTLY SOLVING THE CIRCUIT



$$R_{in} = \frac{1}{\frac{1}{R_{in}^F} - \frac{1}{R_s}} = R_E \parallel r_{re} \parallel \frac{1}{g_m}$$

AGAIN, THIS IS WHAT WE FIND DIRECTLY ANALYSING THE CIRCUIT

$$R_{out} = (R_{out}^F - R_c) \parallel R_c = R_c$$

SAME CONCLUSION HERE!

# EXERCISE # 2: **CER AMPLIFIER**

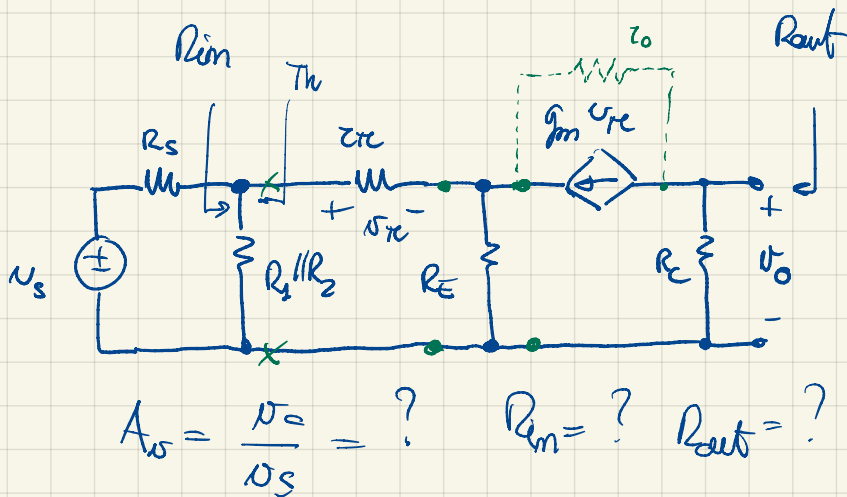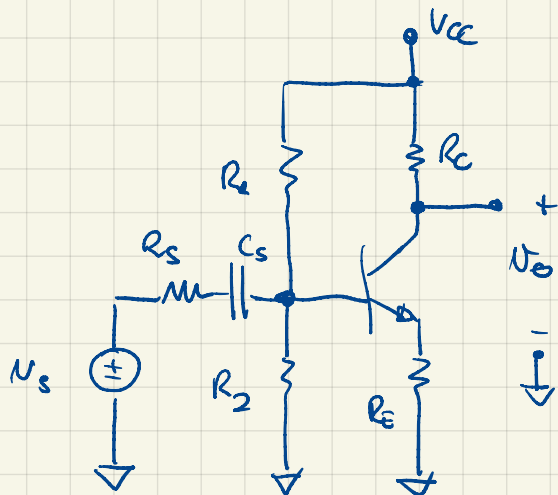


APPLYING FEEDBACK THEORY WE SEE THAT

INPUT MIXING IS **VOLTAGE TYPE**  $\leftrightarrow$  SERIES  $\leftrightarrow$  THEVENIN


OUTPUT SENSING IS **CURRENT TYPE**  $\leftrightarrow$  SERIES  $\leftrightarrow$  THEVENIN

CER IS A CASE OF **TRANS CONDUCTANCE** AMPLIFIER!

$\beta$ -NETWORK IS

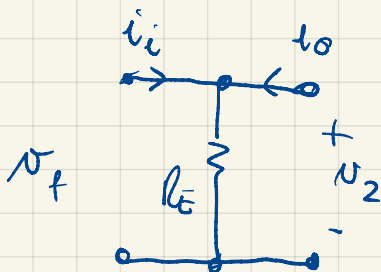

THE MODEL IS

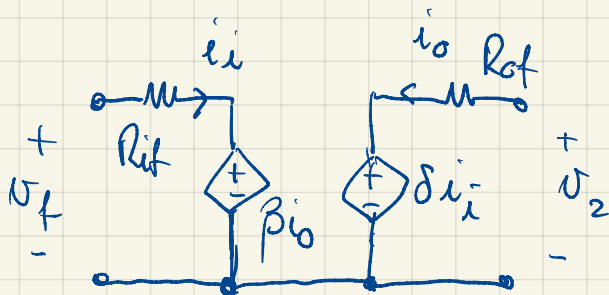


$$R_{if} \triangleq \frac{V_2}{i_i} \Big|_{i_o = 0} = R_{in}$$

$$\beta \triangleq \frac{V_2}{i_o} \Big|_{i_i = 0} = R_E$$

$$R_{of} \triangleq \frac{V_2}{i_o} \Big|_{i_i = 0} = R_E$$

$$d \triangleq \frac{V_2}{i_i} \Big|_{i_o = 0} = R_E$$

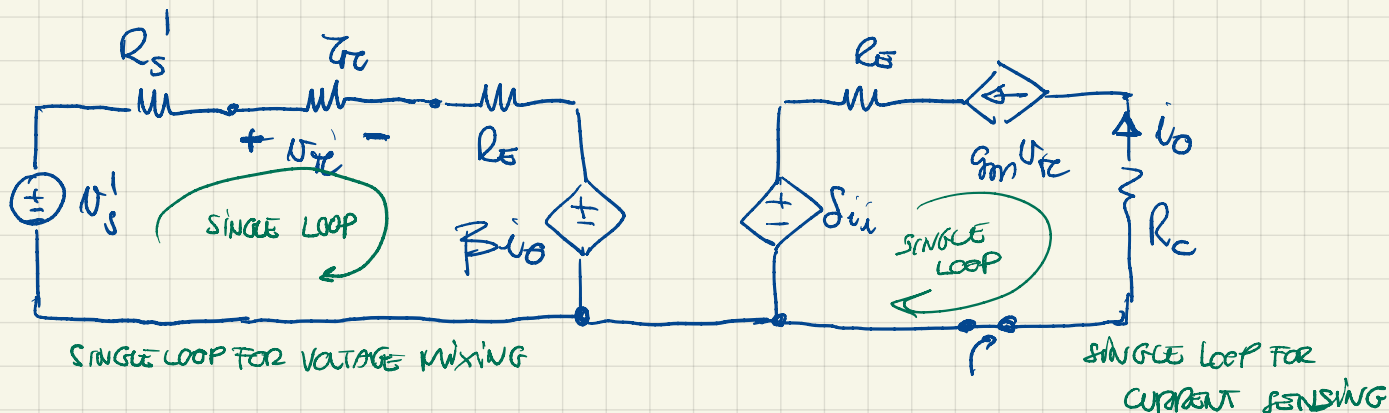REPLACING THE ORIGINAL  $\beta$ -NETWORK WITH ITS 2-PORT MODEL WE FIND THE EQUIVALENT CIRCUIT OF THE FEEDBACK AMPLIFIER



$$v_s' = v_s \cdot \frac{R_1 // R_2}{R_s + R_1 // R_2}$$

$$R_s' = R_s // R_1 // R_2$$

$$\delta i_b \ll g_m \cdot z_c \cdot z_e \cdot i_b$$

↓

$$R_E \ll \beta_0 z_c$$

$$10^3 \ll 10^2 \cdot 10^5$$

WELL VERIFIED  
IN PRACTICE !!

UNILATERALITY ASSUMPTION IS WELL POSSED!

$$G_a \stackrel{\Delta}{=} \frac{i_o}{v_s'} = \frac{z_c}{z_c + R_E + R_s'} \cdot g_m = \frac{\beta_0}{z_c + R_E + R_s'}$$

$$R_{in}^a = R_s' + z_c + R_E$$

$$R_{out}^a = +\infty \quad (R_C + R_E + z_c \text{ IN PRACTICAL CASES})$$

CLOSED LOOP PARAMETERS

$$G_F = \frac{G_a}{1 + \beta G_a} = \frac{\frac{\beta_0}{R_{in}}}{1 + \frac{R_E}{R_{in}} \cdot \beta_0} = \frac{\beta_0}{R_{in} + \beta_0 R_E}$$

$$\begin{aligned} R_{in}^F &= R_{in} (1 + \beta G_a) = R_{in} \cdot \left(1 + R_E \frac{\beta_0}{R_{in}}\right) = R_{in} + \beta_0 R_E = \\ &= R_s' + z_c + (\beta_0 + 1) R_E \end{aligned}$$

$$R_{out}^F = R_{out} (1 + \beta G_a) = +\infty$$

TARGET PARAMETERS

$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v_o'} \cdot \frac{v_o'}{v_s'} \cdot \frac{v_s'}{v_s} = - \frac{\beta_o R_c}{R_s' + r_{\pi} + (\beta_o + 1) R_E} \cdot \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2}$$

$\underbrace{\frac{v_o}{v_o'}}_{-R_c} \quad \underbrace{\frac{v_o'}{v_s'}}_{A_F} \quad \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2}$

WHICH IS THE "USUAL" CCR AMPLIFIER VOLTAGE GAIN

$$R_{in} = (R_{in}^{\#} - R_s') \parallel R_1 \parallel R_2 = [r_{\pi} + (\beta_o + 1) R_E] \parallel R_1 \parallel R_2 \quad \text{AS USUAL!}$$

$$R_{out} = (R_{out}^{\#} - R_c) \parallel R_c = R_c \quad \text{AGAIN, AS USUAL.}$$

ONCE AGAIN, THE APPLICATION OF FEEDBACK THEORY PROVIDES THE SAME RESULTS OF DIRECT CIRCUIT ANALYSIS.