


DISCUSS THE AMPLIFIER STABILITY.

BUT WE CAN ALSO SHAPE THE  $\beta$ -NETWORK TO ENHANCE THE AMPLIFIER'S STABILITY MARGINS (PHASE MARGIN AND/OR GAIN MARGIN)

THIS IS CALLED COMPENSATION OF AN AMPLIFIER. THIS WILL BE THE OBJECT OF NEXT LESSONS.

## EXAMPLE

### CE AMPLIFIER WITH SELF-BIAS

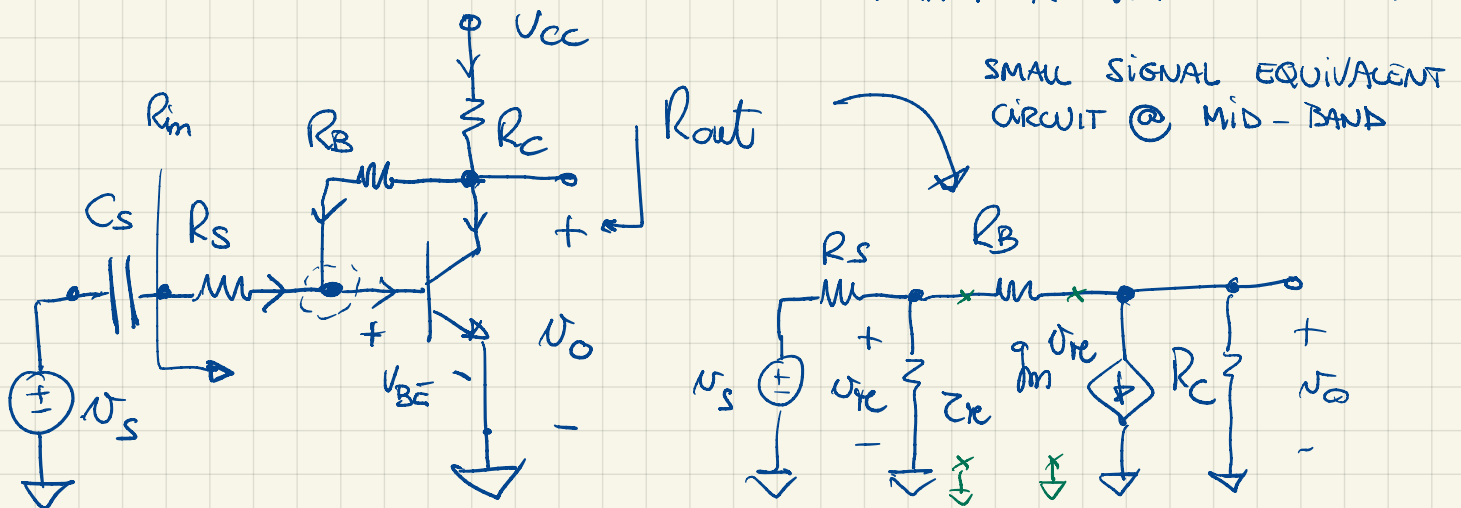

1. FIND  $A_v \triangleq \frac{v_o}{v_s}$ ,  $R_{in}$  AND  $R_{out}$
2. DISCUSS THE POLE LOCATION
3. DRAW THE AMPLIFIER BLOCK DIAGRAM.

BIAS POINT ANALYSIS  $V_{CC} = 5V$   $R_s = 100\Omega$

$$I_C = 1mA$$

$$V_{BE} = 0.7V$$

$$I_B = 10\mu A$$

$$\beta_F = 100 \quad \beta_0 = 200$$

DESIGN CHOICE  $V_o = V_{CC}/2 \rightarrow V_{R_B} = V_o - 0.7V = 1.8V$

$$R_B = \frac{V_{R_B}}{I_B} = 180k\Omega$$

$$R_C = \frac{V_{CC} - V_o}{(\beta_F + 1)I_B} \approx 2.5k\Omega$$



WITH CHOICES  $V_{CE} = 2.5V > V_{CE_{SAT}}$   $I_C = 1mA$  F.A.R. BIAS  $\checkmark$

$$g_m = \frac{I_c}{V_T} = 38 \cdot I_c = 38 \text{ mS}$$

$$V_T = 26 \text{ mV} @ T = 300 \text{ K}$$

$$z_{rc} = \frac{\beta_0}{g_m} \approx 5 \text{ k}\Omega$$

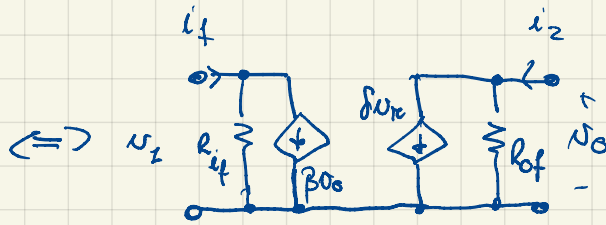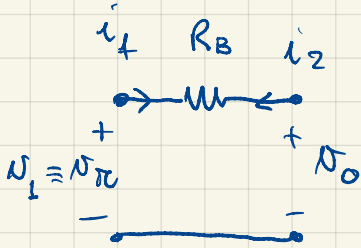FEEDBACK TOPOLOGY: SHUNT-SHUNT (VOLTAGE SENSING, CURRENT MIXING)  $\Rightarrow$  TRANS-RESISTANCE AMPLIFIER




$$R_{if} = \frac{v_1}{i_1} \Big|_{v_o=0} = R_B$$

$$\beta = \frac{i_1}{v_o} \Big|_{v_1=v_{\pi}=0} = -\frac{1}{R_B}$$

$$R_{of} = \frac{v_o}{i_2} \Big|_{v_1=v_{\pi}=0} = R_B$$

$$\delta = \frac{i_2}{v_{\pi}} \Big|_{v_o=0} = -\frac{1}{R_B}$$

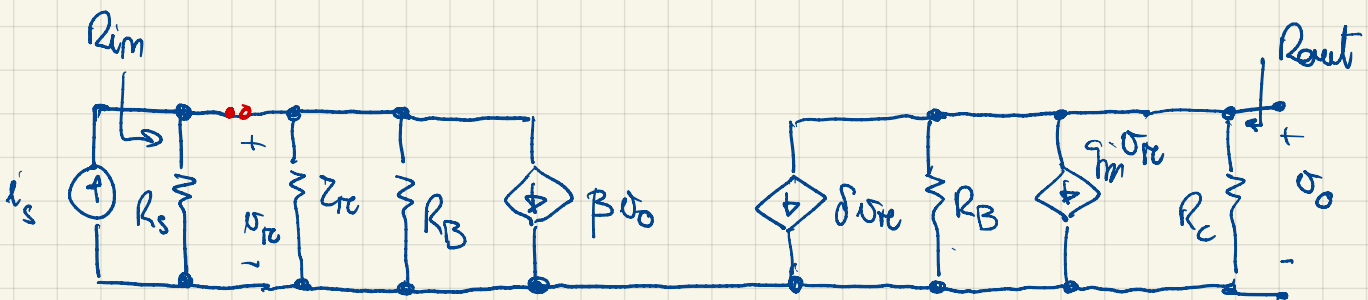

$$i_s = \frac{v_s}{R_s}$$

• UNILATERALITY

$$g_m - \frac{1}{R_B} \approx g_m$$

$\delta$  IS NEGLIGIBLE

$$\uparrow \approx 5 \mu\text{S}$$

• OPEN LOOP PARAMETERS ( $\beta=0, \delta \approx 0$ )

$$A_{ol} = \frac{v_o}{v_s} = -(R_s \parallel R_B \parallel z_{rc}) \cdot g_m \cdot (R_B \parallel R_C) = -R_{in}^{ol} g_m \cdot R_{out}^{ol}$$

$$R_{in}^{ol} = R_s \parallel R_B \parallel z_{rc}$$

$$R_{out}^{ol} = R_B \parallel R_C$$

o CLOSED LOOP PARAMETERS

$$A_F \triangleq \frac{A_a}{1 + \beta A_a} = - \frac{R_{in}^a g_m^a R_{out}^a}{1 - \frac{1}{R_B} (-R_{in}^a g_m^a R_{out}^a)} = - \frac{R_{in}^a g_m^a R_{out}^a}{1 + g_m^a \frac{R_{in}^a R_{out}^a}{R_B}}$$

$$\approx - \frac{10^2 \cdot 38 \cdot 10^{-3} \cdot 2.5 \cdot 10^3}{1 + \frac{10^4}{1.8 \cdot 10^5}} \approx - \frac{10^4}{1.05} \approx 9.5 \cdot 10^3 \text{ } [\Omega]$$

$$R_{in}^F = R_{in}^a / (1 + \beta A_a) \approx 95 \text{ } \Omega$$

$$R_{out}^F = R_{out}^a / (1 + \beta A_a) \approx 2.35 \text{ } k\Omega$$

PARAMETER ADAPTATION

$$Q_{in}^I = \frac{1}{\frac{1}{Q_{in}^F} - \frac{1}{R_s}} = \frac{1}{0.0105 - 0.01} = \frac{1}{0.0005} = 2 \cdot 10^3 \text{ } \Omega$$


$$R_{in} = R_s + Q_{in}^I = 2.1 \text{ } k\Omega$$

$$R_{out} = R_{out}^F$$

$R_s$  INPUT SCALING FACTOR.

$$A_N = \frac{U_o}{U_s} = \frac{U_o}{i_s} \cdot \frac{i_s}{U_s} = A_F \cdot \frac{1}{R_s}$$

BLOCK DIAGRAM OF THE AMPLIFIER

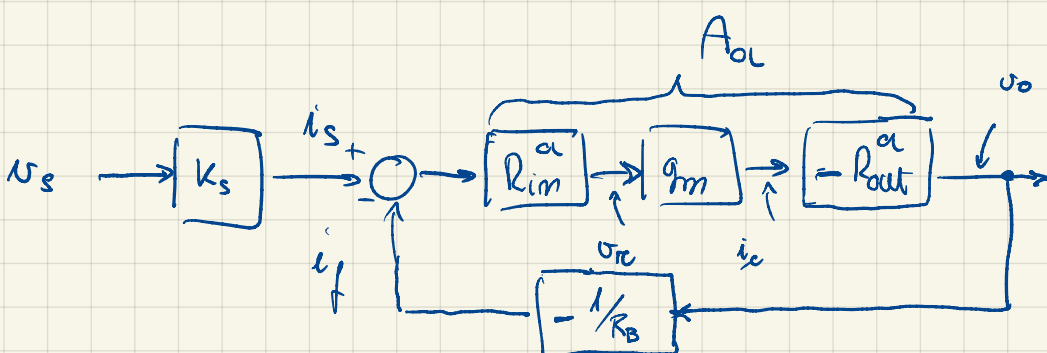

o PZC LOCATION (CONSIDERING ONLY  $C_S \Rightarrow C_{\pi}$  AND  $C_{\mu}$  NEGLIGIBLE)

$$R_{cs} = R_{im} = R_s + R_{im}' = 2.1 \text{ k}\Omega$$

$$Z_{cs} = C_s \cdot R_{cs} \Rightarrow \omega_{cs} = \frac{1}{Z_{cs}} = f_p = \frac{\omega_{cs}}{2\pi}$$

$$R_{cs}^d = R_s + Z_{\pi} \parallel R_B \approx 4.9 \text{ k}\Omega$$

FEEDBACK MADE  $R_{cs}$  SMALLER  $\Rightarrow Z_{cs}$  BECAME SMALLER

$\Rightarrow \omega_p$  IS LARGER!!

NO BANDWIDTH WIDENING IS FOUND.

## EXERCISE #1

Consider the amplifier in the figure, whose parameters at  $T = 25^\circ\text{C}$  are the following:  
 $V_{CC} = 24\text{V}$ ,  $R_2 = 500\text{k}\Omega$ ,  $R_3 = 3\text{k}\Omega$ ,  $R_S = 100\text{k}\Omega$

Q1:  $I_{C1} = 0.6\text{mA}$ ,  $V_{BE} = 0.7\text{V}$ ,  $\beta_F = 50$ ,  $\beta_0 = 80$

Q2:  $V_{BE} = 0.7\text{V}$ ,  $\beta_F = 50$ ,  $\beta_0 = 80$

Considering  $C_1$  a short circuit at mid-band, determine:



- 1) The bias values of  $I_{C2}$ ,  $V_{CE1}$ ,  $V_{CE2}$  and the value of  $R_1$ ; ←
- 2) The type of feedback and the value of  $\beta$ ;
- 3) The open loop amplifier gain  $A_{OL}$ ;
- 4) Voltage gain  $A_V = V_O/V_S$
- 5) Input resistance  $R_{in}$ .

FEEDBACK TOPOLOGY ?

SHUNT @ OUTPUT (VOLTAGE)

SHUNT @ INPUT (CURRENT)

$A_V = -5$  ?

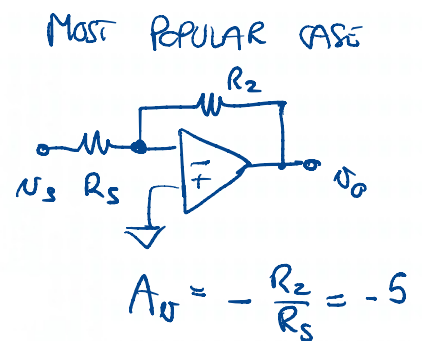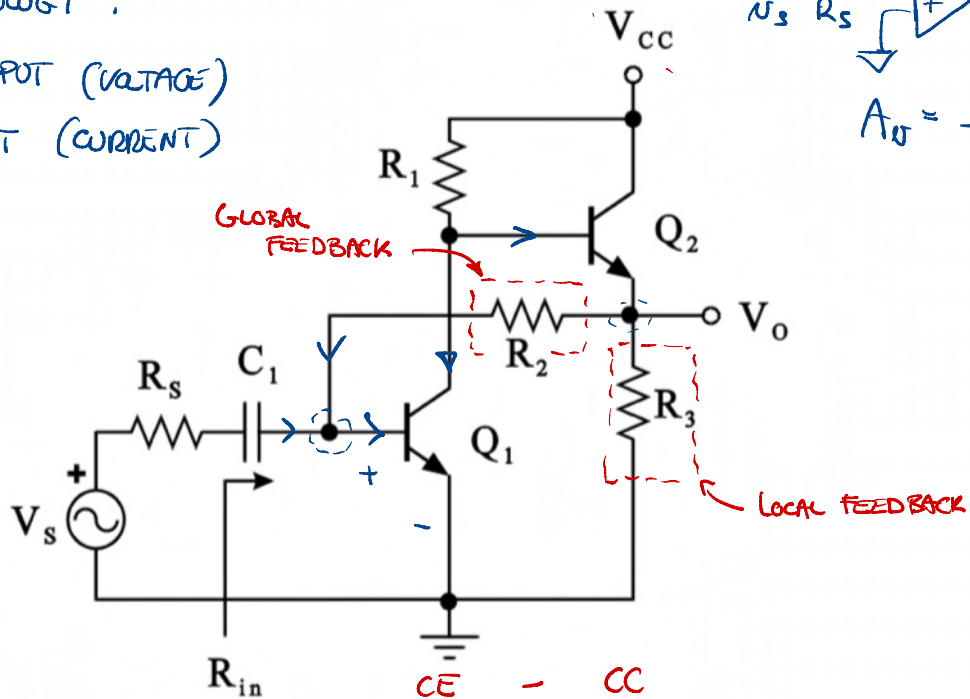

### 1. BIAS POINT ANALYSIS

$$I_{B_1} = \frac{I_{C_1}}{\beta_F} = 12 \mu\text{A}$$

$$V_{O_1} = V_{BE_1} + R_B \cdot I_{B_1} = 0.7\text{V} + 12 \cdot 10^{-6} \cdot 5 \cdot 10^5 = 6.7\text{V}$$

$$V_{CE_2} = V_{CC} - V_{O_1} = 24 - 6.7 = 17.3\text{V} \gg V_{CE_{SAT}}$$

$$I_{R_3} = \frac{V_0}{R_3} = \frac{6.7}{3k} = 2.23 \text{ mA}$$

$$I_{E_2} = I_{R_3} + I_{B_1} = 2.242 \text{ mA}$$

$$I_{B_2} = \frac{I_{E_2}}{\beta_{F_2} + 1} = \frac{2.24}{51} = 44.8 \mu\text{A}$$

$$I_{R_1} = I_{B_2} + I_{C_1} = 0.6 \text{ mA} + 45 \mu\text{A} = 0.645 \text{ mA}$$

$$V_{B_2} = V_0 + V_{BE_2} = 7.4 \text{ V} = V_{CE_1} \gg V_{CE_{SAT_1}} = 0.2 \text{ V}$$

$$V_{R_1} = V_{CC} - V_{B_2} = 24 - 7.4 = 16.6 \text{ V}$$

$$R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{16.6}{0.645} \cdot 10^3 \approx 25.7 \text{ k}\Omega$$

BOTH TRANSISTORS ARE BIASED IN THE FORWARD ACTIVE REGION. ✓

### SIGNAL CIRCUIT PARAMETERS


$$g_{m_1} = \frac{I_{C_1}}{V_T} \approx 25 \text{ mS}$$

$$g_{m_2} = \frac{I_{C_2}}{V_T} \approx 85 \text{ mS}$$

$$r_{\pi_1} = \frac{\beta_{01}}{g_{m_1}} = 3.25 \text{ k}\Omega$$

$$r_{\pi_2} = \frac{\beta_{02}}{g_{m_2}} = 946 \Omega$$

2.

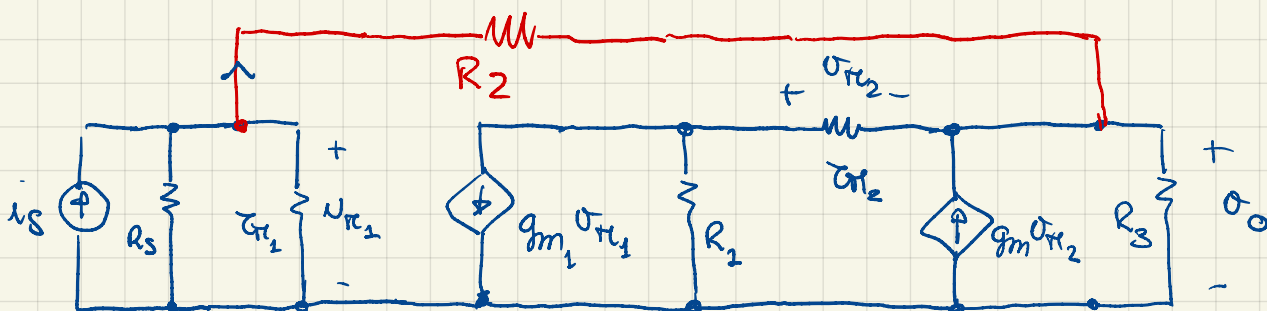


$$i_s = \frac{v_s}{R_s}$$

FEEDBACK TOPOLOGY: SHUNT-SHUNT →

TRANSRESISTANCE AMPLIFIER

### 3. EQUIVALENT CIRCUIT

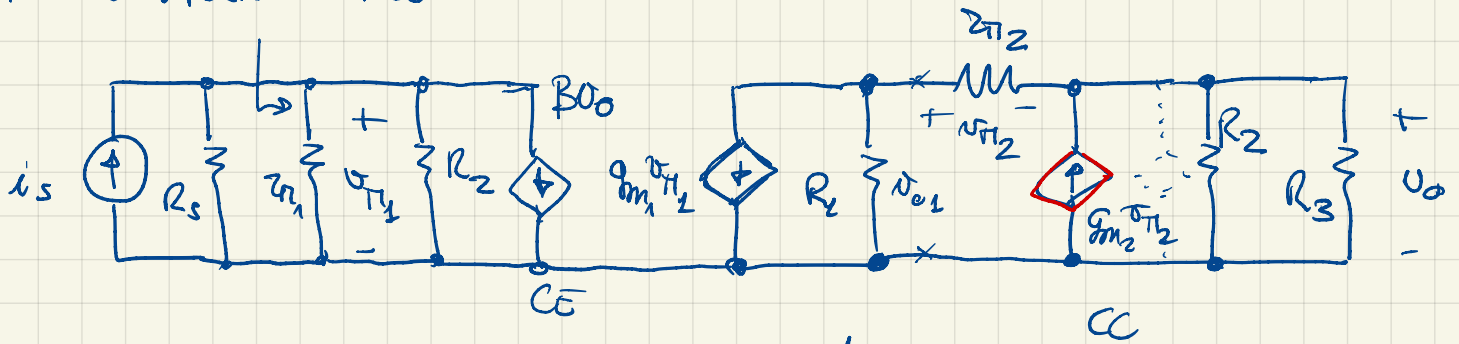

NEGLECTING  $\delta$  AND WITH  $\beta = -\frac{1}{R_2}$

### OPEN LOOP PARAMETERS $\beta=0$

$$\frac{v_o}{v_s} = A_{ol} = - \left( R_s \parallel R_2 \parallel z_{\pi 1} \right) g_{m1} \cdot \left( R_1 \parallel R_{im2}^{cc} \right) \cdot \frac{(\beta_0 + 1) R_2 \parallel R_3}{z_{\pi 2} + (\beta_0 + 1) R_2 \parallel R_3} \approx -1.9 \text{ M}\Omega$$

$$R_{im2}^{cc} = z_{\pi 2} + (\beta_0 + 1) R_2 \parallel R_3 \approx 242 \text{ k}\Omega$$

2.98 k $\Omega$

$$A_f = \frac{A_{ol}}{1 + \beta A_{ol}} = \frac{1.9 \cdot 10^6}{1 + 3.8} = -396 \text{ k}\Omega \quad (\text{DIFFERS FROM } -R_B)$$

T IS NOT  $\gg 1$

$$A_{vD} = \frac{v_o}{v_s} = \underbrace{\frac{v_o}{i_s}}_{A_f} \cdot \underbrace{\frac{i_s}{v_s}}_{r_s = \frac{1}{R_s}} = \frac{A_f}{R_s} = -3.96 \quad (\text{INSTEAD OF } -5)$$

5.

$$R_{in} = \frac{1}{\frac{1}{R_{in}^F} - \frac{1}{R_s}} \approx 706 \text{ }\Omega \quad \text{with} \quad R_{in}^F = \frac{R_{in}}{1 + \beta A_{ol}}$$

# HOMEWORK

## EXERCISE #2

Consider the two stage amplifier in the figure below. The circuit parameters at  $T=25^{\circ}\text{C}$  are the following:

$$V_{CC} = 24 \text{ V}, R_S = 0.6 \text{ k}\Omega, R_1 = 300 \text{ k}\Omega, R_2 = 270 \text{ k}\Omega, R_3 = 4.7 \text{ k}\Omega, R_F = 10 \text{ k}\Omega$$

$$Q_1: I_{DSS} = 1 \text{ mA}, V_T = 5 \text{ V}, r_d = \infty$$

$$Q_2: I_{CQ} = -2 \text{ mA}, V_{CEQ} = -8 \text{ V}, V_{BE} = -0.65 \text{ V}, \beta_F = \beta_0 = 100, r_o = \infty$$

Determine:

- 1) the values of resistances  $R_4$  e  $R_L$ ;
- 2) the type of feedback;
- 3) the feedback gain  $\beta$ ;
- 4) the open loop amplifier gain  $A_{OL}$ ;
- 5) the closed loop amplifier gain  $A_F$ ;
- 6) the voltage gain of the circuit  $A_v = V_O/V_S$ ;
- 7) the indicated output resistance  $R_{OUT}$ .

