


DECEMBER 2ND, 2022

STABILITY AND COMPENSATION OF FEEDBACK AMPLIFIERS

BASIC ASSUMPTIONS

#1 AN ELECTRONIC AMPLIFIER IS **INTRINSICALLY STABLE**

TEST

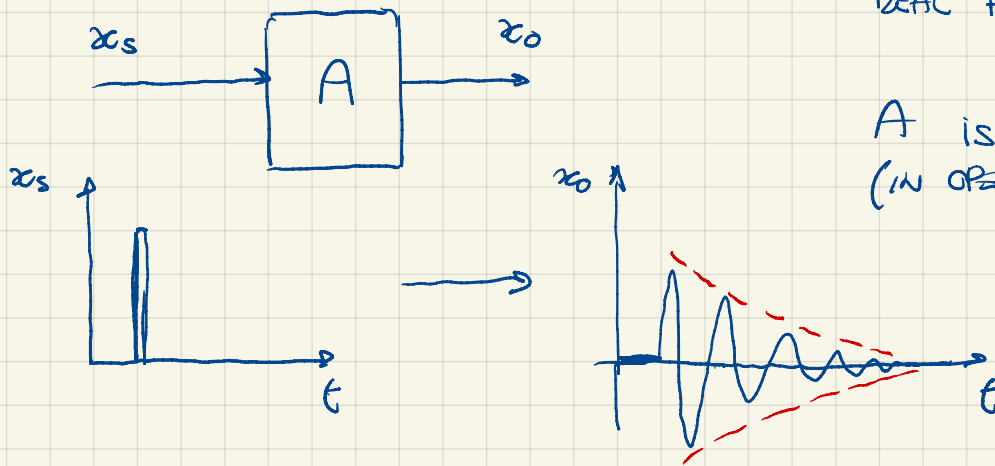

IE. ALL POLES HAVE NEGATIVE REAL PART

A IS BIBO STABLE
(IN OPEN LOOP CONDITIONS)

#2 FEEDBACK IS APPLIED THROUGH A β -NETWORK WHICH IS, MOST OFTEN, A **PASSIVE NETWORK**

\Rightarrow β -NETWORK IS ITSELF INTRINSICALLY STABLE

\Rightarrow THE GAIN OF THE β -NETWORK IS LIMITED AT HIGH FREQUENCY


#1 + #2 \Rightarrow WE CAN USE THE SIMPLEST VERSION OF THE NYQUIST STABILITY CRITERION OR EVEN THE BODE STABILITY CRITERION BECAUSE

$T = \beta \cdot A_{OL}$ HAS NO UNSTABLE POLES

IF INSTABILITY OCCURS, UNDER THE ABOVE ASSUMPTIONS, IT IS ONLY DUE TO **POOR FEEDBACK DESIGN**

THEREFORE STABILITY CAN ALWAYS BE OBTAINED BY PROPERLY DESIGNING THE β -NETWORK. \Rightarrow COMPENSATION IS POSSIBLE.

NYQUIST PLOTS FOR SIMPLE AMPLIFIERS

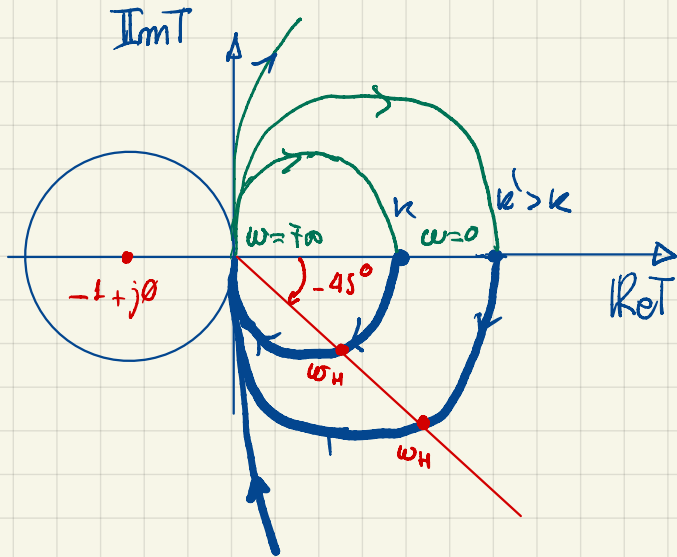


$$T = \frac{k}{1 + \frac{s}{\omega_p}}$$

SINGLE POLE AMPLIFIER

β-NETWORK HAS CONSTANT GAIN β

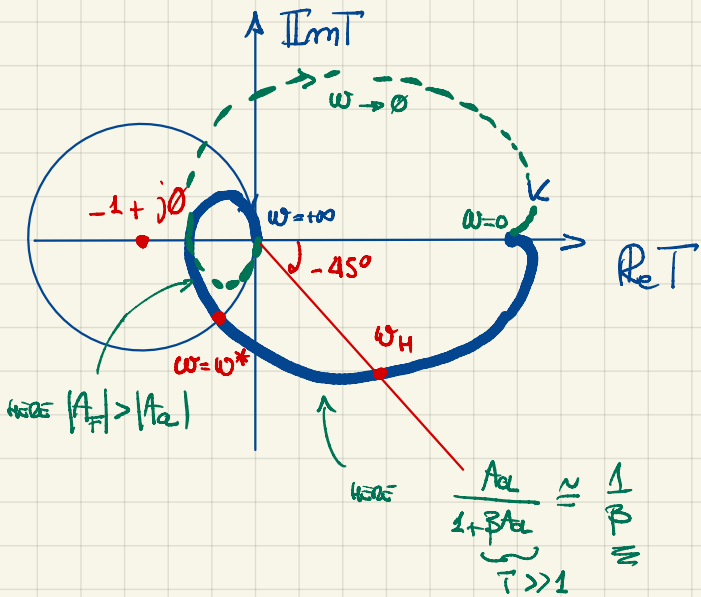THIS TYPE OF AMPLIFIER (SINGLE POLE, CONSTANT β) IS ALWAYS STABLE NO MATTER HOW BIG IS β.




$$T = \frac{k}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \left(1 + \frac{s}{\omega_{p3}}\right)}$$

THE SYSTEM IS STABLE IF k IS SMALL ENOUGH (CAN BE SET WITH β)

AT FREQUENCIES $\omega > \omega^*$ FEEDBACK BECOMES POSITIVE BECAUSE

$$|1+T| < 1 \Rightarrow |A_F| = \left| \frac{A_o}{1+T} \right| > |A_o|$$


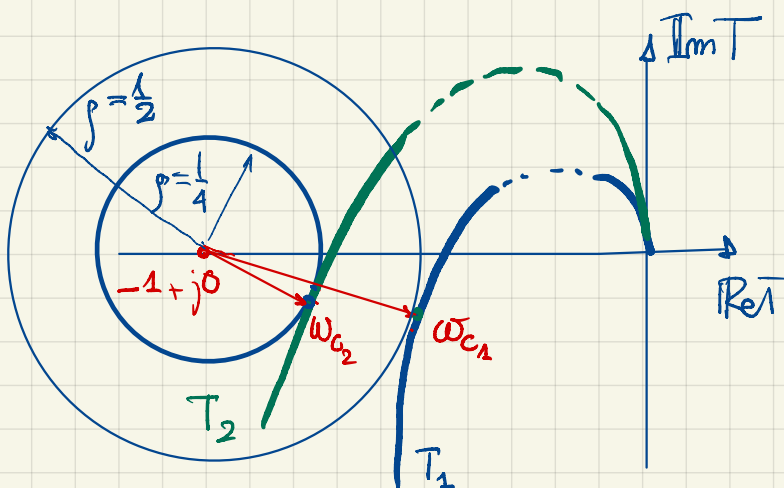
THE IMPACT OF HAVING LOCAL POSITIVE FEEDBACK



$$|1 + T_1(\omega_{c1})| > |1 + T_2(\omega_{c2})| \Rightarrow$$


$$\Rightarrow |A_{F1}(\omega_{c1})| < |A_{F2}(\omega_{c2})|$$

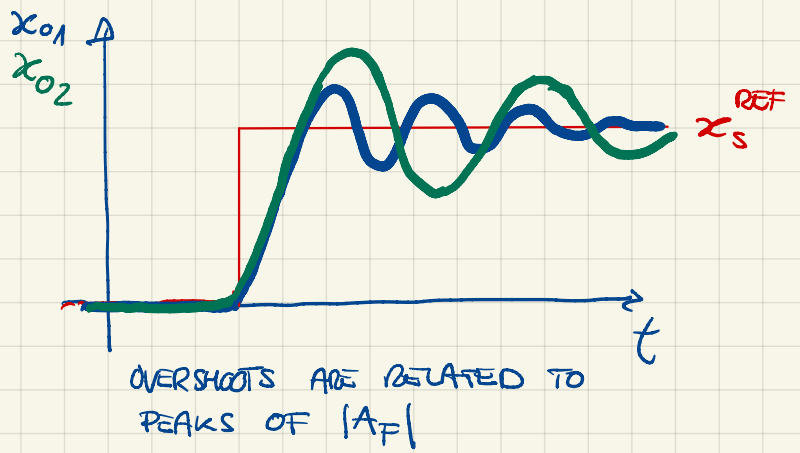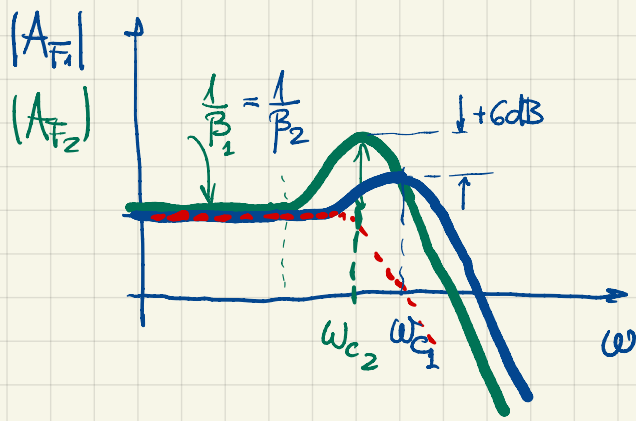PEAKS OF $A_{F1,2}$ FREQUENCY RESPONSE ARE PLACED AT $\omega_{c1,2}$ MINIMUM DISTANCE POINTS OF THE NYQUIST PLOTS



FROM NYQUIST PLOTS, WE CAN ALSO SEE **STABILITY MARGINS**.

- **GAIN MARGIN**

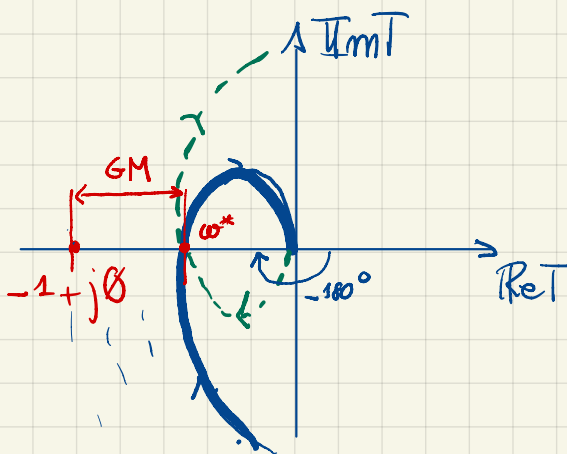


$$GM = 1 - |T(\omega^*)|$$

GM INDICATES HOW MUCH T CAN BE **INFLATED** BEFORE BECOMING UNSTABLE

ω^* IS THE FREQUENCY WHERE $\angle T$ IS EQUAL TO -180° .

- **PHASE MARGIN**

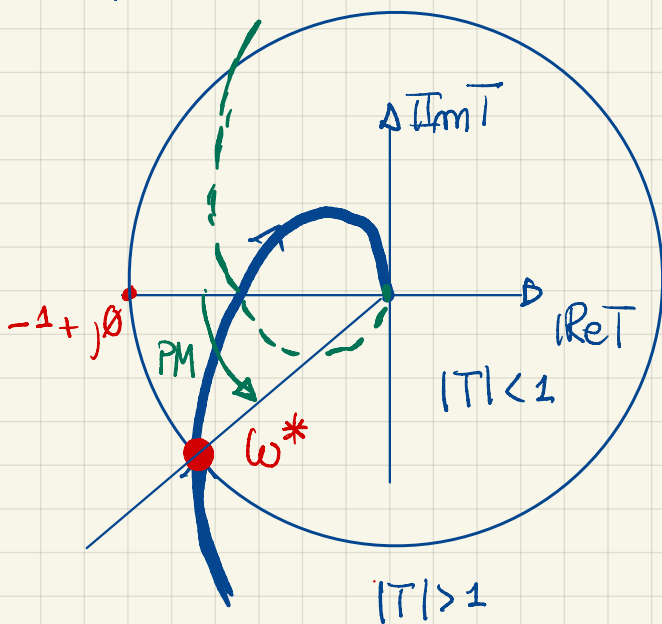


$$PM = 180^\circ + \angle T(\omega^*)$$

PM INDICATES HOW MUCH WE CAN **ROTATE THE PHASE** OF T AT EACH FREQUENCY BEFORE THE SYSTEM BECOMES UNSTABLE

$\omega^* = \omega_{CR}$ FREQUENCY WHERE $|T| = 1$.

IF PM IS < 0 OR GM IS < 0 THE CLOSED LOOP SYSTEM WILL BE UNSTABLE

THERE CAN BE TWO TYPES OF INSTABILITY

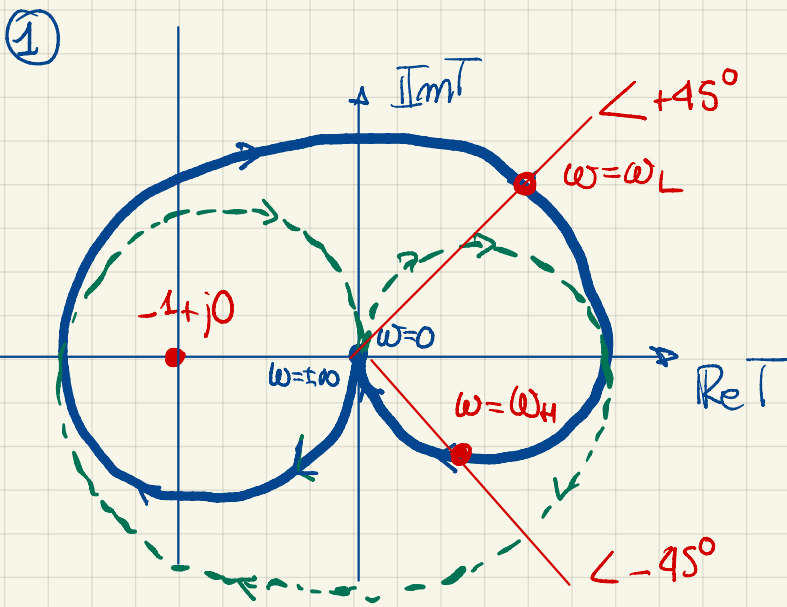


WE HAVE TWO ENCIRCLEMENTS
 → TWO RHP POLES LOCATED
 AT FREQUENCIES BELOW ω_L

THIS IS A LOW FREQUENCY
 TYPE OF INSTABILITY.

IT IS TYPICALLY DUE TO THE
 POOR DESIGN OF COUPLING
 CAPACITORS (TOO SMALL)

"HICCUP" INSTABILITY

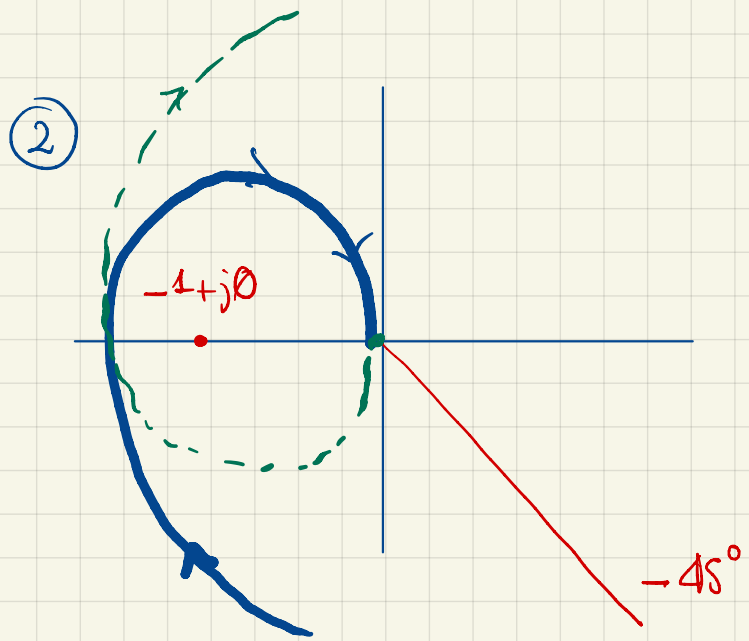


THE INSTABILITY IS TAKING
 PLACE ABOVE ω_H SO AT
 HIGH FREQUENCY

THIS TYPE OF INSTABILITY
 DEPENDS ON THE PARASITIC
 CAPACITORS OF TRANSISTORS
 (C_{μ} , C_{π} , C_{GD} ...) AND
 CAN BE CORRECTED MODIFYING
 THE β -NETWORK.

⇓
 COMPENSATION

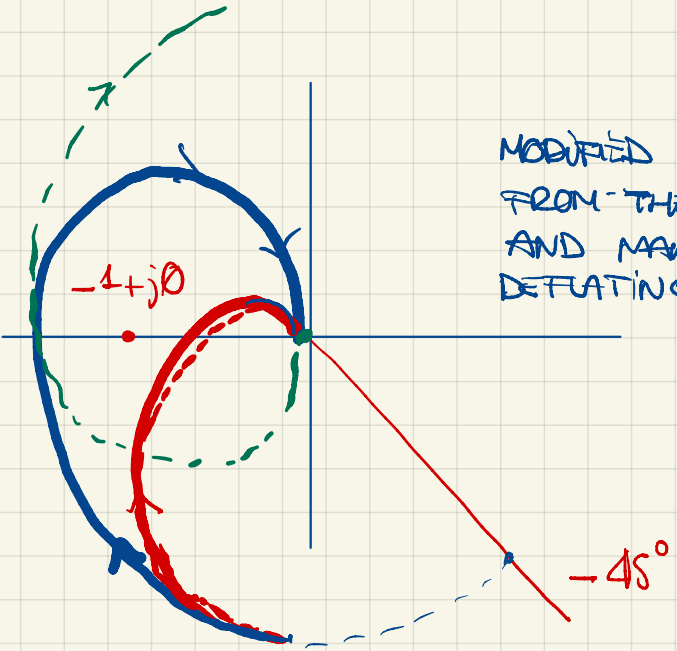FOR EXAMPLE IF WE MODIFY β (WE MAKE IT FREQUENCY DEPENDENT)
 WE CAN STABILIZE THE AMPLIFIER



MODIFIED β -NETWORK BECOMES EFFECTIVE (DIFFERS
 FROM THE ORIGINAL ONE) ONLY AT $\omega \gg \omega_H$
 AND MAKES THE AMPLIFIER STABLE BY
 DEFATING T AT HIGH FREQUENCY.

$T = \beta A_d$ BEFORE COMPENSATION
 $T' = \beta'(s) \cdot A_d$ AFTER COMPENSATION