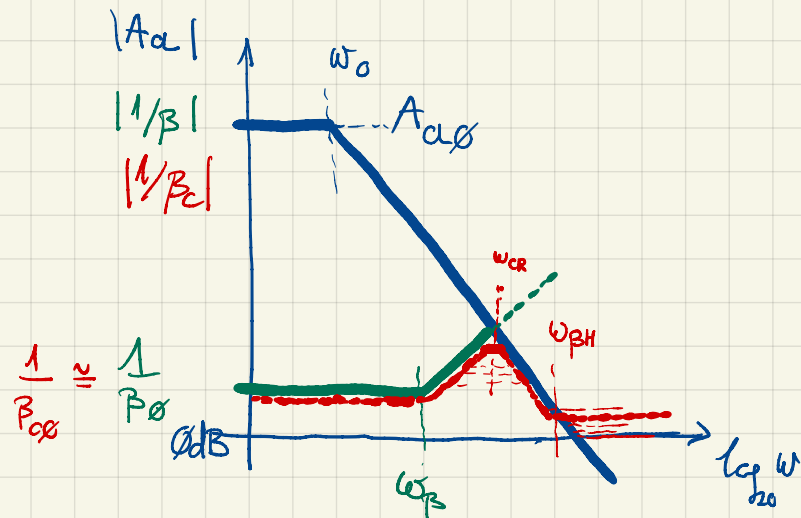



OPENING AND CLOSING RATIOS ARE  $\pm 40 \text{ dB/dec}$   
 $\Rightarrow \text{FM} \approx \emptyset \Rightarrow \text{WE NEED TO APPLY COMPENSATION!}$

$$R_c < R_{out}$$




$$\omega_p = \frac{1}{R_c \cdot C_c}$$

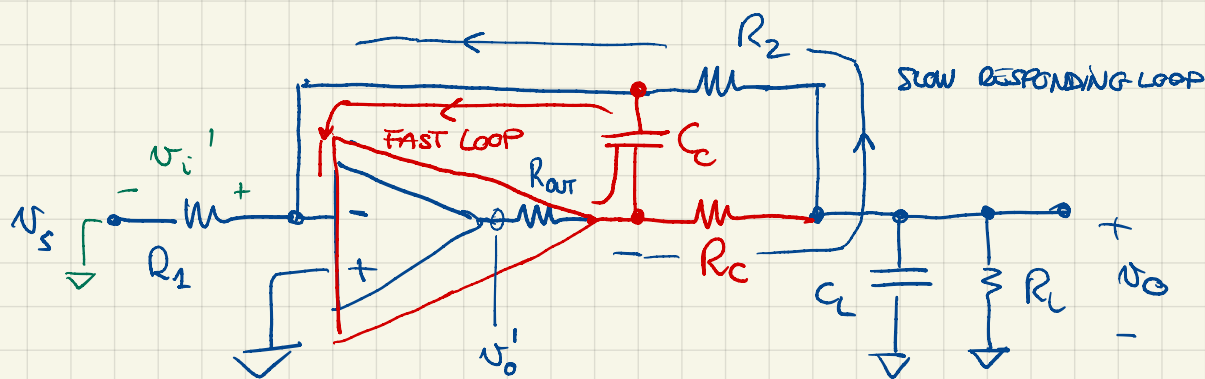A POSSIBLE COMPENSATION NETWORK IS THE FOLLOWING



THE IDEA IS TO **BY-PASS THE DELAYED FEEDBACK** CREATING A FAST FEEDBACK PATH THAT STABILIZES THE AMPLIFIER TURNING IT INTO A FOLLOWER.

$$B_c(s) = \frac{v_o'}{v_o}$$

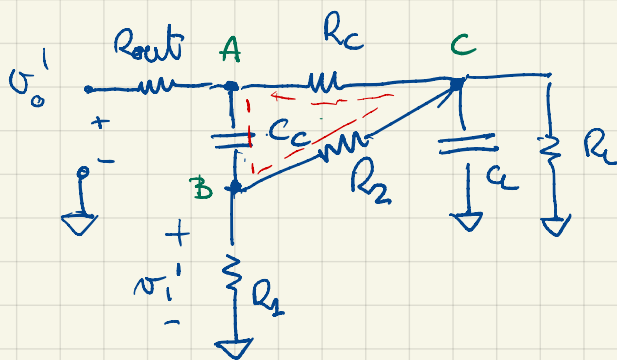

$$R_c = R_c' // (R_c + R_{out})$$

$$\omega_{Bc} \approx \omega_p \quad R_c \ll R_{out}$$

THE EXPLICIT CALCULATION IS CUMBERSOME (TRY AS AN EXERCISE)

HINT: USE TRIANGLE TO STAR TRANSFORM.

$$B_{c0} = \frac{R_1}{R_1 + R_2} \cdot \frac{R_c' // (R_c + R_{out})}{R_{out} + R_c + R_c' // (R_1 + R_2)} \approx B_0$$

$R_{out} + R_c \ll R_c'$

**FIRST DESIGN CRITERION**: KEEP  $\beta_0 \approx \beta_{c0}$  AND  $\omega_p \approx \omega_{pc}$

BOTH CAN BE ACHIEVED WHEN  $R_c \ll R_{out}$ .

$$\beta_{c+\infty} = \frac{R_c \parallel R_1 \parallel R_2}{R_{out} + R_c \parallel R_1 \parallel R_2} \approx \frac{R_c}{R_{out} + R_c} \approx \frac{R_c}{R_{out}} < 1 \rightarrow \text{CHOICE OF } R_c$$

**SECOND DESIGN CRITERION** IS TO PLACE THE HIGH FREQUENCY POLE AT  $\omega_{PH}$  SO THAT

$$A_{ol0} \cdot \omega_0 = \omega_{PH} \cdot \frac{1}{\beta_{c+\infty}} \Rightarrow \omega_{PH} = A_{ol0} \omega_0 \cdot \beta_{c+\infty}$$

$$\omega_{PH} = \frac{1}{C_c R_{cc}} \quad \text{WHERE } R_{cc} = R_c \parallel R_{out} + R_1 \parallel R_2$$


$$C_c = \frac{1}{R_{cc} \cdot \omega_{PH}} \rightarrow \text{CHOICE OF } C_c$$

## SUMMARY

**COMPENSATED OPAMPS**  $\left( A_{cl}(s) = \frac{A_{ol0}}{1 + s/\omega_0} \right)$  DO NOT POSSESS TOO MANY STABILITY PROBLEMS

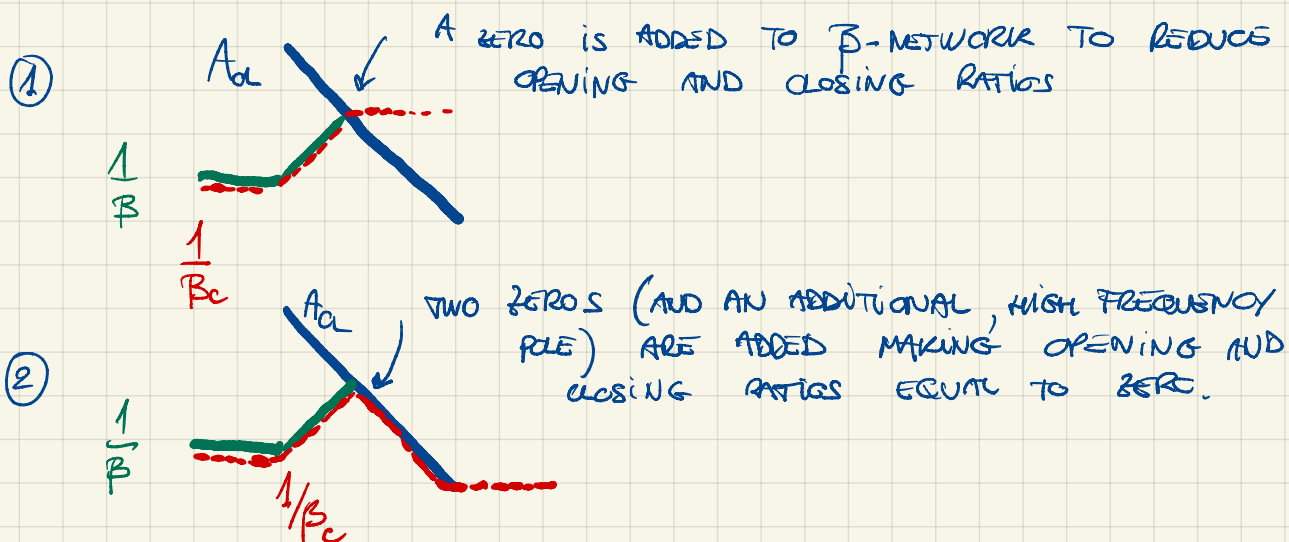
PROBLEMS ARISE MOSTLY FROM **HIGH PASS FREQUENCY RESPONSE** OR FROM **CAPACITIVE LOADS**

COMPENSATION CAN BE IMPLEMENTED IN TWO WAYS



WE DO NOT HAVE ANY STABILITY PROBLEM WHEN


① THE TARGET GAIN IS CONSTANT

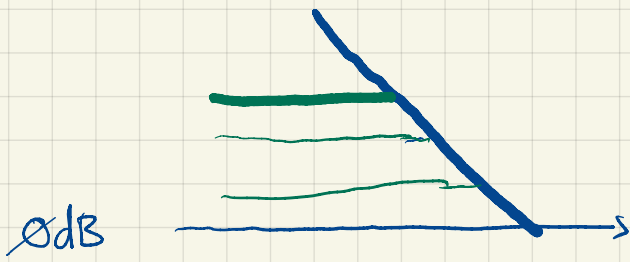

OPENING AND CLOSING RATIOS ARE ALWAYS EQUAL TO  $\pm 20 \text{ dB/dec}$

PM IS LARGE ( $90^\circ$ )

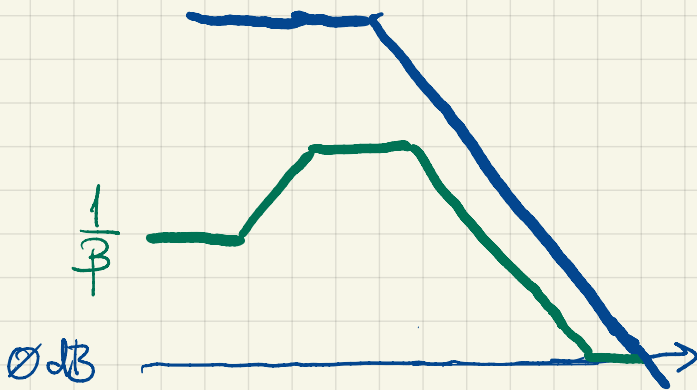
② THE TARGET GAIN IS FREQUENCY DEPENDENT, BUT DOES NOT INTERSECT  $A_\alpha(s)$  WITH CLOSING RATIO  $\leq -40 \text{ dB/dec}$



THE PHASE MARGIN IS ALWAYS LARGE BECAUSE PLOWS OF  $\beta$  DO NOT CAUSE INTERSECTIONS WITH LARGE OPENING AND CLOSING RATIOS

WHAT IF THE OPAMP WE ARE USING IS JUST PARTIALLY COMPENSATED, NON UNITY GAIN STABLE?

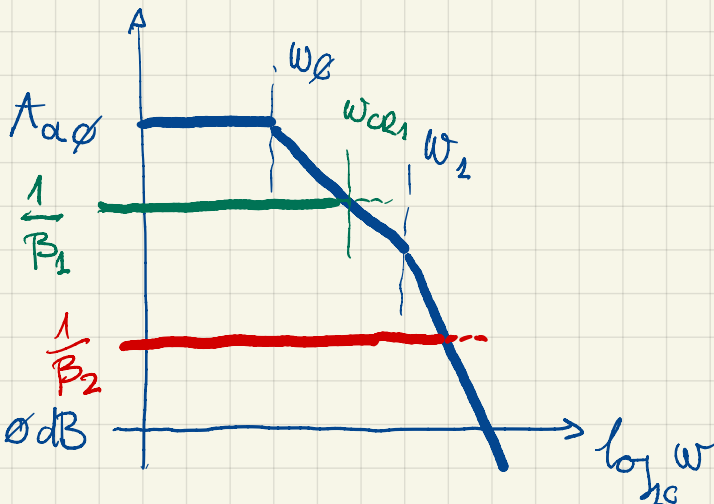THE TYPICAL CASE IS 
$$A_\alpha(s) = \frac{A_{\alpha 0}}{\left(1 + \frac{s}{\omega_0}\right)\left(1 + \frac{s}{\omega_1}\right)}$$




$\beta_1$  YIELDS A STABLE AMPLIFIER WITH CONSTANT GAIN  $1/\beta_1$

$\beta_2$  YIELDS VERY LOW STABILITY MARGIN.


HOW DO WE SOLVE THE PROBLEM? COMPENSATING THE FEED BACK NETWORK.

# STANDARD SOLUTION

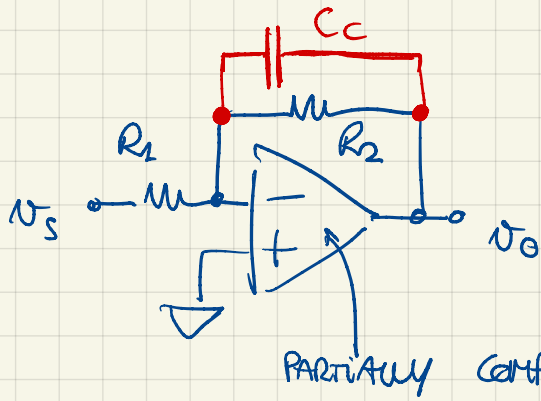

PLACE A COMPENSATION CAPACITOR SO THAT A ZERO IS ADDED TO THE  $\beta$ -NETWORK


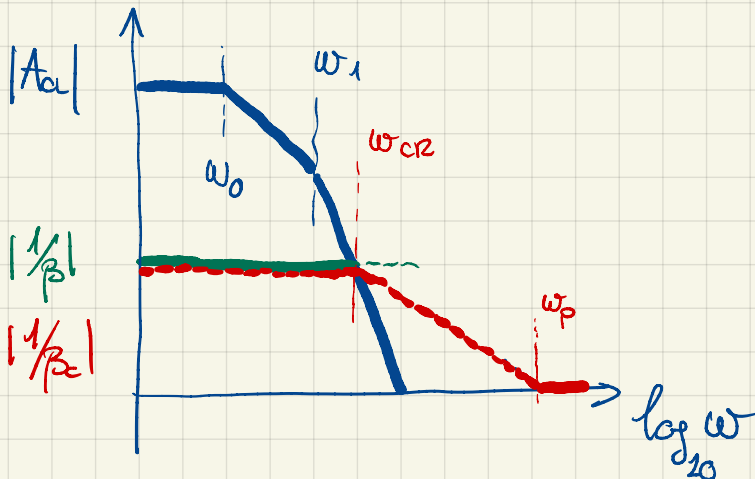
IF  $1 + \frac{R_2}{R_1}$  ( $= \frac{1}{\beta}$ ) IS LOWER THAN SOME LIMIT,  $\Delta PM$  IS



THANKS TO  $C_c$  OPENING AND CLOSING RATIOS ARE  $\pm 20$  dB/dec  $\Rightarrow \Delta PM$  IS LARGER (MINIMUM  $\Delta PM = +45^\circ$ )

THIS TECHNIQUE FAILS TO PROVIDE LARGE  $\Delta PM$  VALUES WHEN THE TARGET GAIN IS RELATIVELY LOW.

EXAMPLE

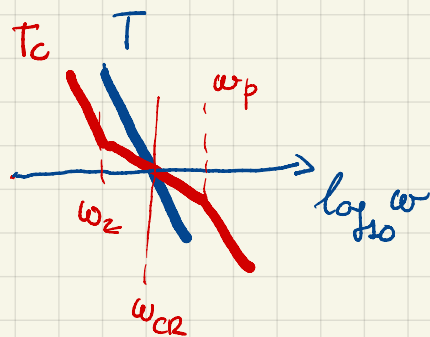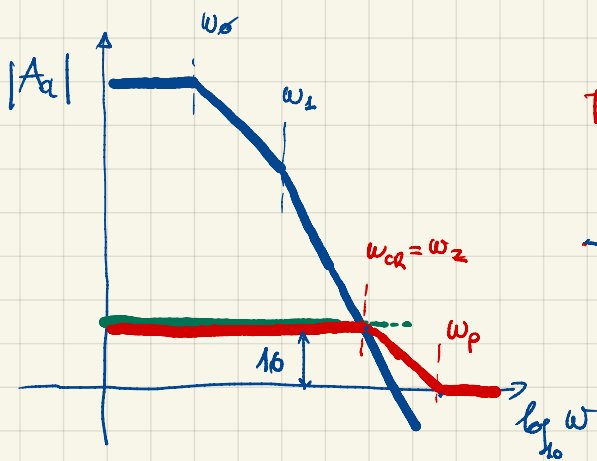


$$\frac{\omega_{cr}}{\omega_2} = \frac{\omega_p}{\omega_{cr}} = 4 \quad \Delta PM = +60^\circ$$

16 IS THE MINIMUM GAIN COMPATIBLE WITH  $\Delta PM = +60^\circ$


16 IS 24 dB!

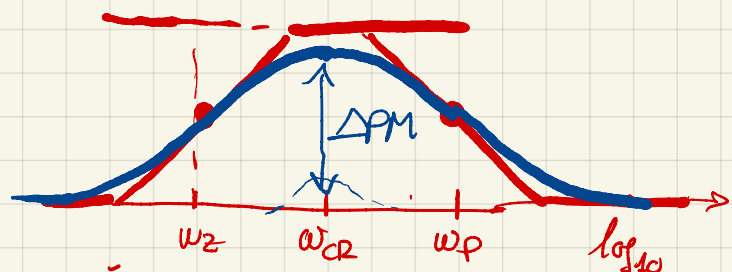WHEN THE TARGET GAIN IS LOWER, THIS TECHNIQUE




NO LONGER ALLOWS  $\Delta PM$  TO BE  $+60^\circ$ .

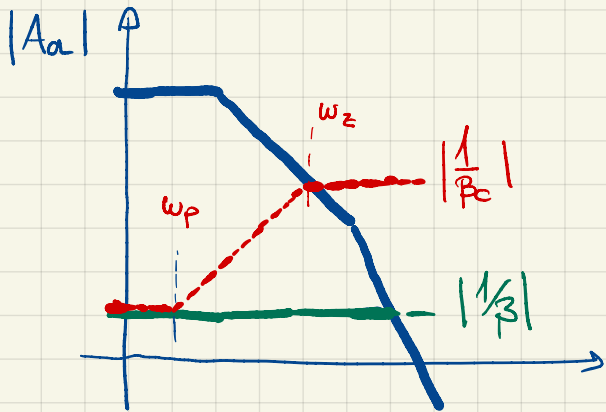OF COURSE, THERE IS AN ALTERNATIVE STRATEGY



THIS IS THE SO-CALLED  
NOISE GAIN COMPENSATION

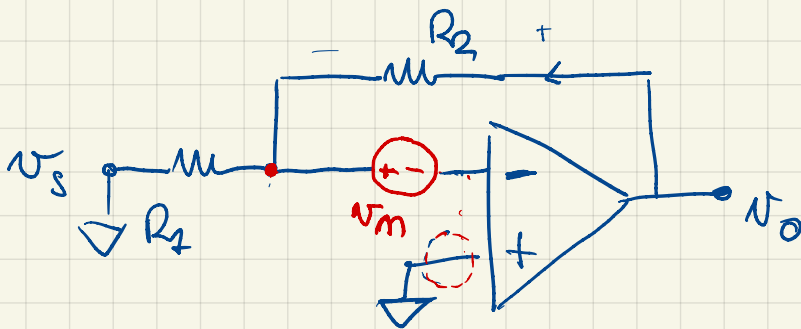$\Delta PM$  CAN BE AS HIGH AS  $+90^\circ$



THE TERM NOISE GAIN  
NG DERIVES FROM

$$1 + \frac{R_2}{R_1}$$


BEING THE AMPLIFICATION  
OF NOISE.

$N_m$  IS NOISE

$$\frac{V_o}{N_m} = 1 + \frac{R_2}{R_1}$$

← THIS IS THE "NOISE GAIN"

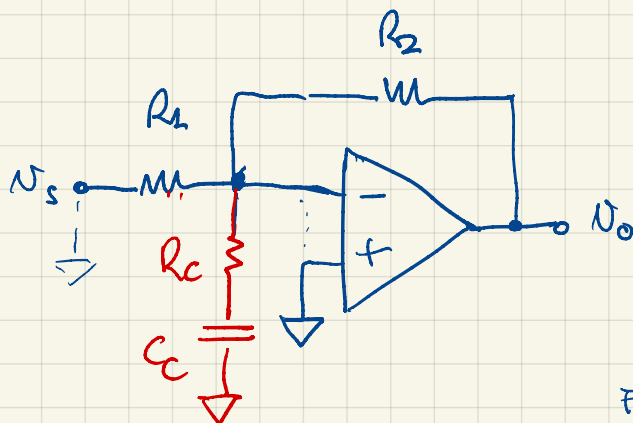
IN THE INVERTING CONFIGURATION NG COMPENSATION LOOKS LIKE THIS:



$$\beta = \frac{V_-}{V_o} = \frac{R_1}{R_1 + R_2}$$

$$\beta_c = \frac{V_-}{V_o} = \frac{R_1 // Z_c}{R_1 // Z_c + R_2}$$

FROM LOOP INSPECTION

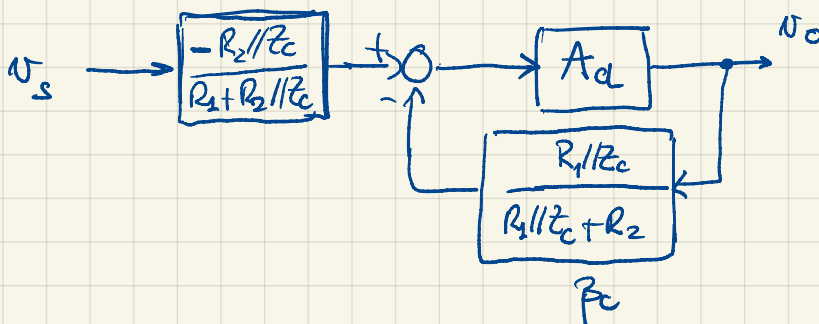

For  $|T| \gg 1$

$$A_{10} = \frac{V_o}{V_s} \stackrel{N}{=} - \frac{R_2 \parallel Z_c}{R_1 + R_2 \parallel Z_c} \cdot \frac{R_2 + R_1 \parallel Z_c}{R_1 \parallel Z_c} = - \frac{R_2}{R_1}$$

↑  
PROVE AS EXERCISE

HINT:  $\frac{R_2 \parallel Z_c}{R_1 + R_2 \parallel Z_c} = R_1 \parallel R_2 \parallel Z_c \cdot \frac{1}{R_1}$

$$\frac{R_2 + R_1 \parallel Z_c}{R_1 \parallel Z_c} = \frac{R_2}{R_2 \parallel R_1 \parallel Z_c} \quad \square$$