

**Xmas homework #2**

**Exercise 1**

Consider the two-stage amplifier in Fig. 1. The circuit parameters, at  $T = 25^\circ\text{C}$ , are the following:

$V_{DD} = 9\text{ V}$ ,  $R_g = 1\text{ k}\Omega$ ,  $R_{G1} = R_{G2} = 100\text{ k}\Omega$ ,  $R_D = 5.6\text{ k}\Omega$ ,  $R_S = 1\text{ k}\Omega$ ,  $R_C = 10\text{ k}\Omega$ ,  $R_E = 2.2\text{ k}\Omega$ ;  
 $R_F = 20\text{ k}\Omega$ ,  $C_g = 10\text{ nF}$ ,  $C_F = 1\text{ }\mu\text{F}$ .

$Q_1$ :  $V_{BE} = -0.7\text{ V}$ ;  $\beta_F = 100$ ;  $\beta_0 = 100$ ;  $r_0 = +$ ;

$Q_2$ :  $V_t = 3\text{ V}$ ;  $I_{DSS} = 2.25\text{ mA}$  ;  $r_0 = +$ ;

$V_T = 25\text{ mV}$ .

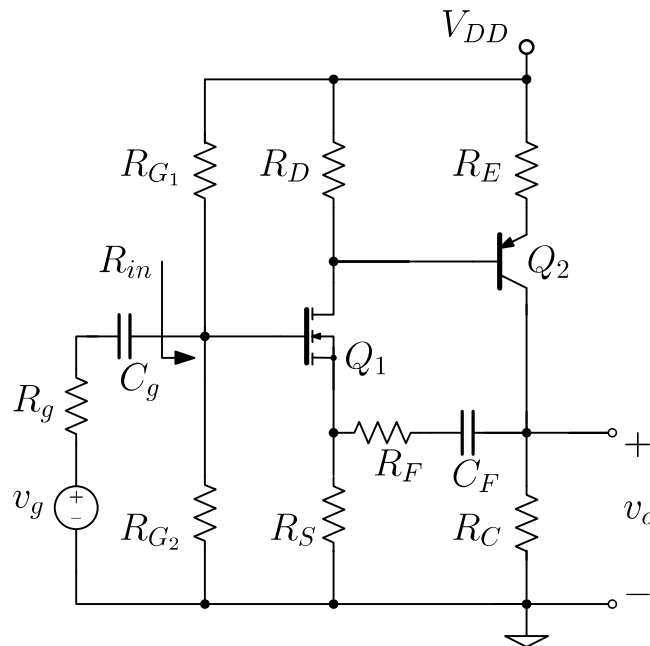


Fig. 1 – Two stage amplifier with feedback.

Considering all capacitors to be equivalent to open circuits, determine:

1. the operating points ( $V_{DS}$ ,  $I_D$ ) of  $Q_1$  and ( $V_{CE}$ ,  $I_C$ ) of  $Q_2$ .

Assuming all capacitors to be equivalent to *short circuits* at the frequencies of interest, determine also:

2. the voltage gain of the amplifier,  $A_v = v_o/v_g$ ;
3. the input resistance indicated in the figure.

Applying the time constant method and **neglecting capacitor  $C_F$** , determine also:


4. an estimation of the low frequency bandwidth limit of the amplifier.

## Exercise 2

Consider the operational amplifier configuration shown in Fig. 2. The circuit parameters are the following:

$R_1 = 1 \text{ k}\Omega$ ;  $R_2 = 33 \text{ k}\Omega$ .
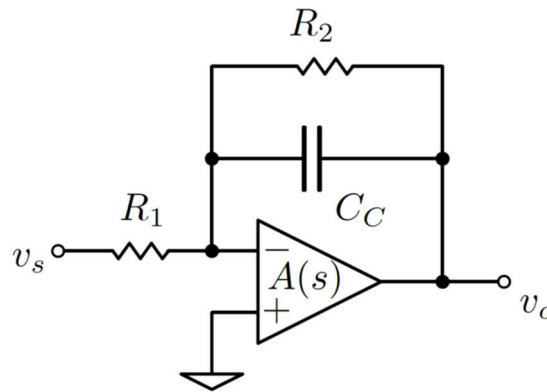
$$A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)} \text{ [V/V]}, \text{ with } A_0 = 10^5 \text{ [V/V]}; \omega_{p1} = 10^2 \text{ rad/s}; \omega_{p2} = 5 \cdot 10^3 \text{ rad/s}.$$



Determine:

1. an estimation of the circuit *phase margin* without  $C_C$ ;
2. a block diagram representation of the amplifier, consistent with feedback theory;
3. the value of  $C_C$  that, ideally, makes the low pass filter bandwidth equal to the inverting amplifier's one (before compensation);
4. the new phase margin after  $C_C$  is placed in the circuit.