

FOR  $|T| \gg 1$

$$A_o = \frac{v_o}{v_s} \approx - \frac{R_2 \parallel Z_c}{R_1 + R_2 \parallel Z_c} \cdot \frac{R_2 + R_1 \parallel Z_c}{R_1 \parallel Z_c} = - \frac{R_2}{R_1}$$


PROVE AS EXERCISE

**IMPORTANT:**  
THIS DOES NOT HAPPEN IF  $Z_c$  IS CONNECTED IN PARALLEL TO  $R_1$

HINT:

$$\frac{R_2 \parallel Z_c}{R_1 + R_2 \parallel Z_c} = R_1 \parallel R_2 \parallel Z_c \cdot \frac{1}{R_1}$$
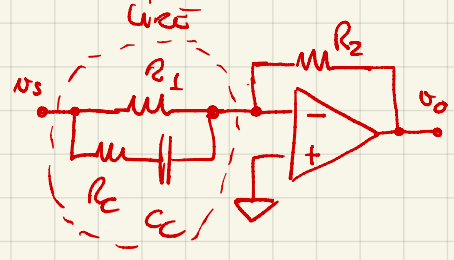
$$\frac{R_2 + R_1 \parallel Z_c}{R_1 \parallel Z_c} = \frac{R_2}{R_2 \parallel R_1 \parallel Z_c}$$




DO NOT USE THIS CONFIGURATION !!

DESIGN OF COMPENSATION NETWORK

TARGET  $\Delta PM = +60^\circ$

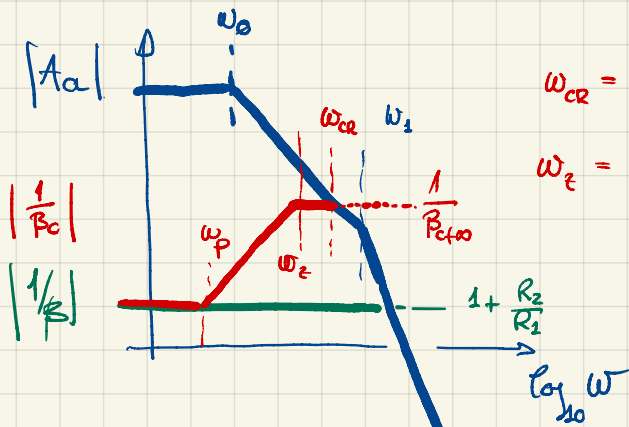THIS MEANS WE ARE DESIGNING  $\beta_c$  SO THAT:



$$\left. \begin{aligned} \omega_{cr} &= \frac{\omega_1}{4} \\ \omega_z &= \frac{\omega_{cr}}{4} \end{aligned} \right\} \Rightarrow \omega_z = \frac{\omega_1}{16}$$

CONDITION TO GET  $\Delta PM = 60^\circ$  WITH A ZERO ( $\omega_z$ ) POLE ( $\omega_1$ ) COMBINATION AROUND  $\omega_{cr}$

TO FIND  $\omega_p$  WE CAN FIND  $\frac{1}{\beta_{ct0}}$

$$A_{cl0} \cdot \omega_0 = \frac{1}{\beta_{ct0}} \cdot \frac{\omega_1}{4} \Rightarrow \frac{1}{\beta_{ct0}} = \frac{4 A_{cl0} \omega_0}{\omega_1}$$

THAT IS KNOWN FROM OPAAMP CHARACTERISTICS

FROM THIS WE FIND  $\omega_p$  IMPOSING

$$\frac{1}{\omega_p \beta_{ct0}} = \frac{1}{\beta_{ct0}} \cdot \frac{1}{\omega_p} = \frac{1}{\beta_{ct0}} \cdot \frac{16}{\omega_1} \Rightarrow \omega_p = \frac{\beta_{ct0} \omega_1}{16 \beta_{ct0}} = \frac{\omega_1^2}{64 A_{cl0} \omega_0 \beta_{ct0}}$$

IN THIS CIRCUIT

$$\frac{1}{\beta_c}(s) = 1 + \frac{R_2}{R_1 \parallel Z_c} = 1 + R_2 \cdot \left( \frac{1}{R_1} + \frac{1}{R_1 \frac{1}{sC_c}} \right) = 1 + \frac{R_2}{R_1} + \frac{sR_2C_c}{1 + sR_1C_c}$$

$$= \frac{(1 + sR_1C_c)(R_1 + R_2) + sR_2R_1C_c}{R_1(1 + sR_1C_c)} = \frac{R_1 + R_2}{R_1} \cdot \frac{1 + sC_c(R_1 + R_2)}{1 + sR_1C_c}$$

FROM WHICH WE SEE THAT :

$$\frac{1}{\beta_{FB}} = 1 + \frac{R_2}{R_1} \quad \text{AS WE EXPECTED IT IS EQUAL TO } \frac{1}{\beta_{FB}}$$

$$\omega_z = 1/R_C C_C \quad \rightarrow \text{ FROM HERE WE SET } C_C = \frac{1}{R_C \omega_z}$$

$$\omega_p = 1/C_C (R_C + R_1 \parallel R_2) \quad \rightarrow \text{ FROM WHICH, USING THIS, WE FIND}$$

$$\omega_p = \frac{R_C \cdot \omega_z}{R_C + R_1 \parallel R_2} = \frac{\omega_z}{1 + \frac{R_1 \parallel R_2}{R_C}} \Leftrightarrow$$

$$R_C = \frac{R_1 \parallel R_2}{\frac{\omega_z}{\omega_p} - 1}$$

$$C_C = \frac{1}{R_C \omega_z}$$

FROM WHICH, FINALLY, WE CAN FIND


### FASTER PROCEDURE

FROM THE CIRCUIT WE SEE THAT  $\frac{1}{\beta_{FB}} = 1 + \frac{R_2}{R_1 \parallel R_C} = \underbrace{A_0 \frac{\omega_0}{\omega_z}}_{\text{KNOWN}}$

FROM HERE WE CAN DIRECTLY FIND  $R_C$

THEN,  $C_C$  IS FOUND AS  $\frac{1}{R_C \omega_z}$

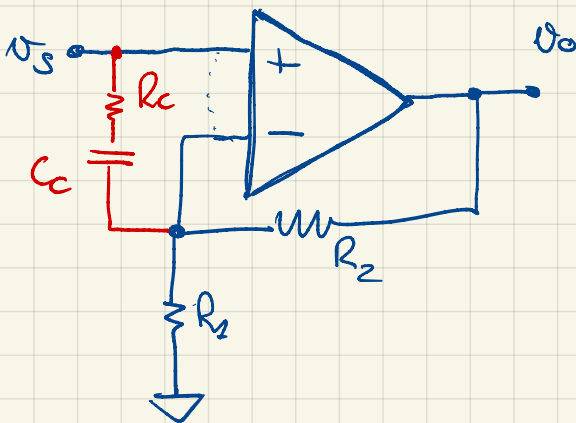IN THE NON-INVERTING CASE THE NOISE GAIN COMPENSATION LOOKS LIKE THIS



WHEN  $|T| \gg 1$   $A_0 = \frac{v_o}{v_s} \approx 1 + \frac{R_2}{R_1}$

BUT THE AMPLIFIER WILL BE COMPENSATED.


THE DESIGN PROCEDURE FOR  $R_C$  AND  $C_C$  IS THE SAME AS IN THE INVERTING CONFIGURATION CASE.

VERIFY THIS AS AN EXERCISE!
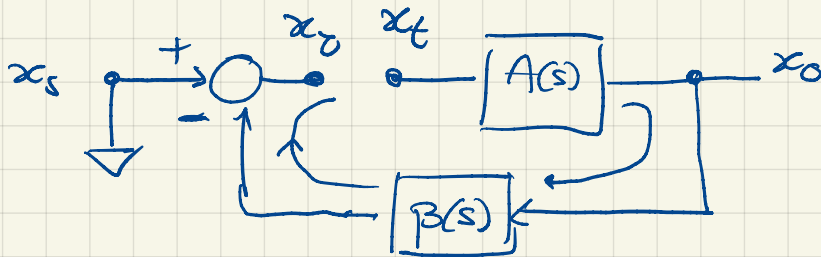
## ◇ OSCILLATORS

- NON SINUSOIDAL (SCHMITT TRIGGER)
- SINUSOIDAL

WE CONSIDER THE LATTER CASE. ALL BEGINS WITH A FEEDBACK AMPLIFIER



$$\frac{x_o}{x_e} = \frac{A}{1+T}$$

$$\frac{x_R}{x_T}(s) = -A(s) \cdot \beta(s) = -T(s)$$

N.B.  $\angle \frac{x_R}{x_T} = \angle T + \pi$   
DUE TO THE "-" SIGN AT THE SUMMING NODE

IN SINUSOIDAL OSCILLATORS, WE INTENTIONALLY CREATE THE CONDITIONS TO HAVE THE CIRCUIT OSCILLATE AT SOME FREQUENCY  $\omega_0$

THESE CONDITIONS ARE NAMED **BARKHAUSEN** CONDITIONS

$$\begin{cases} |T(j\omega_0)| = 1 \\ \angle T(j\omega_0) = \pm (2m+1)\pi \quad m \in \mathbb{N} \end{cases}$$

THE SIMPLEST WAY TO SATISFY BARKHAUSEN CONDITIONS IS TO HAVE


$$T = -1 \quad @ \quad \omega = \omega_0 \quad \Rightarrow \quad \frac{x_R}{x_T}(j\omega_0) = +1 !!$$

THIS HAPPENS ANY TIME  $1+T$  INCLUDES A TERM AS


$$(s^2 + \omega_0^2) \quad \text{WHICH IS } = 0 \quad @ \quad \omega = \omega_0$$

◇ A TYPICAL OSCILLATOR CIRCUIT IS THE ONE CALLED THE **WIEN BRIDGE**

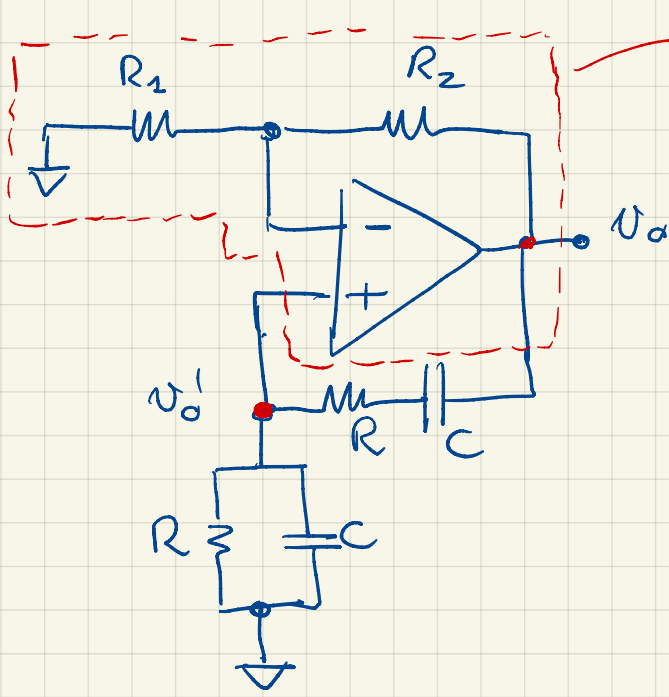OSCILLATOR THAT IS BASED ON A SIMPLE OPAMP CONFIGURATION.



$$A = 1 + \frac{R_2}{R_1}$$

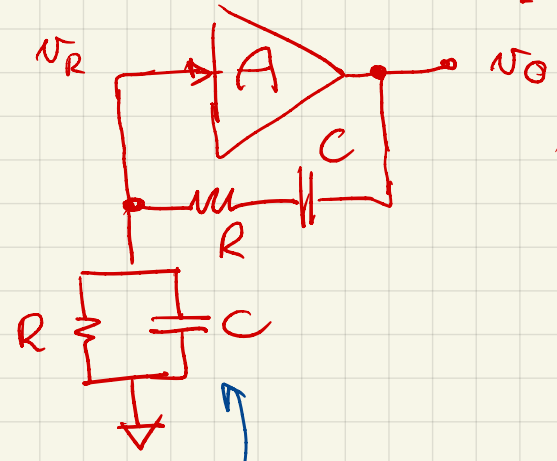

LET'S FIND  $T(s)$  FOR THIS AMPLIFIER

$$T(s) = A \cdot \frac{\frac{R}{1+sRC}}{\frac{R}{1+sRC} + R + \frac{1}{sC}} = A \cdot \frac{R}{R + R(1+sRC) + \frac{1+sRC}{sC}} =$$

$$= A \cdot \frac{sCR}{sCR(2+sCR) + 1+sCR} = A \cdot \frac{sCR}{1+3sCR + s^2(CR)^2}$$

LET'S CONSIDER  $T(j\omega_0)$  WHERE  $\omega_0 = \frac{1}{RC}$

$$\begin{cases} |T(j\omega_0)| = A \cdot \left| \frac{j}{1+3j-1} \right| = \frac{A}{3} \\ \angle T(j\omega_0) = 0^\circ \end{cases}$$


N.B. IN THIS CASE  $\frac{X_R}{X_T}(s) = T(s)$  BECAUSE THERE IS NO SUMMING NODE AND NO SIGN INVERSION.

WE CAN SATISFY BARKHAUSEN CONDITIONS BY MAKING


$$A = 3 \Rightarrow 1 + \frac{R_2}{R_1} = 3 \Rightarrow R_2 = 2R_1$$

IN PRACTICE WE CHOOSE  $R_2 > 2R_1$  TO START THE OSCILLATION RAPIDLY.

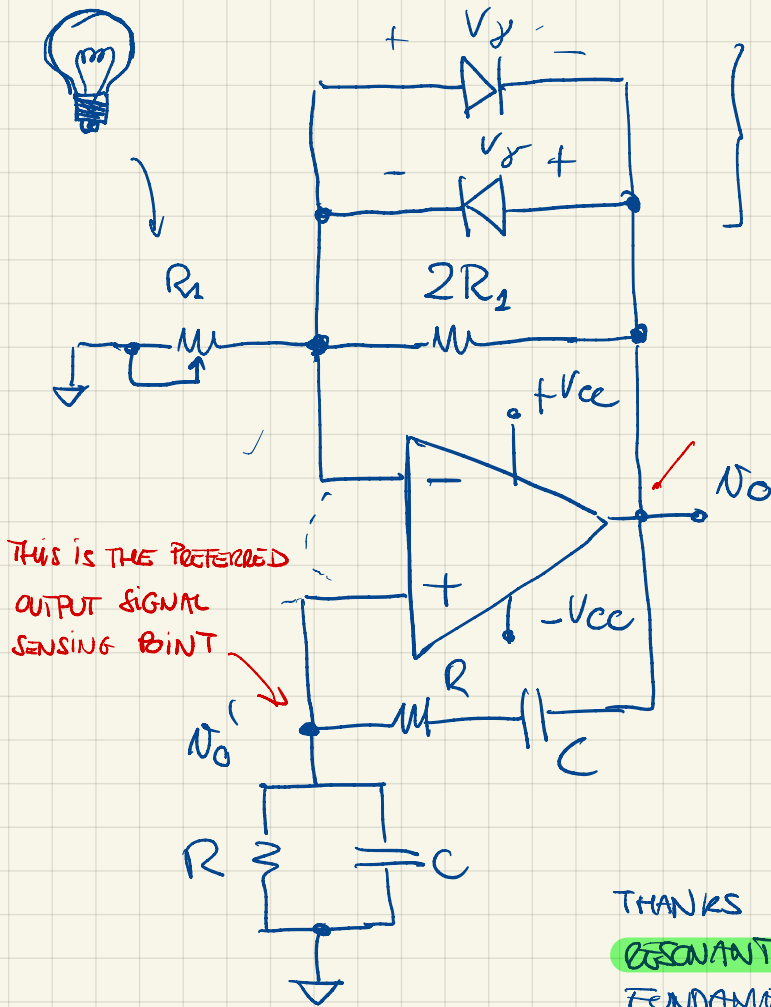AND THEN WE PREVENT SATURATION BY ACTIVELY LIMITING THE OSCILLATION AMPLITUDE. A SIMPLE IMPLEMENTATION IS:



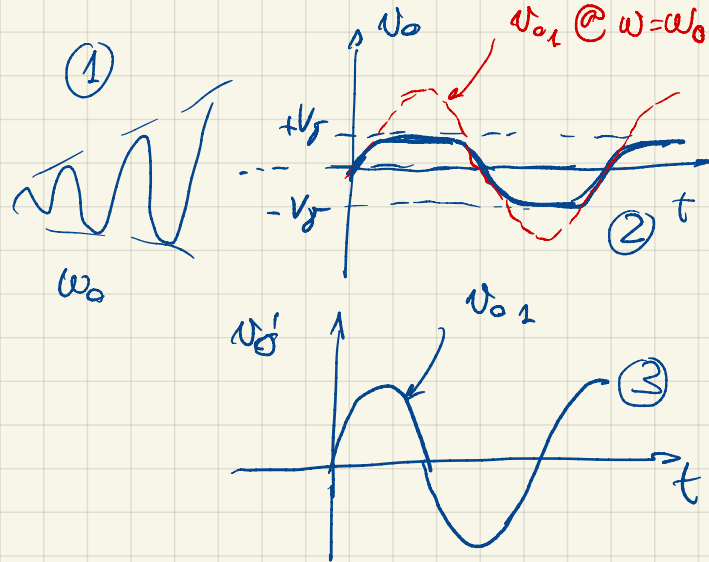
NOW LINEAR NETWORK REDUCES THE CURRENT GAIN ANY TIME  $v_o(t)$  GETS CLOSE TO  $\pm V_f$  (THE DIODE FORWARD VOLTAGE DROP)



THANKS TO THE SELECTIVITY OF THE RESONANT  $\beta$ -NETWORK  $v_o' \approx v_o$  THE FUNDAMENTAL HARMONIC COMPONENT OF  $v_o$

ANOTHER WAY IS TO MAKE  $R_2$  A PTC RESISTOR. A SIMPLE EXAMPLE OF PTC RESISTOR IS A LIGHT BULB. REPLACING  $R_2$  WITH A PTC AGAIN STABILIZES THE AMPLITUDE

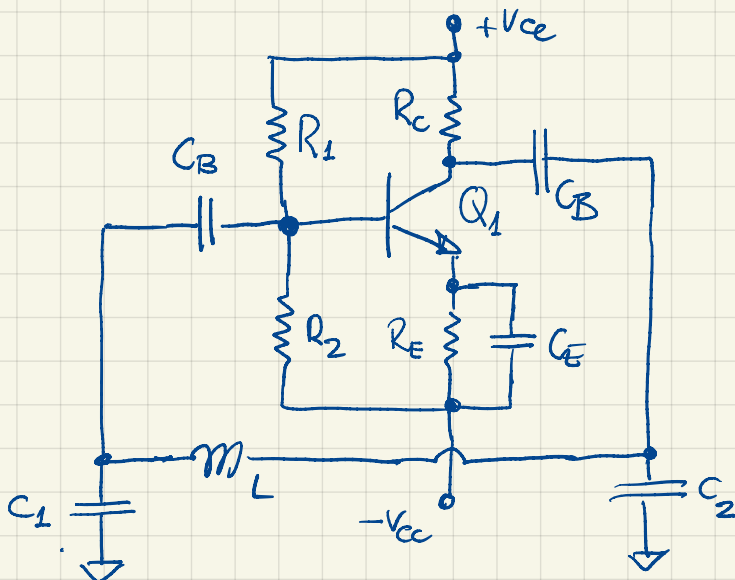A SINUSOIDAL OSCILLATOR CAN BE MADE ALSO USING A SIMPLE C-E (OR C-S) AMPLIFIER.




COLPITTS OSCILLATOR (COMMON EMITTER BASED)

typ: @  $\omega = \omega_0$


(1)  $C_L$  AND  $C_B$  ARE PRACTICALLY SHORTED

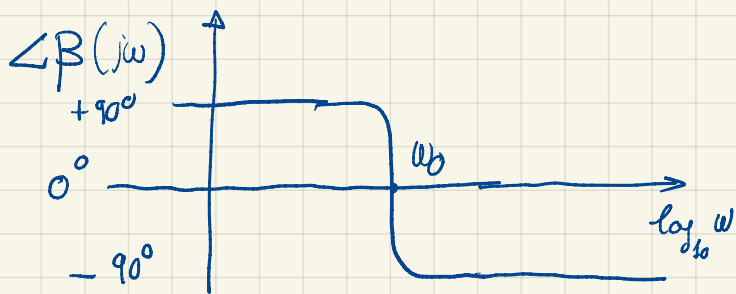(2)  $\omega_0 \ll \omega_T$  SO THAT

$C_{RE}$  AND  $C_{EL}$  ARE PRACTICALLY OPEN



THE  $\beta$ -NETWORK

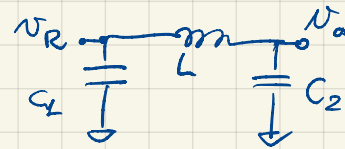

IS "SELECTIVE", ITS PHASE IS EQUAL TO  $0^\circ$  AT  $\omega = \omega_0$  BUT

PHASE VARIATION IS VERY "FAST". A SIGNAL WITH FREQUENCY DIFFERENT FROM  $\omega_0$  (EVEN BY A LITTLE AMOUNT) WILL NOT MEET BARKHAUSEN CONDITIONS AND WILL NOT PROPAGATE AROUND THE LOOP

SELECTIVITY  $\Rightarrow$  THE OSCILLATION FREQUENCY WILL BE VERY STABLE