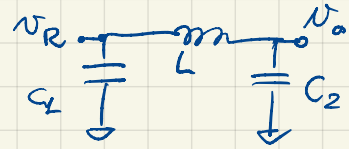



THE β -NETWORK



IS "SELECTIVE", ITS PHASE IS EQUAL TO 0° AT $\omega = \omega_0$ BUT

PHASE VARIATION IS VERY "FAST". A SIGNAL WITH FREQUENCY DIFFERENT FROM ω_0 (EVEN BY A LITTLE AMOUNT) WILL NOT MEET BARKHAUSEN CONDITIONS AND WILL NOT PROPAGATE AROUND THE LOOP

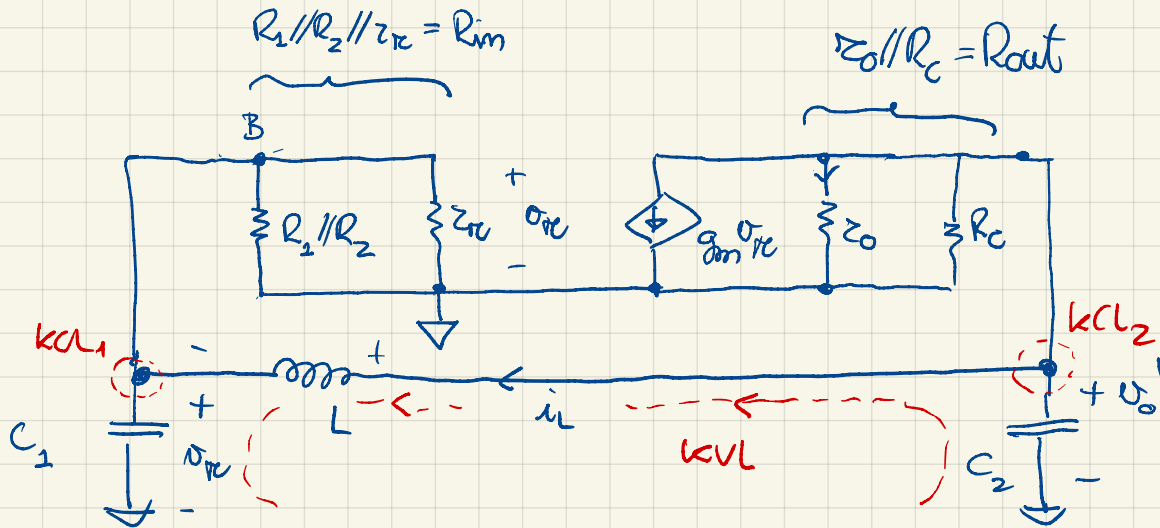SELECTIVITY \Rightarrow THE OSCILLATION FREQUENCY WILL BE VERY STABLE



$$\begin{cases} i_L = v_{be} \cdot sC_1 + v_{be} \cdot \frac{1}{R_{in}} = v_{be} \left(sC_1 + \frac{1}{R_{in}} \right) & \text{KCL}_1 \\ v_o' = sL i_L + v_{be} = v_{be} \left[1 + sL \left(sC_1 + \frac{1}{R_{in}} \right) \right] & \text{KVL} \\ v_o' = -\frac{1}{sC_2} \left(i_L + g_m v_{be} + \frac{v_o'}{R_{out}} \right) & \text{KCL}_2 \end{cases}$$

$$v_o' \cdot \left(1 + \frac{1}{sC_2 R_{out}} \right) = -\frac{v_{be}}{sC_2} \left(g_m + sC_1 + \frac{1}{R_{in}} \right)$$

$$v_o' = -\frac{v_{be}}{sC_2} \left(g_m + \frac{1}{R_{in}} + sC_1 \right) \cdot \frac{sC_2 R_{out}}{1 + sC_2 R_{out}}$$

$$\text{Hyp: } \omega_0 \gg \frac{1}{R_{out} C_2} \Rightarrow \frac{sC_2 R_{out}}{1 + sC_2 R_{out}} \approx 1$$

$$U_{TH} \left[1 + sL \left(sC_1 + \frac{1}{R_{im}} \right) \right] = - \frac{U_H}{sC_2} \left(g_m + \frac{1}{R_{im}} + sC_1 \right)$$

$$U_{TH} \left[1 + s^2 LC_1 + s \frac{L}{R_{im}} + \frac{g_m}{sC_2} + \frac{1}{R_{im} sC_2} + \frac{C_1}{C_2} \right] = 0 \quad \leftarrow$$

TWO SOLUTIONS

o $U_{TH} = 0 \Rightarrow$ THE CIRCUIT IS "TURNED OFF" \Rightarrow NOT INTERESTING

$U_{TH} \neq 0$ THE EQUATION IS EQUIVALENT TO

$$s R_{im} C_2 + s^3 R_{im} L C_1 C_2 + s^2 L C_2 + g_m R_{im} + 1 + s C_1 R_{im} = 0$$

$$s = j\omega_0 \Rightarrow$$

$$\begin{cases} \text{Re}(\) = -\omega_0^2 L C_2 + 1 + g_m R_{im} \stackrel{!}{=} 0 \Leftrightarrow |T(\omega_0)| = 1 \\ \text{Im}(\) = -\omega_0^3 R_{im} L C_1 C_2 + \omega_0 R_{im} (C_1 + C_2) \stackrel{!}{=} 0 \Leftrightarrow \angle T(\omega_0) = 2k\pi \end{cases}$$

FROM THE SECOND

$$\omega_0 = \sqrt{\frac{C_1 + C_2}{L C_1 C_2}} = \sqrt{\frac{1}{L C_{eq}}} \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2} \quad \text{SERIES OF } C_1 \text{ AND } C_2$$

REARANGING IN THE FIRST

$$-\frac{C_1 + C_2}{L C_1 C_2} \cdot \frac{L C_2}{2} + 1 + g_m R_{im} = 0 \Leftrightarrow \boxed{g_m R_{im} = \frac{C_2}{C_1}}$$

ω_0 IS THE OSCILLATION FREQUENCY

THE OSCILLATION WILL START IF $g_m R_{im} > \frac{C_2}{C_1} \quad ! \quad \leftarrow$

TO DESIGN THE CIRCUIT IT IS TYPICALLY EASIER TO CHOOSE

1. $C_1 \ll C_2 \Rightarrow \omega_0 \approx \sqrt{\frac{1}{LC_1}} \Rightarrow \omega_0 \text{ BE CHOSEN } \ll \omega_T$


2. $\omega_0 \gg \frac{1}{R_{out}C_2} \Rightarrow \text{WE CAN FIND } C_2$

10^7
 $f_0 \approx 1 \text{ MHz}$

$\propto 10^3 \Omega \Rightarrow C_2 \propto 10^{-9} \text{ F} \Rightarrow C_1 \approx 100 \text{ pF} \Rightarrow L \approx 100 \mu\text{H}$

— • — • — • —

EXERCISE # 1

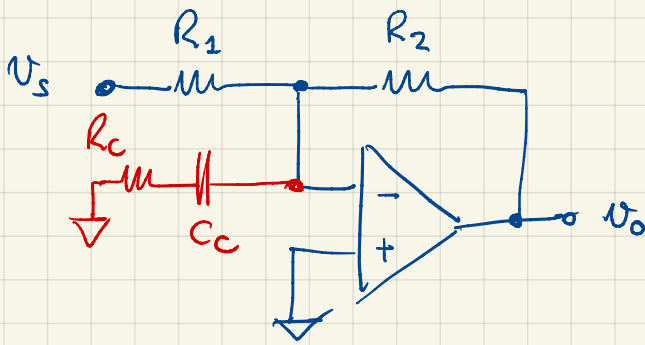


$$A_d(s) = \frac{10^5}{\left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{10^5}\right)}$$

$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

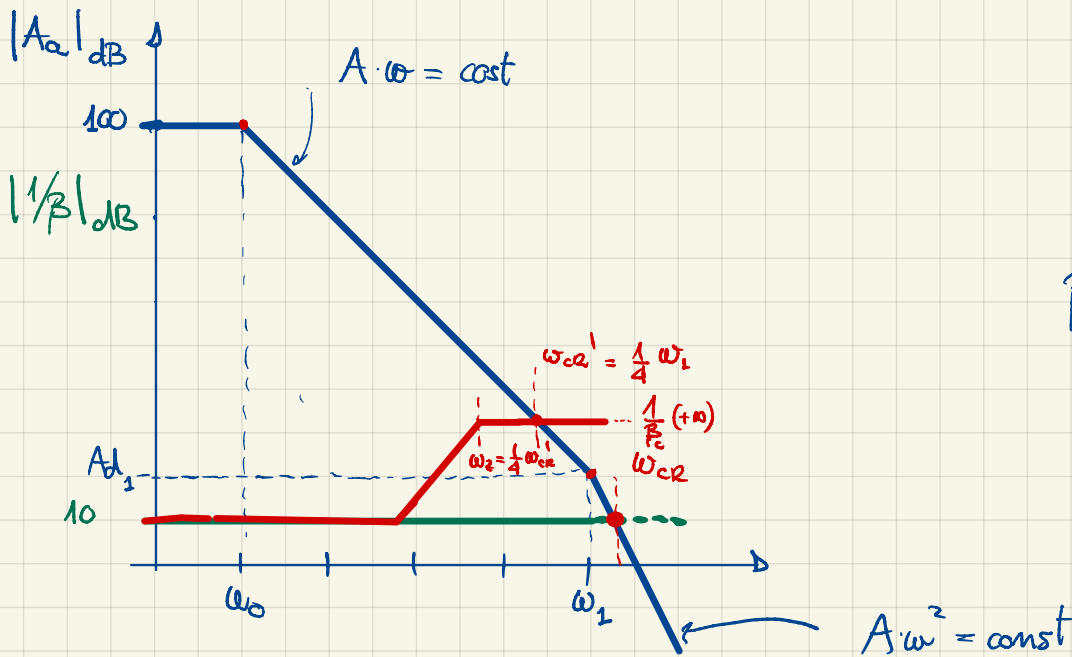1. PHASE MARGIN BEFORE COMPENSATION
2. $R_c - C_c$ TO HAVE 60° MINIMUM PHASE MARGIN



$$A_d(s) = A_d(s)$$

$$\omega_0 = 10 \text{ rad/s}$$

$$\omega_1 = 10^5 \text{ rad/s}$$

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{1}{3}$$

1. PM BEFORE COMPENSATION

$$A_{d0} \cdot \omega_0 = A_{d1} \cdot \omega_1 \Rightarrow A_{d1} = \frac{A_{d0} \omega_0}{\omega_1}$$

$$\frac{1}{\beta} \cdot \omega_{cr}^2 = A_{d1} \cdot \omega_1^2 \Rightarrow \omega_{cr} = \sqrt{\beta A_{d0} \omega_0 \omega_1} = 1.82 \cdot 10^5 \text{ rad/s}$$

$$PM = 180^\circ - \arctan\left(\frac{\omega_{cr}}{\omega_0}\right) - \arctan\left(\frac{\omega_{cr}}{\omega_1}\right) \approx 28^\circ$$

$$2. \quad \beta_c(s) = \frac{R_1 // Z_c}{R_1 // Z_c + R_2} \xrightarrow{s \rightarrow +\infty} \frac{R_1 // R_c}{R_2 + R_1 // R_c}$$

$$\frac{1}{R_c}(+\infty) = 1 + \frac{R_2}{R_1 // R_c} = 40 \rightarrow R_c$$

$$\frac{1}{R_c}(+\infty) \cdot \omega_{cr}' = A_{d\phi} \cdot \omega_0 \quad \omega_{cr}' = \frac{\omega_z}{4} = 2.5 \cdot 10^4$$

$$\frac{1}{R_c}(+\infty) = \frac{A_{d\phi} \omega_0}{\omega_{cr}'} = \frac{10^6}{2.5 \cdot 10^4} = 40$$

TO FIND R_c


$$\frac{R_2}{R_1 // R_c} = 39 \rightarrow R_1 // R_c = R_2 / 39 \rightarrow$$

$$\rightarrow \frac{1}{R_2} + \frac{1}{R_c} = \frac{39}{R_2} \rightarrow \frac{1}{R_c} = \frac{39}{R_2} - \frac{1}{R_2} \rightarrow R_c = 270 \Omega$$

THEN WE KNOW $\omega_z = \frac{1}{R_c C_c} = \frac{\omega_{cr}'}{4} \Rightarrow C_c = \frac{4}{R_c \cdot \omega_{cr}'} \approx 592 \text{ pF}$

$$\varphi_{M'} \approx \varphi_M + \omega^0 = 80^\circ \Rightarrow \text{LIKE A FIRST ORDER CLOSED LOOP SYSTEM}$$

EXERCISE # 2

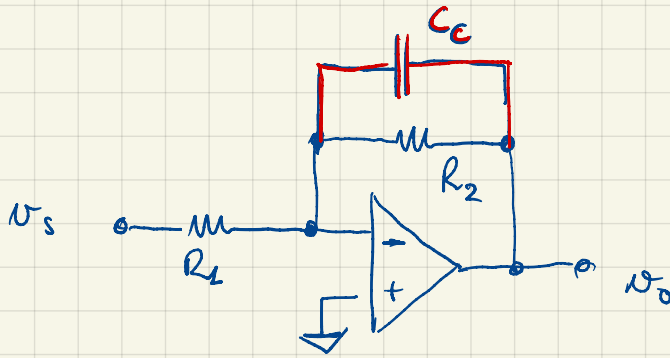

$$\rightarrow A_d(s) = \frac{10^5}{\left(1 + \frac{s}{\omega_0}\right) \left(1 + \frac{s}{\omega_1}\right)}$$


$$\omega_0 = 10^2 \text{ rad/s}$$

$$\omega_1 = 5 \cdot 10^3 \text{ rad/s}$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 33 \text{ k}\Omega$$

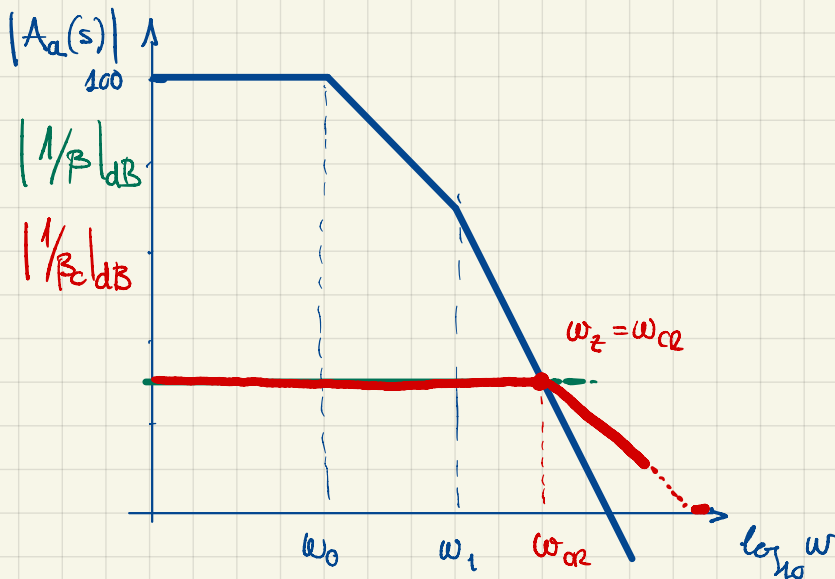1. PHASE MARGIN WITHOUT C_c
2. C_c TO HAVE THE SAME ω_{CR}
3. NEW PHASE MARGIN



$$A_d(s) = A_d(s)$$

$$\frac{1}{\beta} = 1 + \frac{R_2}{R_1} = 34$$

1. AS IN THE PREVIOUS CASE

$$\omega_{CR} = \sqrt{\beta A_{d0} \omega_0 \omega_1} = 54 \cdot 10^3 \text{ rad/s}$$

$$PM = 180^\circ - \text{atan}\left(\frac{\omega_{CR}}{\omega_0}\right) - \text{atan}\left(\frac{\omega_{CR}}{\omega_1}\right) \approx 7.6^\circ \ll 45^\circ$$

- 2.

$$\beta_c(s) = \frac{R_1}{R_1 + \frac{R_2}{1 + sC_c R_2}} = \frac{R_1 (1 + sC_c R_2)}{R_1 + R_2 + sC_c R_1 R_2} = \frac{R_1}{R_1 + R_2} \cdot \frac{1 + sC_c R_2}{1 + sC_c R_1 R_2 / (R_1 + R_2)}$$

$$\omega_z = \frac{1}{R_2 C_C} = \omega_{cr} \Rightarrow C_C = \frac{1}{R_2 \cdot \omega_{cr}} = 0.8 \text{ mF}$$

3. $PM^{\text{neu}} = PM + 45^\circ = 52.6^\circ$