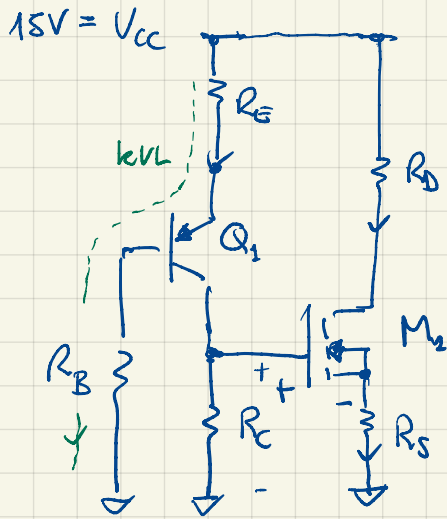


13-1-2023

BIAS POINT ANALYSIS



$$R_E = 1.2 \text{ k}\Omega$$

$$\beta_{F1} = 100 = \beta_0$$

$$R_D = 6.8 \text{ k}\Omega$$

$$V_{BE1} = -0.7 \text{ V}$$

$$R_S = 1 \text{ k}\Omega$$

$$\bar{I}_{DSS} = 0.2 \text{ mA}$$

$$R_C = 10 \text{ k}\Omega$$

$$V_t = 2 \text{ V}$$

$$R_B = 1.8 \text{ M}\Omega$$

KVL: 
$$V_{CC} = R_E \cdot I_{B1} (\beta_{F1} + 1) - V_{BE1} + R_B \cdot I_{B1}$$

$$I_{B1} = \frac{V_{CC} + V_{BE1}}{R_B + R_E (\beta_{F1} + 1)} = \frac{14.3}{1.8 \cdot 10^6 + 1.2 \cdot (101) \cdot 10^3} \approx 7.44 \mu\text{A}$$

$$I_{C1} = \beta_{F1} \cdot I_{B1} = 0.74 \text{ mA}$$

$$V_{CE} = -V_{CC} + R_C \cdot I_{C1} + R_E \cdot I_{B1} (\beta_{F1} + 1) \approx -6.65 \text{ V}$$

$$V_{C1} = R_C \cdot I_{C1} = 7.44 \text{ V}$$

$$\begin{cases} V_{GS1} = V_{G1} - R_S \cdot I_D \\ I_D = I_{DSS} \left( \frac{V_{GS}}{V_t} - 1 \right)^2 \end{cases}$$

$$V_{G1} - R_S I_{DSS} \left[ \left( \frac{V_{GS}}{V_t} \right)^2 + 1 - 2 \frac{V_{GS}}{V_t} \right] - V_{GS1} = 0$$

$$a = \frac{R_S I_{DSS}}{V_t^2} = 0.05$$

$$c = R_S I_{DSS} - V_{G1} = -7.24$$

$$b = \frac{2R_S I_{DSS}}{V_t} - 1 = -0.8$$

$$V_{GS_{1,2}} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \begin{cases} +6.45 \text{ V} > V_t \\ \dots < V_t \end{cases}$$

$$I_D = I_{DSS} \left( \frac{V_{GS_1}}{V_t} - 1 \right)^2 \approx 1 \text{ mA}$$

$$V_{CE_1} < -0.2 \text{ V} \quad (V_{CE_{SAT}} \text{ pmp}) \quad \text{F.A.R. OR.}$$

$$V_{DS} = V_{CC} - (R_D + R_S) I_D = 7.27 \text{ V} > V_{GS} - V_t$$

$\Rightarrow Q_2$  IS IN THE SATURATION REGION

$$g_{m1} = \frac{I_{C1}}{V_T} = 0.03 \text{ } \Omega^{-1} = 30 \text{ mS}$$


$$g_{m2} = \frac{2}{V_t} \sqrt{I_D I_{DSS}} = 0.45 \text{ mS}$$

$$Z_{i1} = \frac{R_{o1}}{g_{m1}} = 3.36 \text{ k}\Omega$$

SMALL SIGNAL ANALYSIS

TOPOLOGY: VOLTAGE AMPLIFIER

$\beta$  - NETWORK

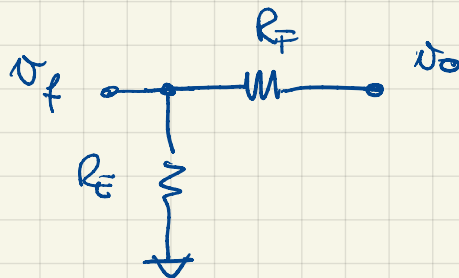


$$\beta = \frac{R_E}{R_E + R_F} = 0.353$$

$$R_{if} = R_E \parallel R_F$$

$$R_{of} = R_E + R_F$$

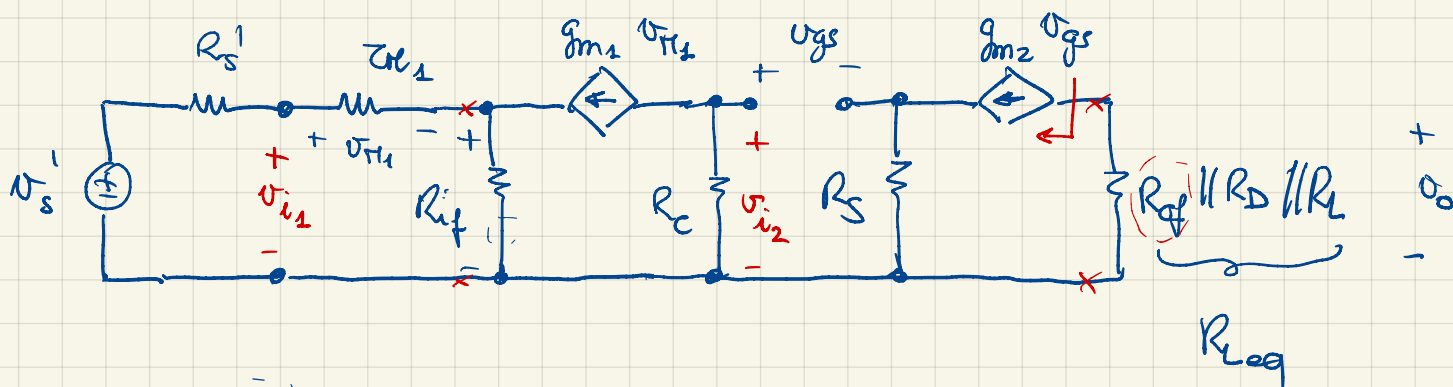SMALL SIGNAL EQUIVALENT CIRCUIT  $\beta = \infty$



$$v_s' = \left( \frac{R_B}{R_S + R_B} \right) v_s$$

$$R_{eq} = R_D \parallel R_L \parallel R_C$$

$$R_s' = R_S \parallel R_B$$

$$A_2 = \frac{v_o}{v_{i2}} = - \frac{g_{m2} R_{eq}}{1 + g_{m2} R_S} = - 0.827$$

$$A_1 = \frac{v_{o1}}{v_{i1}} = \frac{v_{i2}}{v_{i1}} = - \frac{\beta_0 R_C}{r_{i2} + (\beta_0 + 1) R_{if}} = - 10.9$$

$$k_s' = \frac{v_{i1}}{v_s} = \frac{r_{i2} + (\beta_0 + 1) R_{if}}{R_s' + r_{i2} + (\beta_0 + 1) R_{if}} \approx 1$$

$$A_a = k_s' \cdot A_1 \cdot A_2 = + 6.84$$

$$A_F = \frac{A_a}{1 + \beta A_a} = + 2 \quad T \approx 2. \dots$$

$$A_{v'} = \frac{v_o}{v_s} = \underbrace{\frac{v_o}{v_s'}}_{A_F} \cdot \frac{v_s'}{v_s} = 1.99$$



$$R_{out} = R_{eq} \rightarrow R_{out_F} = \frac{R_{eq}}{1 + \beta A_a} = 596 \Omega$$

$$R_{out} = \frac{1}{\frac{1}{R_{outF}} - \frac{1}{R}} = 615 \Omega$$

$f_L$  SCRC METHOD

$$R_{Cg} = R_g + R_B \parallel \left[ \alpha_{v2} + (\beta_{o1} + 1) R_{if} \right] = 88 \text{ k}\Omega$$
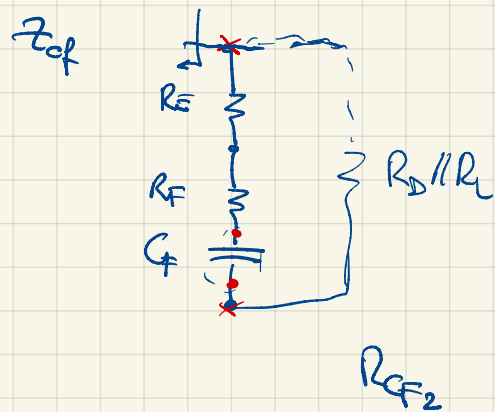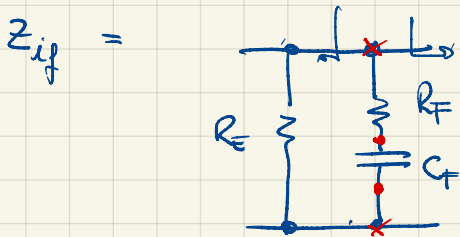
$$R_{Cc} = R_L + R_D \parallel R_{of} = 22.3 \text{ k}\Omega$$



$R_{CF1}$


$$+ \dots \underbrace{\frac{1}{2\pi C_F R_{CF1}} + \frac{1}{2\pi C_F R_{CF2}} + \dots}$$

$$\frac{1}{2\pi C_F} \cdot \left( \frac{1}{R_{CF1}} + \frac{1}{R_{CF2}} \right) = \frac{1}{2\pi C_F} \cdot \frac{1}{R_{CF1} \parallel R_{CF2}}$$

$$R_{CF1} \approx R_F + R_E \parallel \frac{1}{g_{m1}} \left( = R_F + R_E \parallel \frac{\alpha_{v2} + R_S'}{\beta_{o1} + 1} \right) = 2.32 \text{ k}\Omega$$

$$R_{CF2} = R_D \parallel R_L + (R_E + R_F) = 8.47 \text{ k}\Omega$$
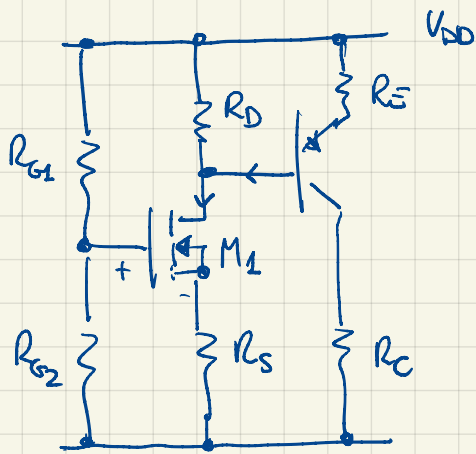
$$f_L = \frac{1}{2\pi} \cdot \left( \frac{1}{1 + \beta A_{ol}} \right) \cdot \sum_i \frac{1}{R_i C_i} = \underline{57 \text{ Hz}}$$



$$V_{G1} = V_{DD} \cdot \frac{R_{G2}}{R_{G1} + R_{G2}}$$

$$A_a = 6$$

$$A_f = 4.66$$

$$A_{Vf} = 4.57$$

$$f_L \approx 324 \text{ Hz} !!$$

No EFFECT OF FEEDBACK



$$a = \frac{R_S I_{DSS}}{V_t^2}$$

$$b = \frac{2 R_S I_{DSS}}{V_t} - 1$$

$$c = -V_{G1} + R_S I_{DSS}$$

$$V_{GS} = \frac{-b + \sqrt{b^2 - 4ac}}{2a} = 4.16 \text{ V} > V_t = 3 \text{ V}$$
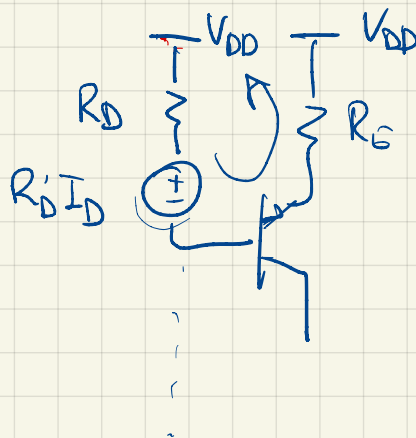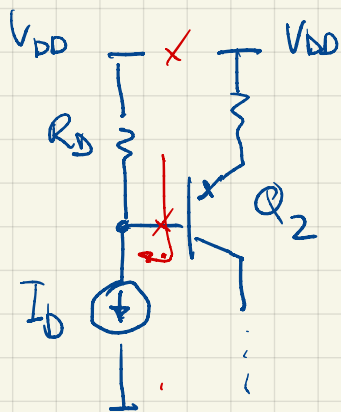
$$I_D = I_{DSS} \left( \frac{V_{GS}}{V_t} - 1 \right)^2 = 3.4 \text{ mA}$$



$$I_{B2} = \frac{R_D I_D + V_{BE2}}{R_D + R_E (\beta_{F2} + 1)} = 5.23 \mu\text{A}$$

$$I_C = \beta_{F2} I_{B2} = 0.52 \text{ mA}$$

$$V_{GS} = V_{DD} - R_S I_D - R_D (I_D - I_{B2}) = 6.8 \text{ V} > V_{GS} - V_t$$

$$V_{CE} = V_{DD} - R_C I_{C2} - R_E (\beta_{F2} + 1) I_{B2} = -2.61 \text{ V} < -0.2 \text{ V}$$

BOTH TRANSISTORS OPERATE IN THE LINEAR REGION.