



UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Oscilloscope analog front end


Lecture #3

Electronic measurements

Claudio Narduzzi, Alessandro Pozzebon



The oscilloscope

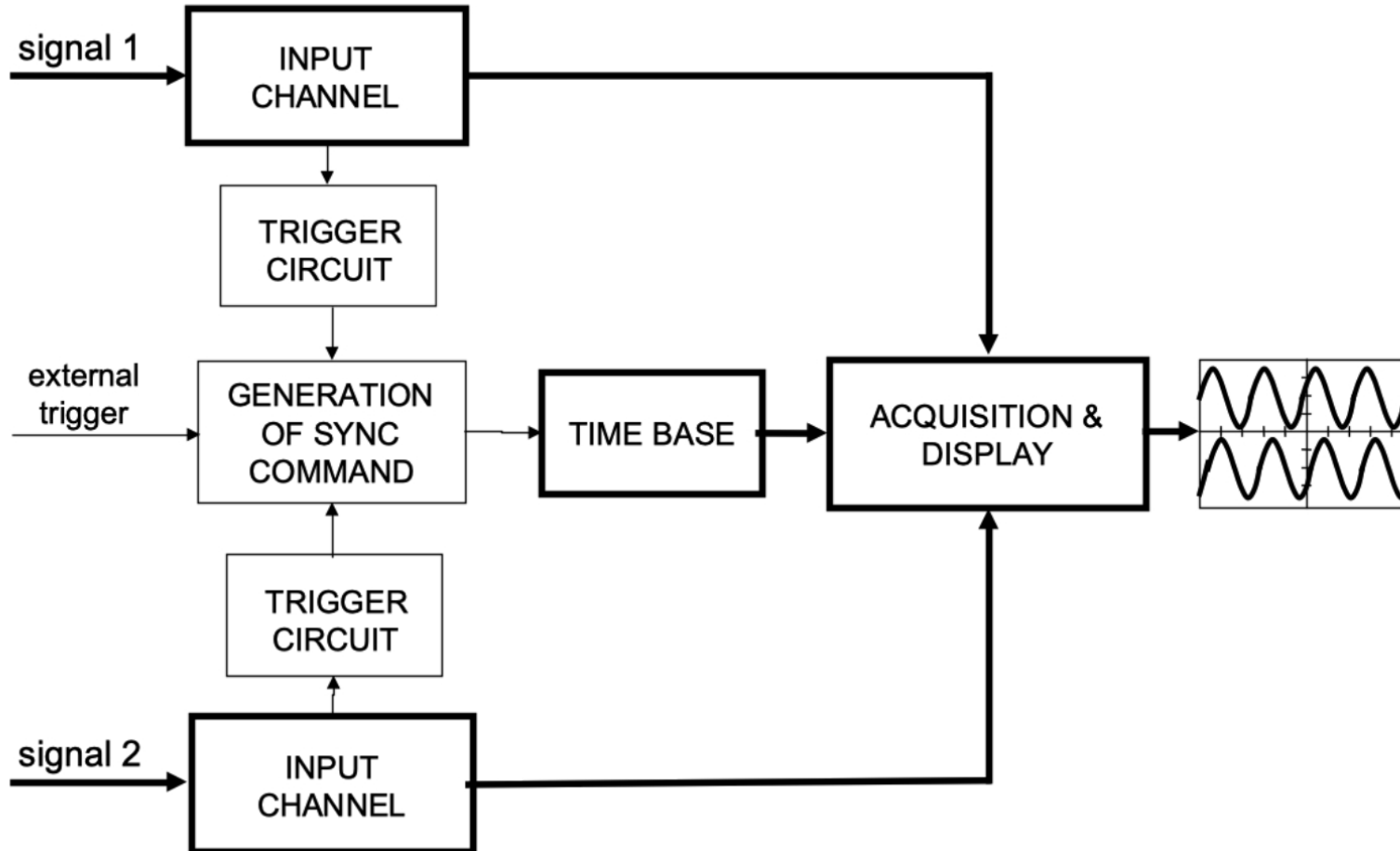




Input channel functions

- **Amplify or attenuate** the signal
- Realize a stable **input impedance**
- Provide a choice of **coupling modes**



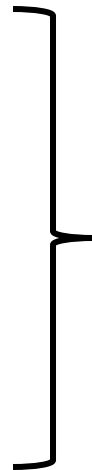- Variable-gain amplifiers
- Attenuators
- Filters
- Coupling circuits




Configured through the processors



Signal conditioning



Input channel functions

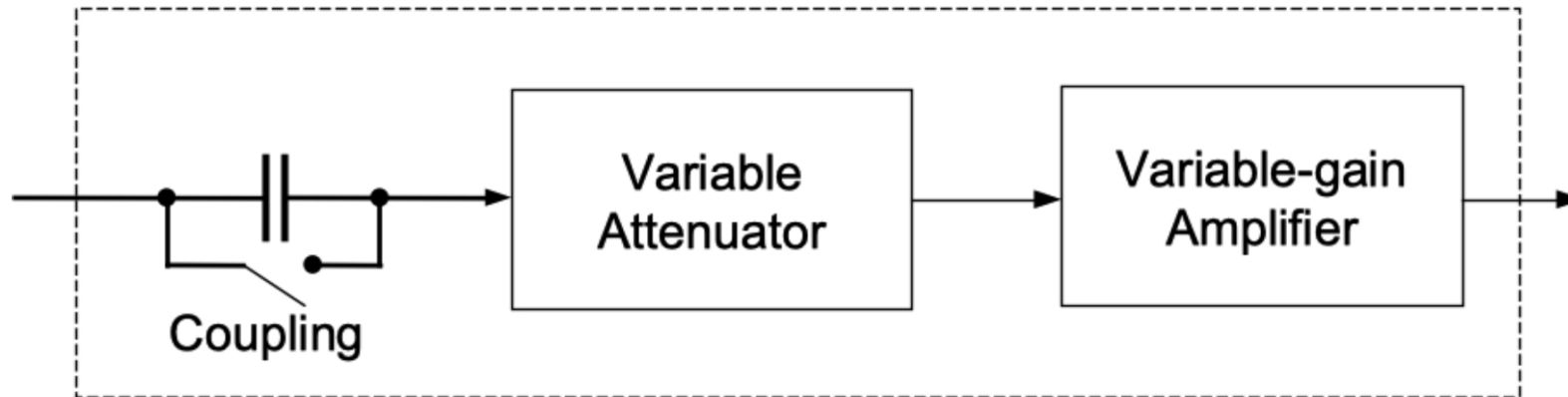


- 2-4 channels
- **Simultaneous acquisition** of different signals
- **Common time reference**
- **Separate vertical scale settings**



Input channel model

- Voltage controlled generator

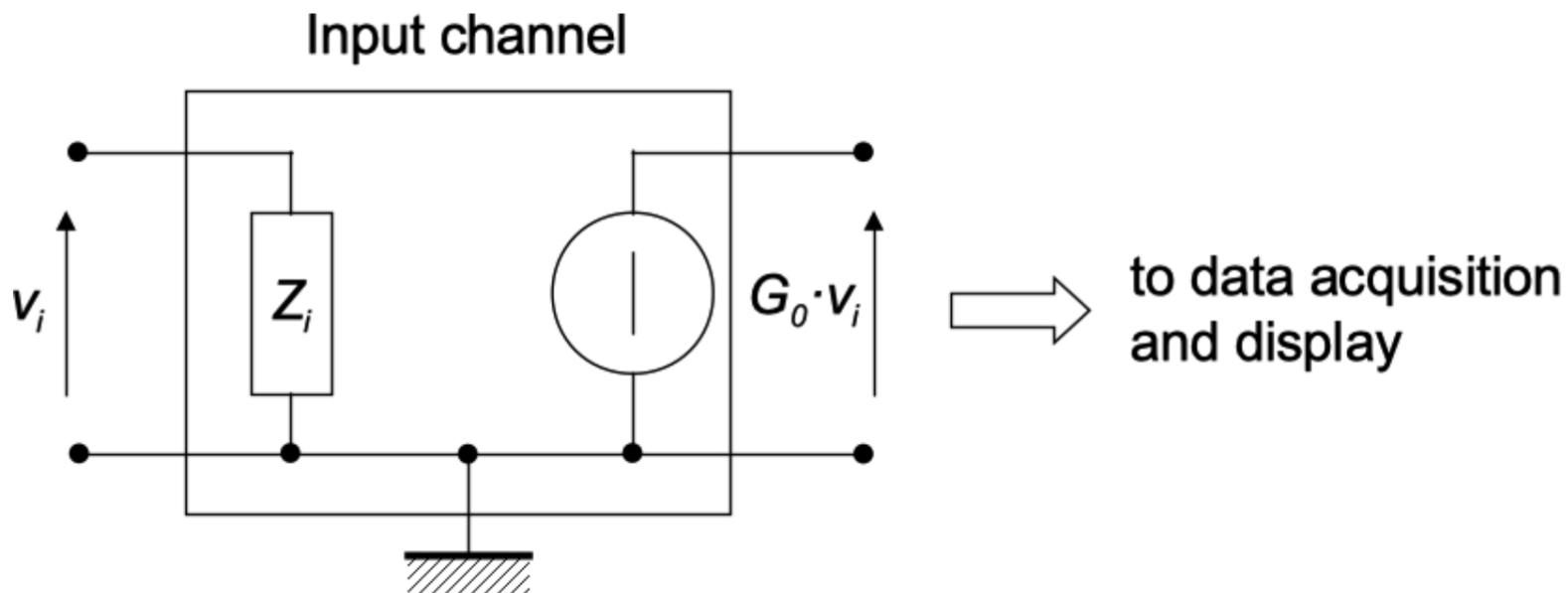

- Input impedance Z_i
- Frequency response $G(f)$
- Static gain $G_0 = G(0)$
- Calibrated vertical scale factor $1/G_0$



Calibration through comparison
with **known DC voltage levels**



Input impedance

- Input impedance Z_i as large as possible
- Parallel of a large resistance R_i and a small capacitance C_i
- $R_i = 10 \text{ M}\Omega$, $C_i = 10 - 20 \text{ pF}$
- Low frequencies $\Rightarrow |Z_i| \cong R_i \Rightarrow$ Negligible loading effect
- High frequencies \Rightarrow Capacitive reactance \Rightarrow impedance drop

$$Z_i = R_i \frac{1}{1 + j\omega R_i C_i}$$



Input impedance

$$R_i = 1 \text{ M}\Omega \text{ and } C_i = 15 \text{ pF}$$


| f | R_i | $ X_i $ | $ Z_i $ |
|---------|--------------|---------------|----------------|
| 0 | 1 M Ω | ∞ | 1 M Ω |
| 1 kHz | 1 M Ω | 10 M Ω | 900 k Ω |
| 1 MHz | 1 M Ω | 10 k Ω | 10 k Ω |
| 10 MHz | 1 M Ω | 1 k Ω | 1 k Ω |
| 100 MHz | 1 M Ω | 100 Ω | 100 Ω |

- **Lower input impedance** \Rightarrow larger current absorption at higher frequencies
- **High input impedance:** limited loading effect
- **50 Ω input impedance:** matched impedance \Rightarrow wavelength comparable to the physical size of circuits
 \Downarrow
avoid reflections



Coupling

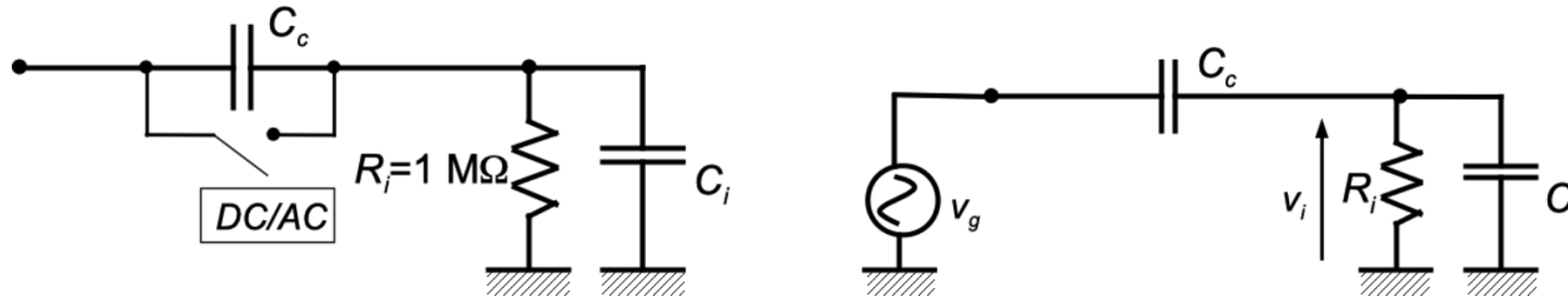- **Direct-current (DC) coupling:** the whole signal, including its DC component, is acquired
- **Alternating-current (AC) coupling:** only the alternating is acquired



$$V_i(s) = V_g(s) \cdot \frac{j\omega R_i C_c}{1 + j\omega R_i (C_c + C_i)}$$


- **High pass filter**
- -3 dB cut-off frequency ~ 10 Hz
- C_c in the order of some tens of nF $\Rightarrow C_c \gg C_i$



Sensitivity and noise

- **Thermal noise:** random motion of electrons
- Power spectral density kT [W/Hz] (k Boltzmann constant = 1.38×10^{-23} J/K)

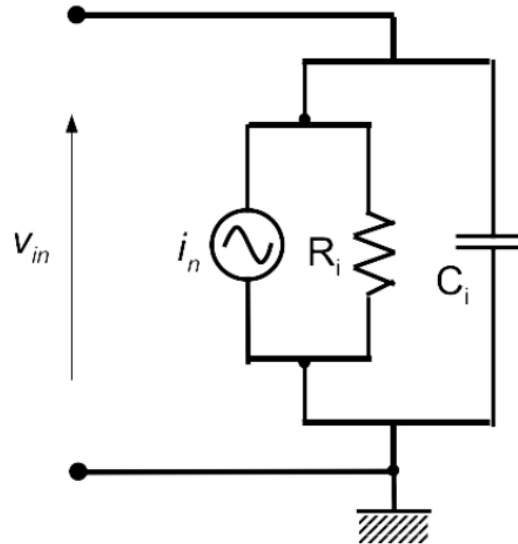- Noise power is generated by an equivalent current source i_n in parallel to the “noiseless” input resistance R_{in}




$$S_{nn}(f) = \frac{4kT}{R_i} A^2 / \text{Hz}$$

- **Noise voltage** v_{in} is produced by the noise current i_n flowing through the input impedance Z_i and is displayed as additive noise superposed on the measured signal



Sensitivity and noise

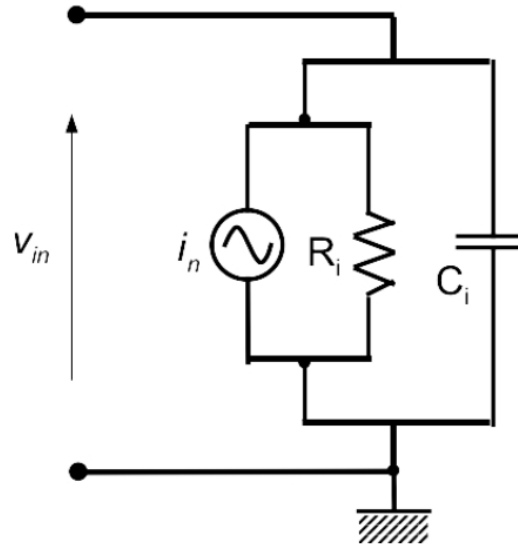- **Thermal noise:** random motion of electrons
- Power spectral density kT [W/Hz] (k Boltzmann constant = 1.38×10^{-23} J/K)



$$S_{nn}(f) = \frac{4kT}{R_i} A^2 / \text{Hz}$$

- **Input noise variance**

$$E[v_{in}^2] = \frac{4kT}{R_i} \cdot \frac{1}{2\pi} \int_0^{+\infty} \frac{R_i^2}{1 + \omega^2 (R_i C_i)^2} d\omega = 4kT \cdot \frac{1}{2\pi} \frac{\pi}{2R_i C_i}$$



Sensitivity and noise

- $v_{in(RMS)} = \sigma_n = \sqrt{\frac{kT}{C_i}}$
- Determined by the the equivalent noise of the input RC circuit
- **Smaller levels of C_i lead to higher levels of noise**
- $C_i = 10 \text{ pF}$ and $T = 300 \text{ K} \Rightarrow v_{in(RMS)} \cong 20 \mu V$
- **Signal-to-Noise Ratio (SNR)**
 - Uniform probability density function for signals within the input voltage range $\pm V_{FS} \Rightarrow \text{Variance } \sigma_S^2 = V_{FS}^2/3$
 - $SNR_{thermal} = \frac{V_{FS}^2}{3} \frac{C_i}{kT}$



Dynamic characteristics

- **Flatness:** maximum deviation of $|G(f)|$ from the DC value

$$\text{flatness} = \frac{\max_j |G(f) - G(0)|}{G(0)}$$


- **Non distortion conditions**
- Linear frequency response with:
 - **Constant magnitude**
 - **Linear phase (constant group delay)**



Dynamic characteristics: Step response


- Faithful waveform reproduction in the time domain
- **Step response:**
 - Shortest possible rise time
 - No overshoot
- Follow any voltage variation **avoiding the creation of artifacts**
- Linear system with Gaussian impulse response

$$g(t) = A \cdot e^{-(t-\tau_0)^2}$$

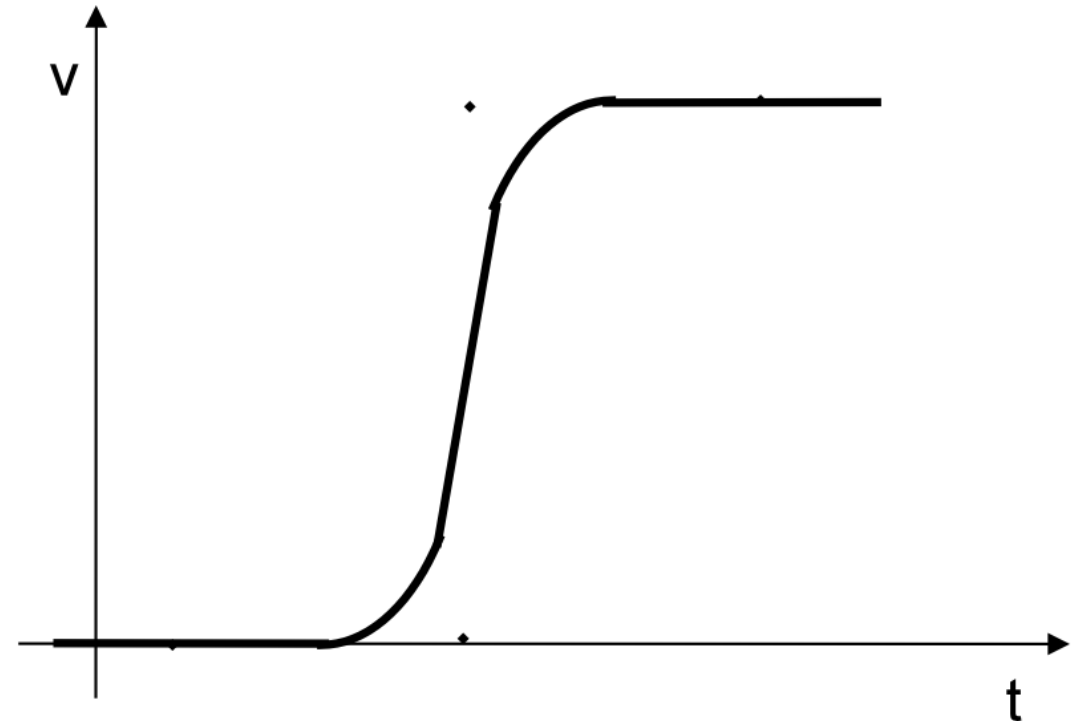



Dynamic characteristics: Step response

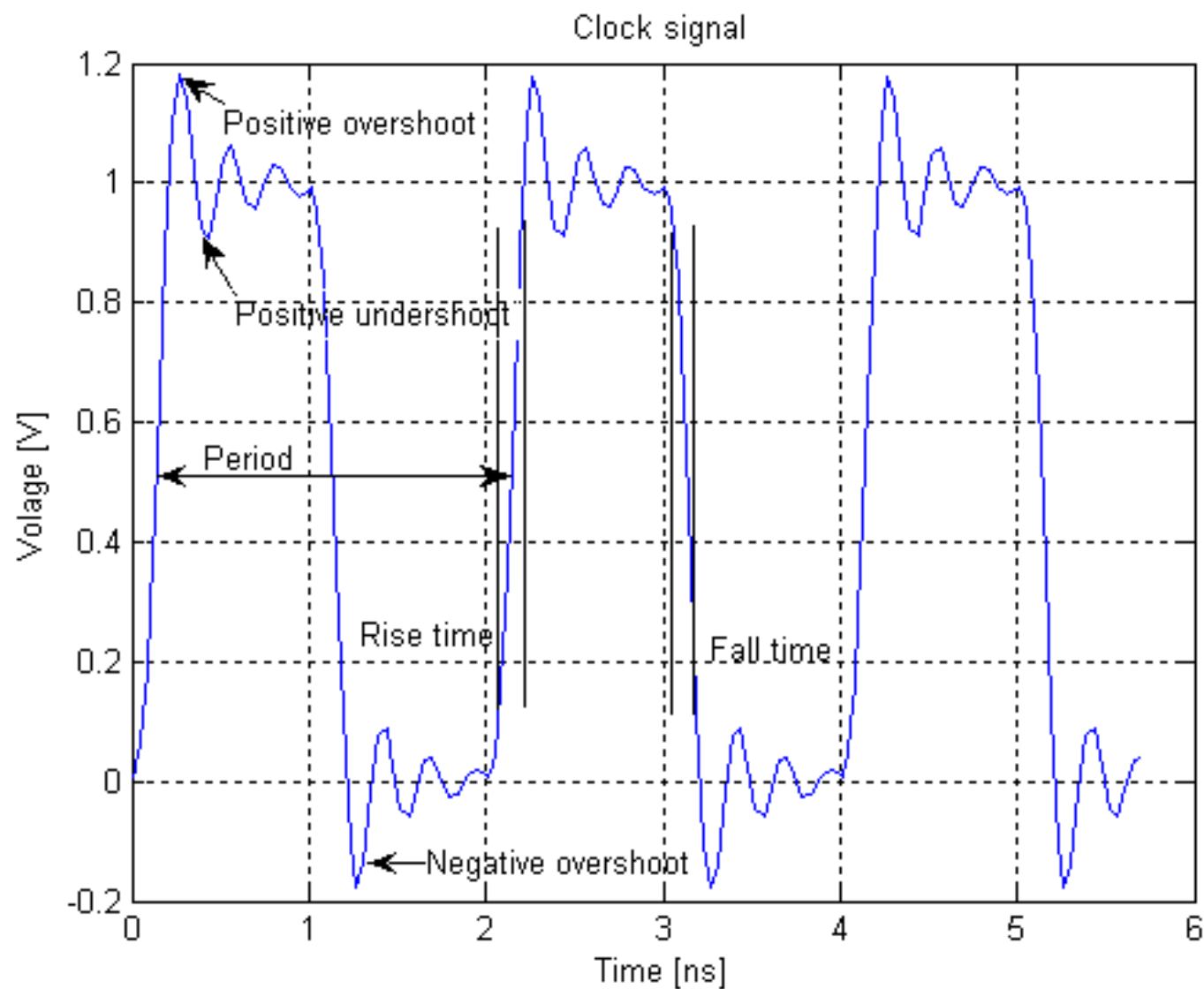



Dynamic characteristics:

Rise time

- Signals with sharp edges (**digital signals or clock signals**)
- Edge not distorted
 - **Significant high-frequency contributions**
 - **Instrument bandwidth limitations**
- **Rise time:** time required for the transition between two levels



Dynamic characteristics:

Rise time

- T_r : oscilloscope rise time
- T_v : visualized rise time
- T_s : signal rise time
- Relative deviation from T_s :

$$\frac{T_v - T_s}{T_s}$$
$$T_v \cong \sqrt{T_s^2 + T_r^2}$$


- To make the difference from T_v negligible, $T_r \ll T_s$



Dynamic characteristics: Rise time

$$\frac{T_r}{T_s}$$


$$\frac{T_v - T_s}{T_s}$$

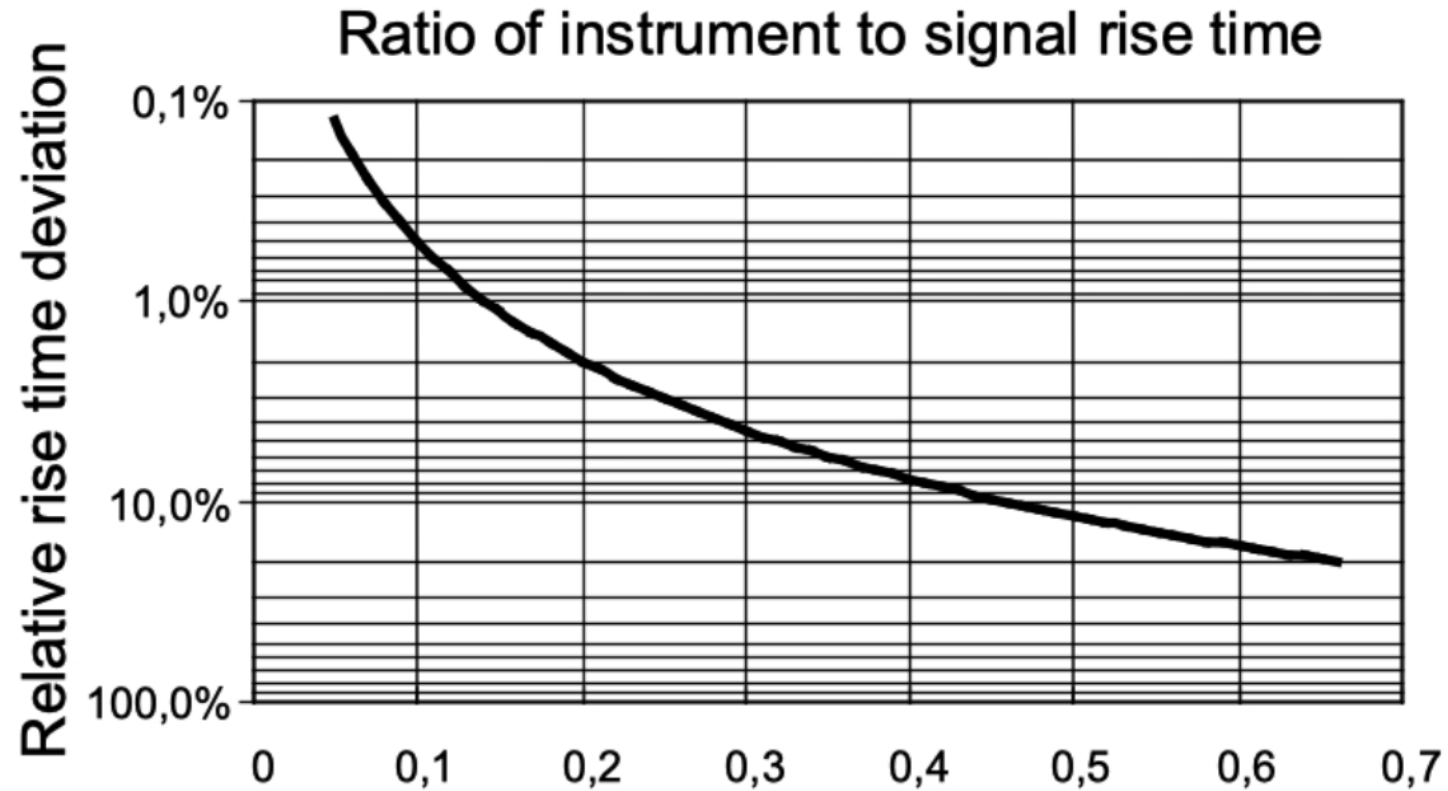



Frequency response

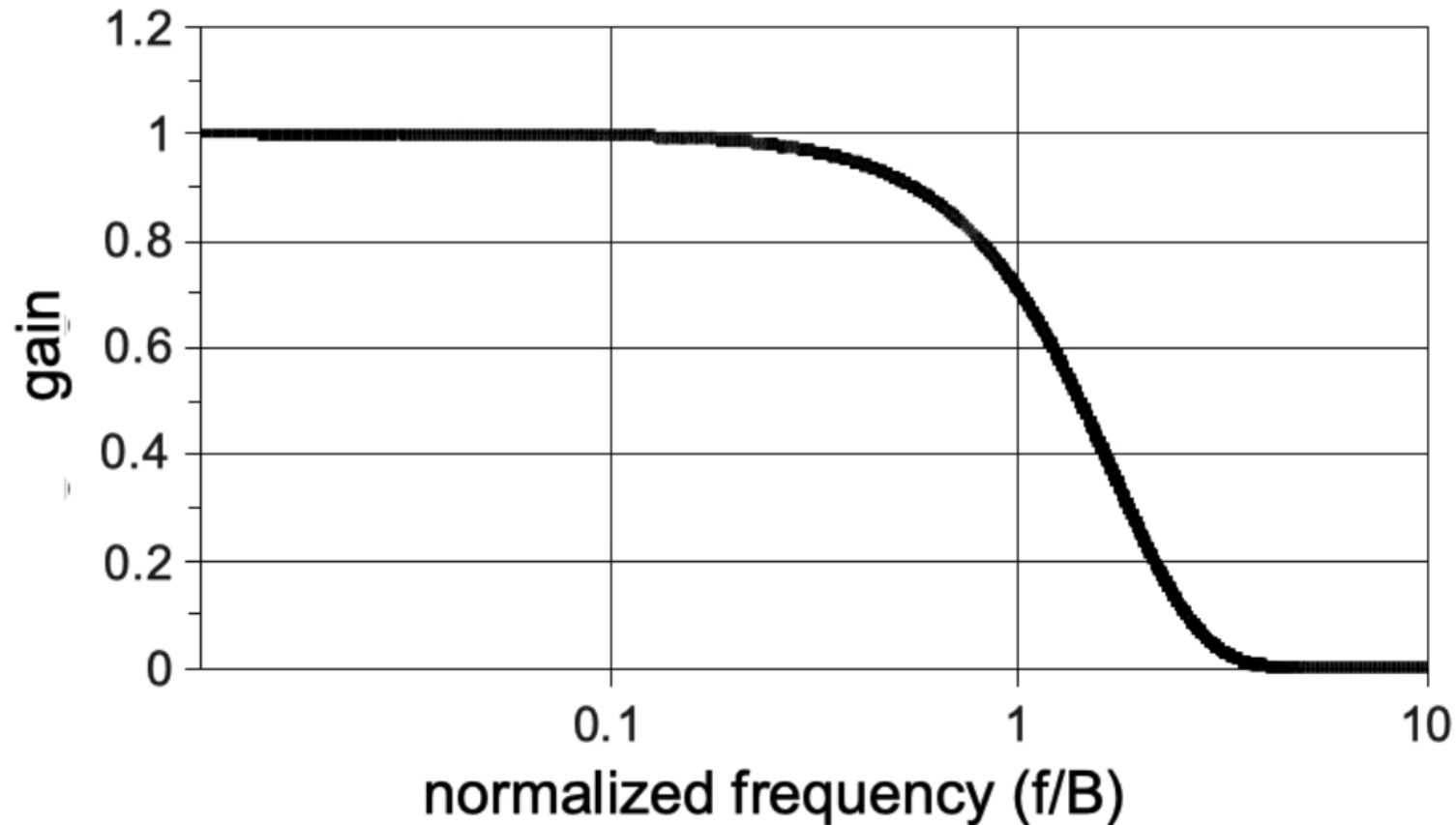- $B \Rightarrow$ -3 dB bandwidth \Rightarrow attenuation about 30%



$$T_r \cong \frac{0.35}{B}$$




Frequency response

- The frequency response may present some ripple \Rightarrow flatness
- Two parallel paths for **broad band amplification**
 - **DC-coupled** low-frequency
 - **AC-coupled** high-frequency (cross-over frequency around 1 kHz)
- Output noise **higher** for higher-gain circuits \rightarrow Different vertical scale factor, different noise level



Frequency response with AC coupling

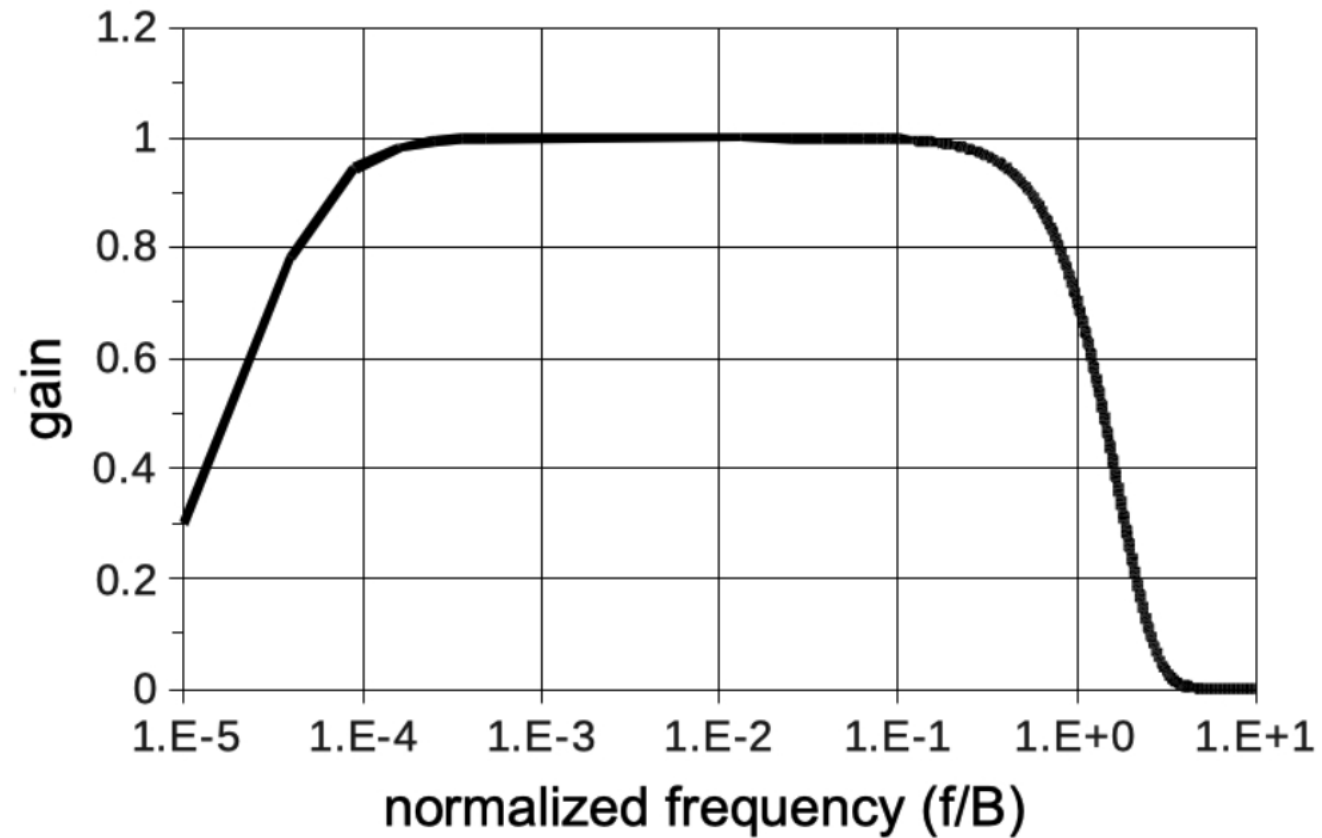




UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Oscilloscope probes





Oscilloscope probes

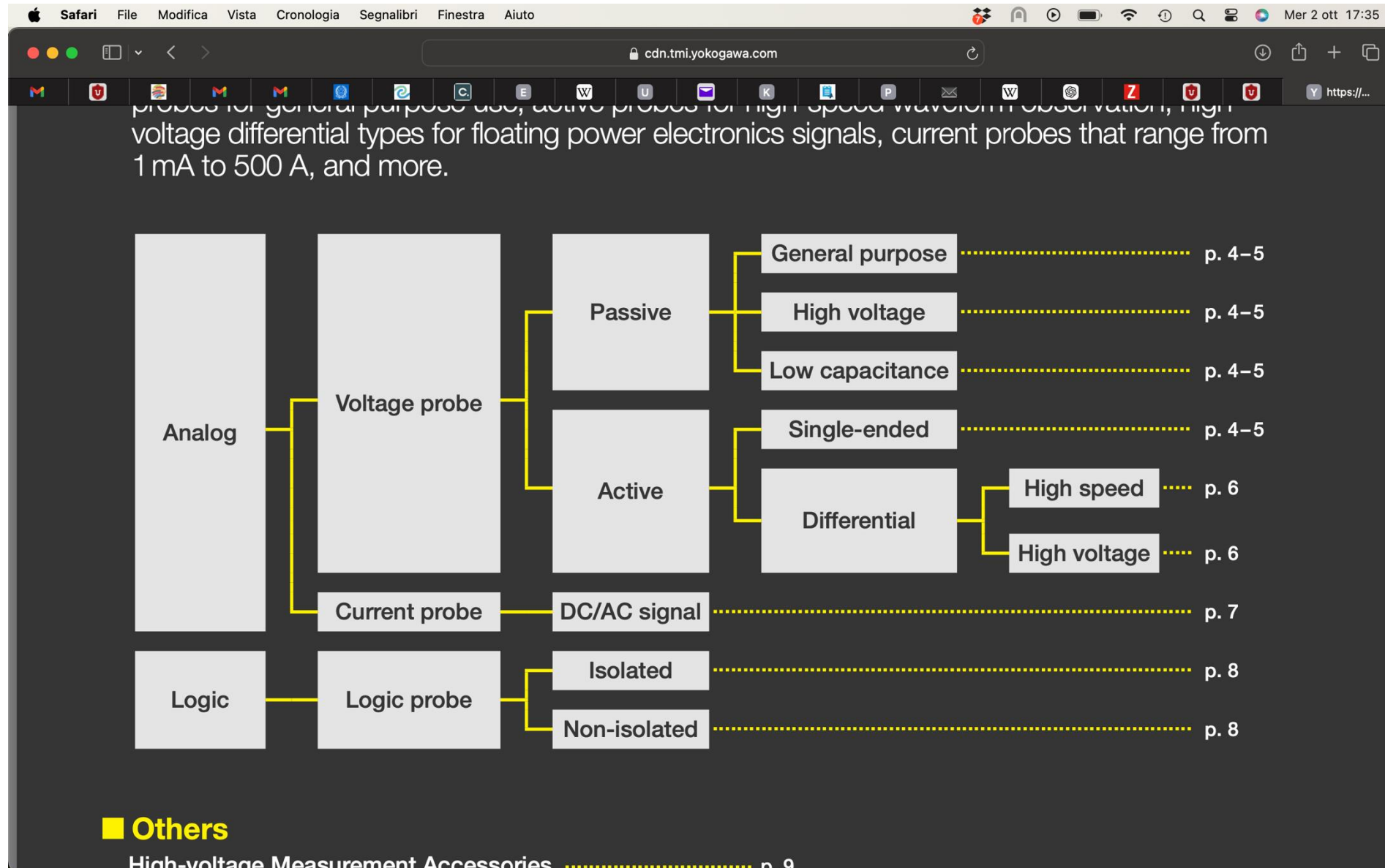



Oscilloscope probes

- **Connections are circuits** with their own parameters
- Connections may alter the circuit behaviour (**Loading effect**)
- Length is comparable to the wavelength \Rightarrow **Transmission lines**
- **Probe**: device enabling to **pick up the signal of interest** and take it to the input connectors of the measuring instrument
- **A pair of conductors, a coaxial cable and a BNC connector**
 - Reduce the loading effect
 - Avoid signal distortion
 - Enable contact with test points



Oscilloscope probes

- Cable length \Rightarrow **Propagation effects**
- Propagation speed $v = 1/\sqrt{\epsilon\mu} = \frac{c}{\sqrt{\epsilon_r}}$
- **Polyethylene** $\Rightarrow \epsilon_r = 2.3 \Rightarrow v \cong 2 \times 10^8$ m/s
- 1 m cable \Rightarrow 200 MHz sinewave
- Up to **few MHz** the cable can be described by a **lumped-parameter** electrical network
- **Coaxial cables capacitance** C_c : 0.5-2 pF/cm
- In parallel with the instrument input impedance




Passive probes

- A tip containing a **parallel RC network**
 - A connector body, that contains a **variable capacitor**, placed in parallel to the BNC connector linking the probe to the oscilloscope
 - A **coaxial cable** from the tip to the connector body
-
- **Attenuation factor**: ratio between the voltage v_x at the signal source and the voltage v_i at the oscilloscope input
 - Typical factor **10**



Passive probes

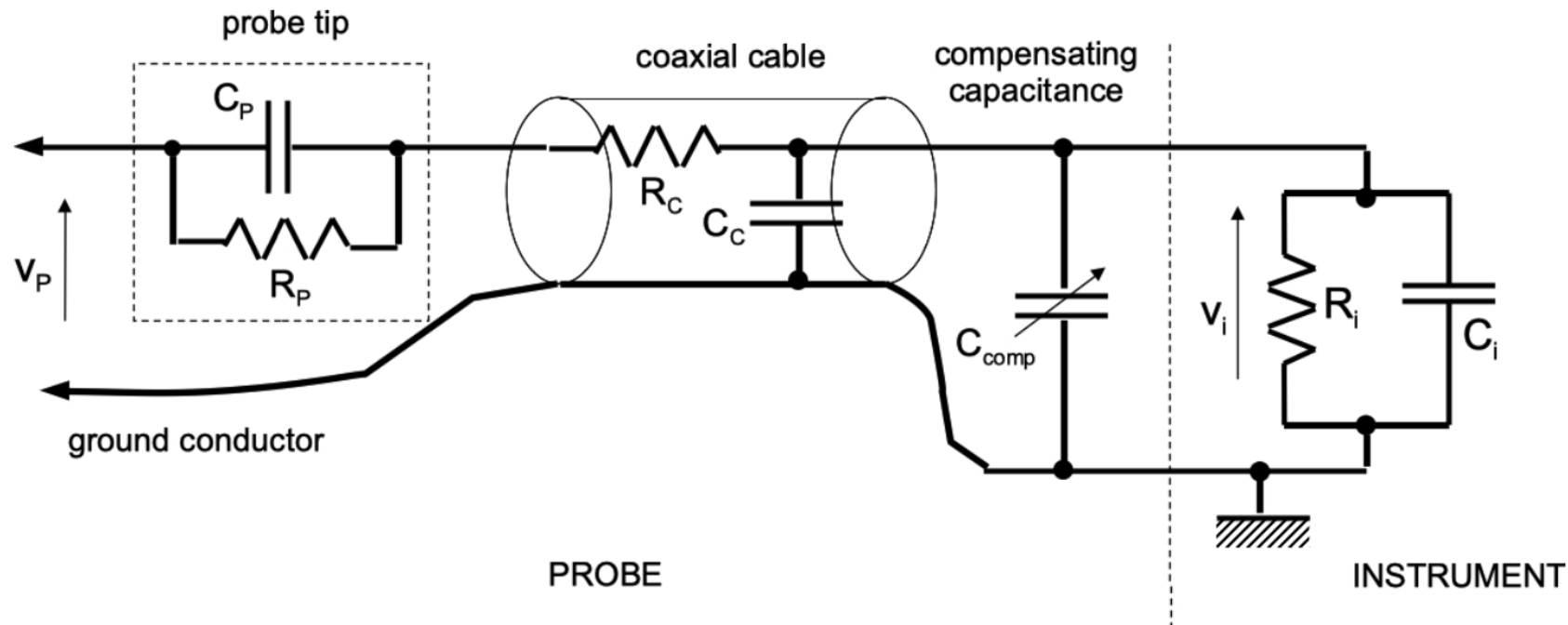- **Probe tip:** C_p and R_p in parallel
- **Coaxial cable:** small R_c and C_c in series
- **Compensation capacitance** C_{comp}






Passive probes

- **Parallel:**

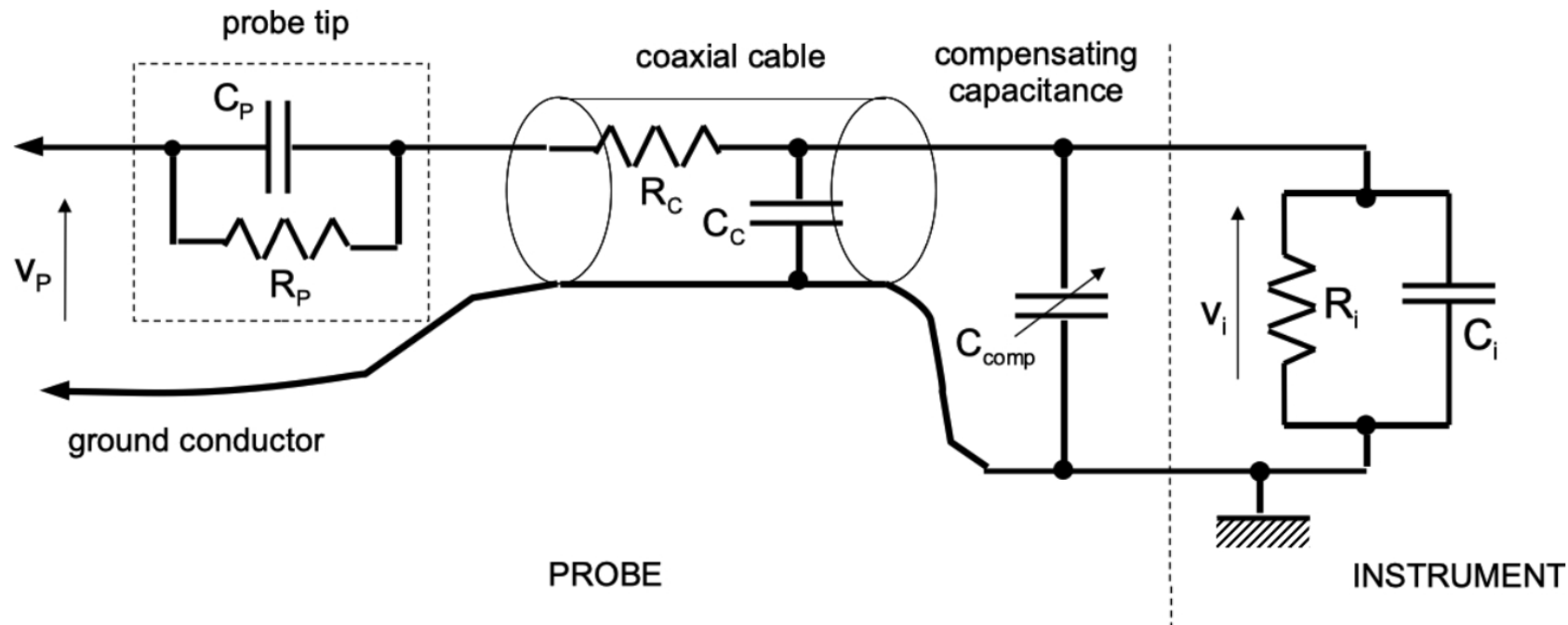- Oscilloscope input capacitance C_i
 - Cable capacitance C_c
 - Compensation capacitance C_{comp}
- } $C_{i(eq)}$ (R_c Neglectable)






Passive probes

- **Series:**

- Parallel in the probe tip
- $Z_{i(eq)}$ (parallel of $C_{i(eq)}$ and R_i)

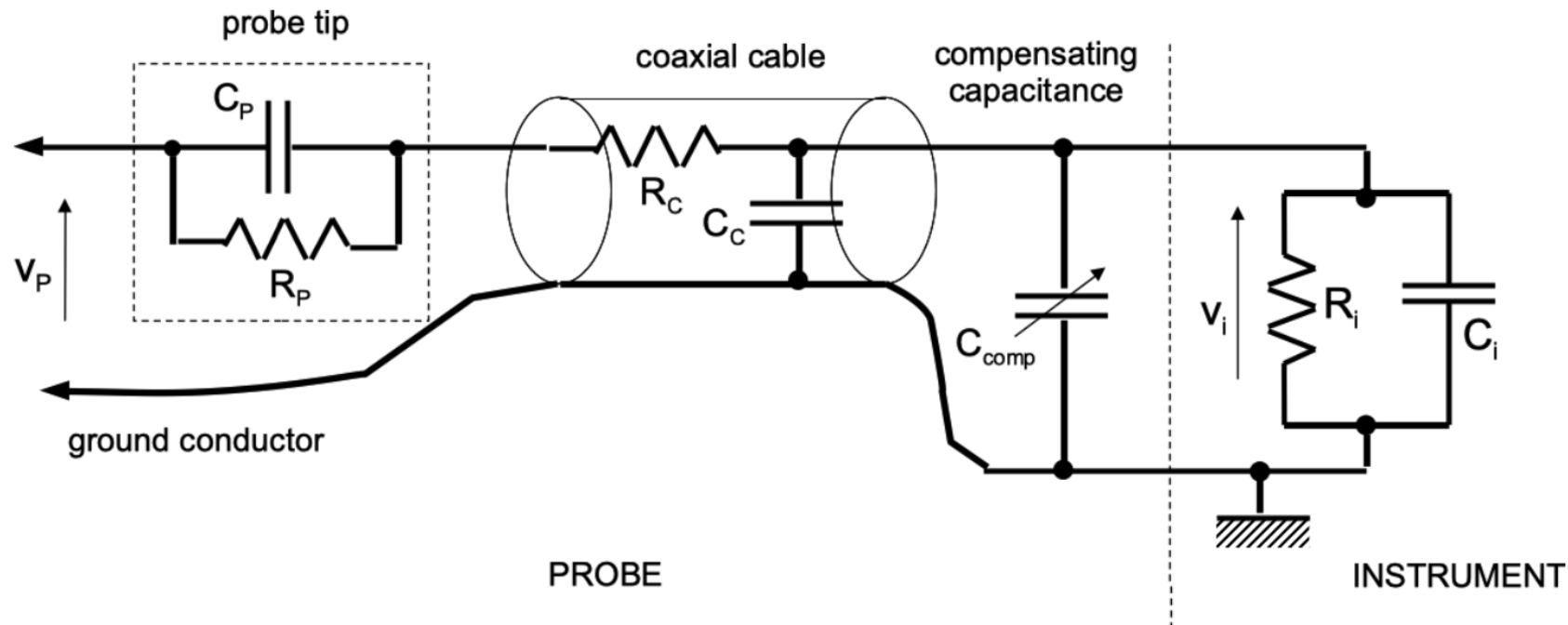- Constant input $\Rightarrow v_i = v_p \frac{R_i}{R_i + R_p}$
- $R_p = 9R_i$






Passive probes

- Probe impedance $Z_p(s) = R_p \frac{1}{1+sR_pC_p}$
- Input impedance $Z_{i(eq)}(s) = R_i \frac{1}{1+sR_iC_{i(eq)}}$
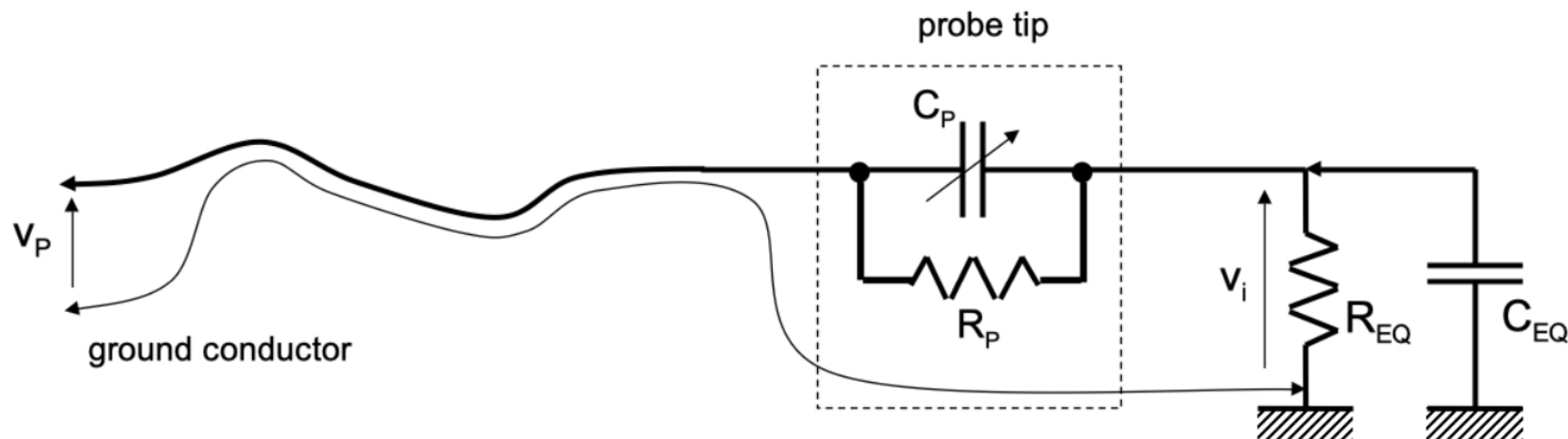
$$\frac{1}{\alpha_{probe}} = \frac{R_i \frac{1}{1+sR_iC_{i(eq)}}}{R_p \frac{1}{1+sR_pC_p} + R_i \frac{1}{1+sR_iC_{i(eq)}}}$$





Passive probes

- Probe impedance $Z_p(s) = R_p \frac{1}{1+sR_pC_p}$
- Input impedance $Z_{i(eq)}(s) = R_i \frac{1}{1+sR_iC_{i(eq)}}$

$$\frac{1}{\alpha_{probe}} = \frac{R_i \frac{1}{1+sR_iC_{i(eq)}}}{R_p \frac{1}{1+sR_pC_p} + R_i \frac{1}{1+sR_iC_{i(eq)}}}$$

$$R_p C_p = R_i C_{i(eq)}$$

$$\alpha_{probe} = \frac{R_p + R_i}{R_i}$$



Independent of
frequency




Passive probes

- Equivalent impedance:

$$Z_{EQ}(s) = R_p \frac{1}{1 + sR_p C_p} + R_i \frac{1}{1 + sR_i C_{i(eq)}}$$

- Compensation condition satisfied:
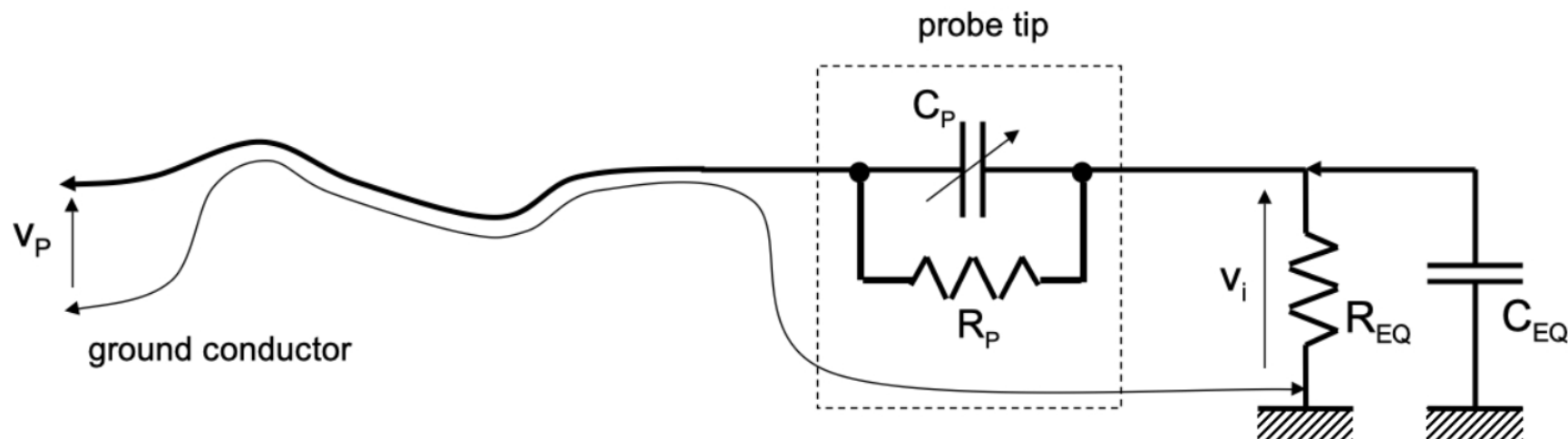
$$Z_{EQ}(s) = (R_p + R_i) \frac{1}{1 + s(R_p + R_i) \frac{C_{i(eq)}}{\alpha_{probe}}}$$





Passive probes

- Equivalent impedance:

$$Z_{EQ}(s) = R_p \frac{1}{1 + sR_p C_p} + R_i \frac{1}{1 + sR_i C_{i(eq)}}$$


- Compensation condition satisfied:

$$Z_{EQ}(s) = (R_p + R_i) \frac{1}{1 + s(R_p + R_i) \frac{C_{i(eq)}}{\alpha_{probe}}}$$


- $R_{EQ} = R_p + R_i = R_i \cdot \alpha_{probe}$
- $C_{EQ} = \frac{C_{i(eq)}}{\alpha_{probe}}$




Passive probes

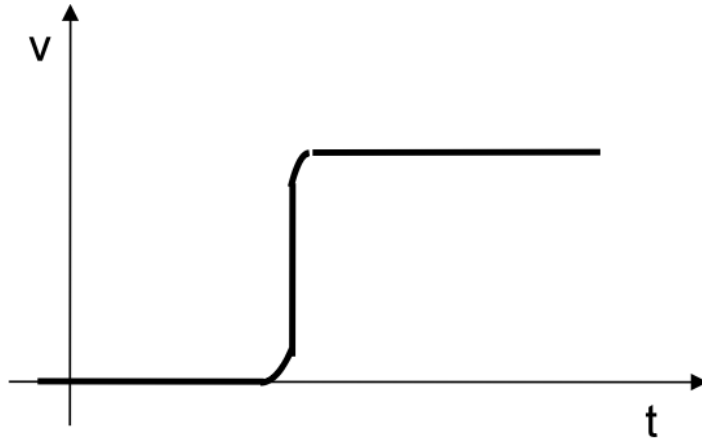

(a) compensated probe;

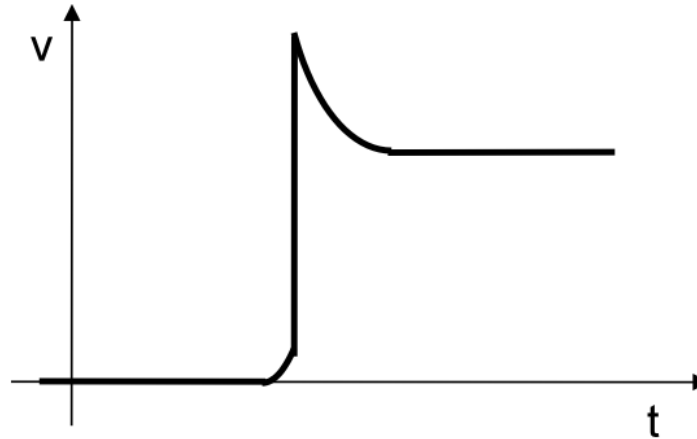

(b) over-compensated probe;

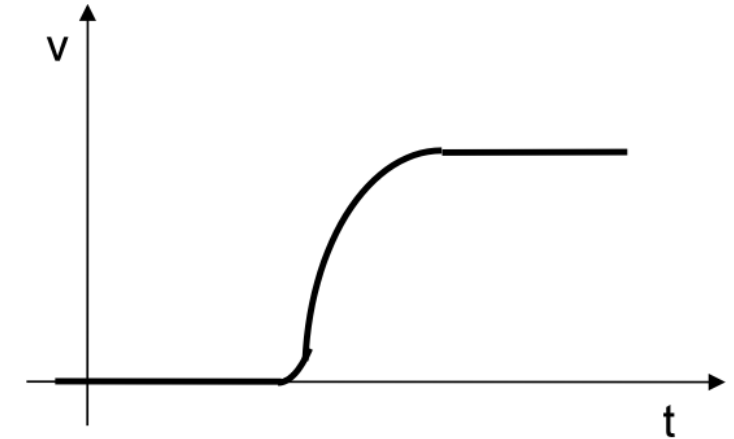


(c) under-compensated probe;

- **Over-compensated:** C too high \rightarrow Limited attenuation of the high order harmonics
- **Under-compensated:** C too small \rightarrow Larger attenuation of the high order harmonics



UNIVERSITÀ
DEGLI STUDI
DI PADOVA


Active probes

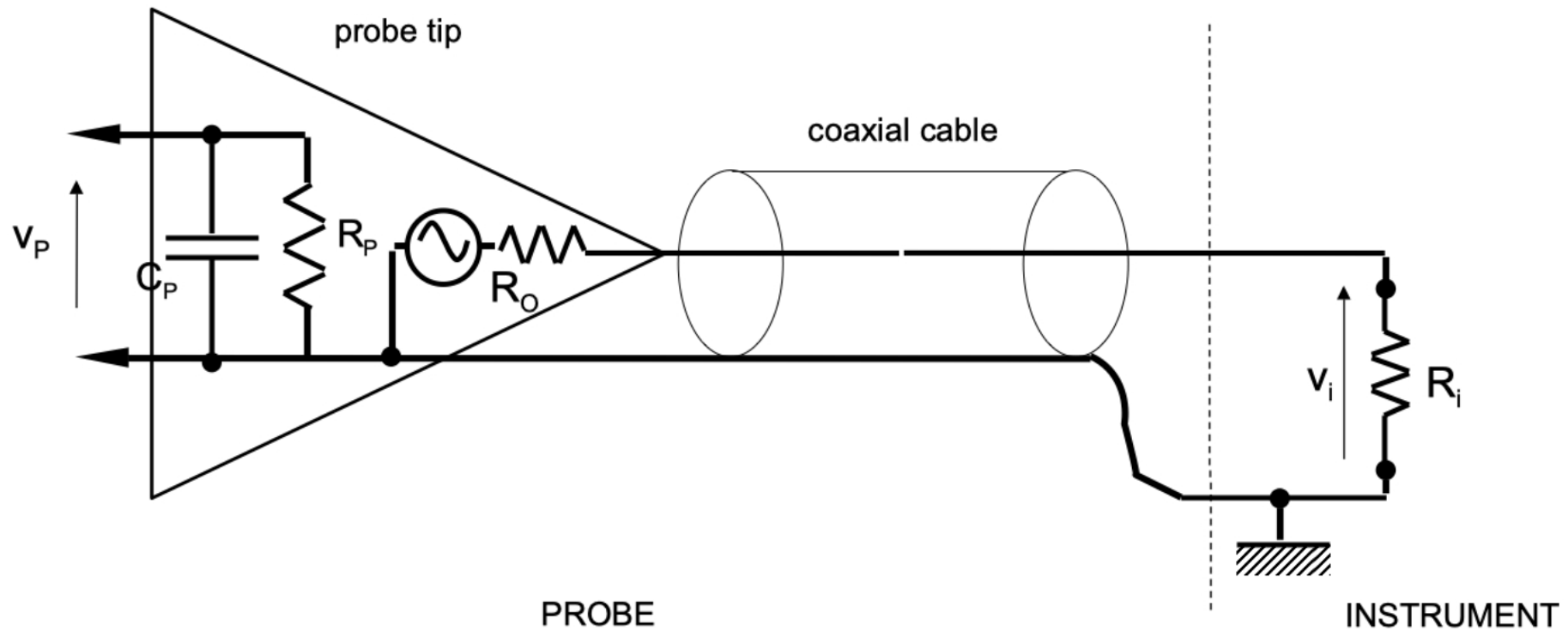




Pseudo-differential measurement

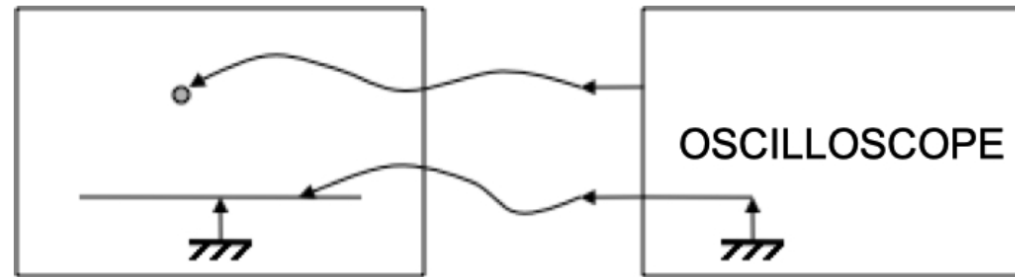- Oscilloscopes feature a **single-ended input** with the ground reference connected to earth



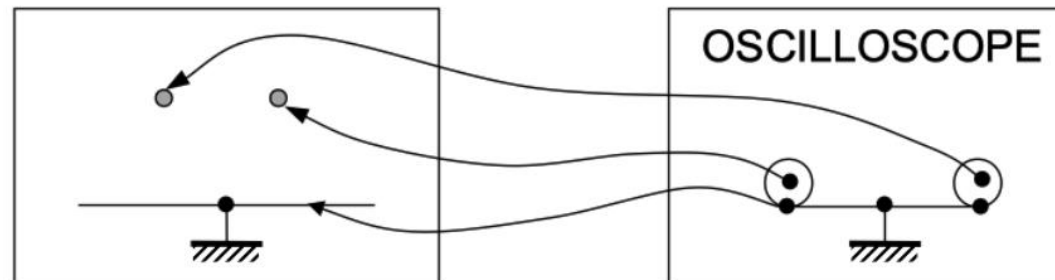
- Pseudo-differential measurement:** measure the “voltage to ground” of the two points independently, then determine their difference





UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Differential probes

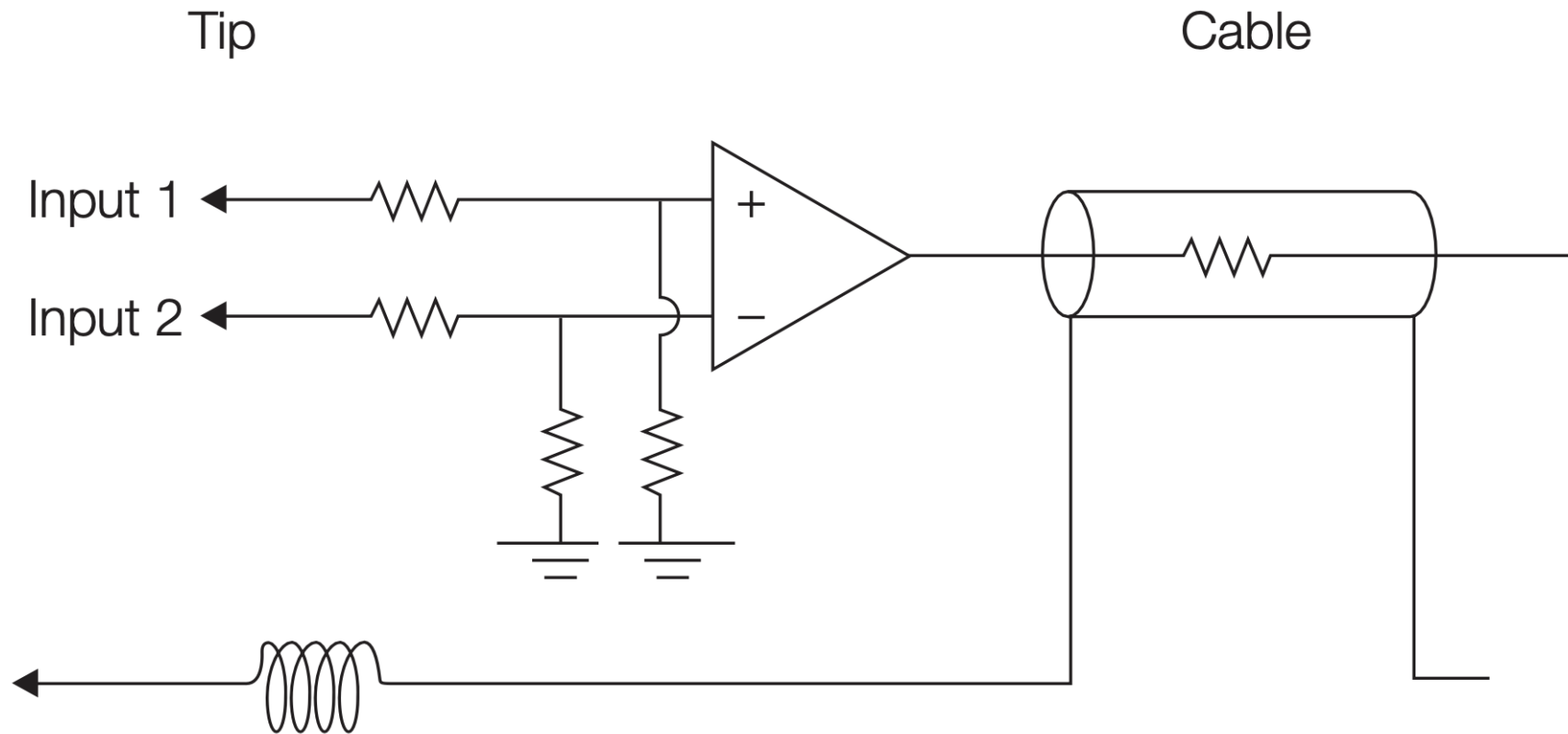



UNIVERSITÀ
DEGLI STUDI
DI PADOVA