



UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Test circuits – Measuring component specifications

Lecture #5

Electronic measurements

Alessandro Pozzebon



Electronic Components Testing

- **Component specifications**

- Performances
- Power consumption
- Operating limits



Behavioural model



System-level design



Computer-assisted design

- **Digital circuits**



- Boolean algebra

- **Analog circuits**

- Blocks model




Electronic Components Testing

- **Measurements**  **Extract relevant component data**
- **Specifications** (maximum and minimum values)

- Results of measurements
- Test circuits:
 - Create suitable operating conditions for the **Device Under Test (DUT)**
 - Enable test signals to be accurately measured



Operational Amplifier

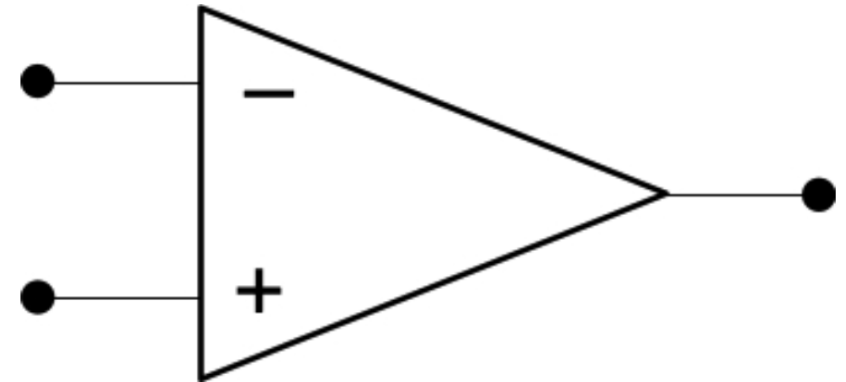
- Single, ground-referenced output and two differential inputs called, respectively, inverting (−) and non-inverting (+) inputs
- **Voltage gain** is infinite (very large in practice, order of 10^5 or more)
- **Input impedance** is infinite (order of $10^8 \Omega$)
- **Output impedance** is null (a few Ω in practice)










Operational Amplifier

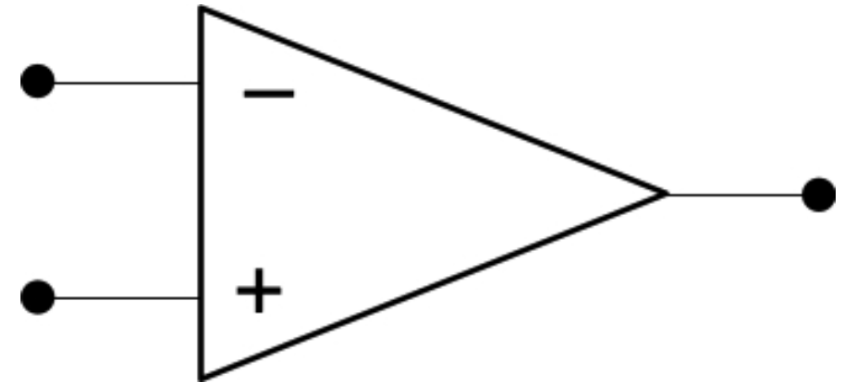- **Current drawn by the inputs** is zero, since input impedance is infinite
- Since output voltage must be finite and voltage gain is close to infinite, the **two inputs** may be assumed to be equipotential for most practical purposes
- Any intensity of **output current** can be obtained, since output impedance is negligible






Operational Amplifier

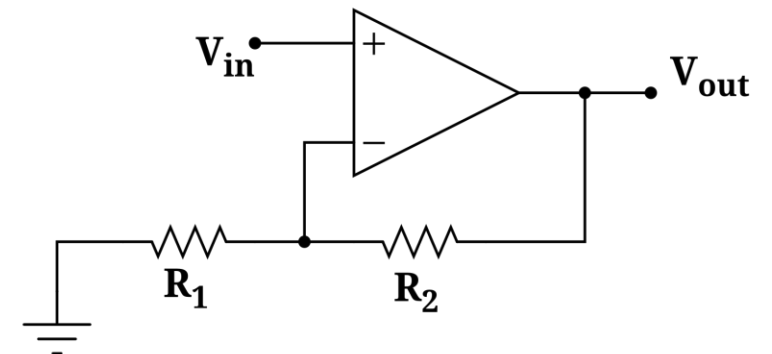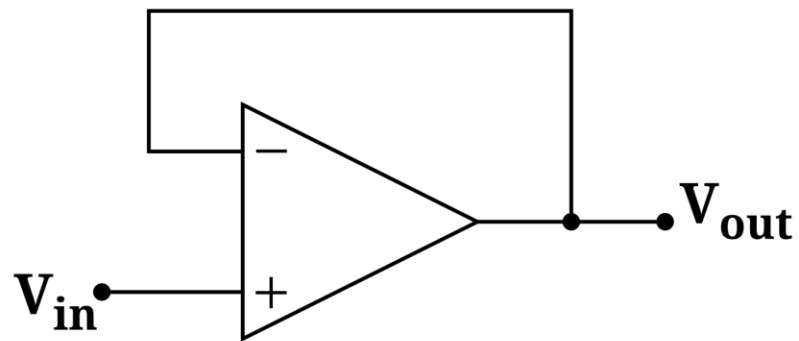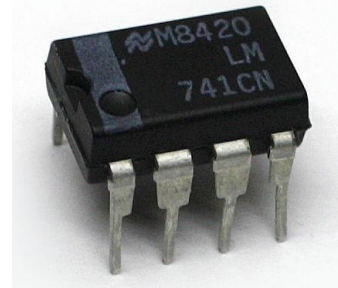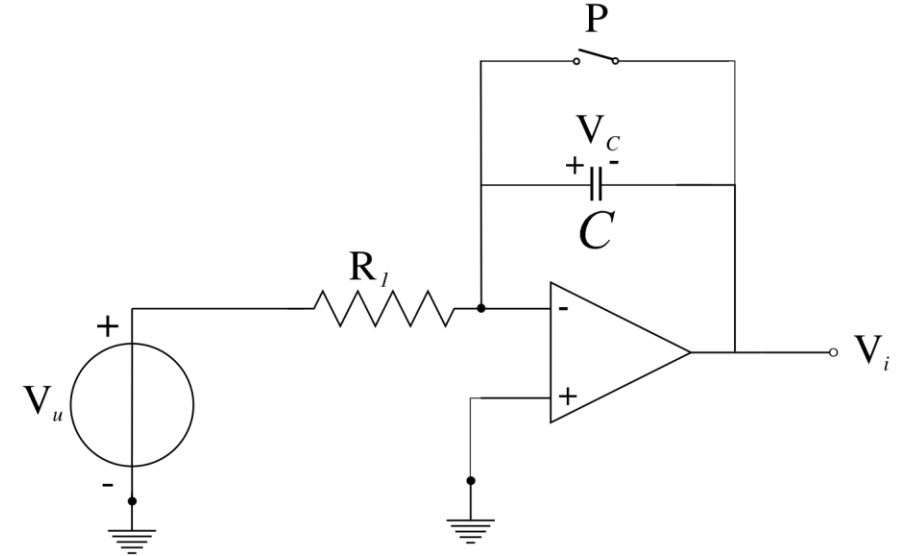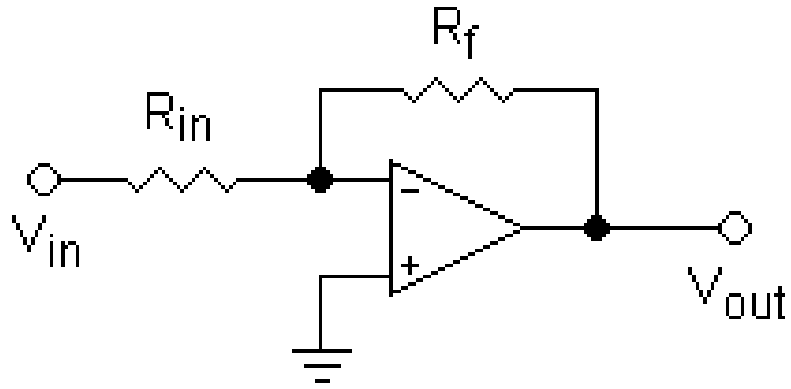



Real operational amplifier

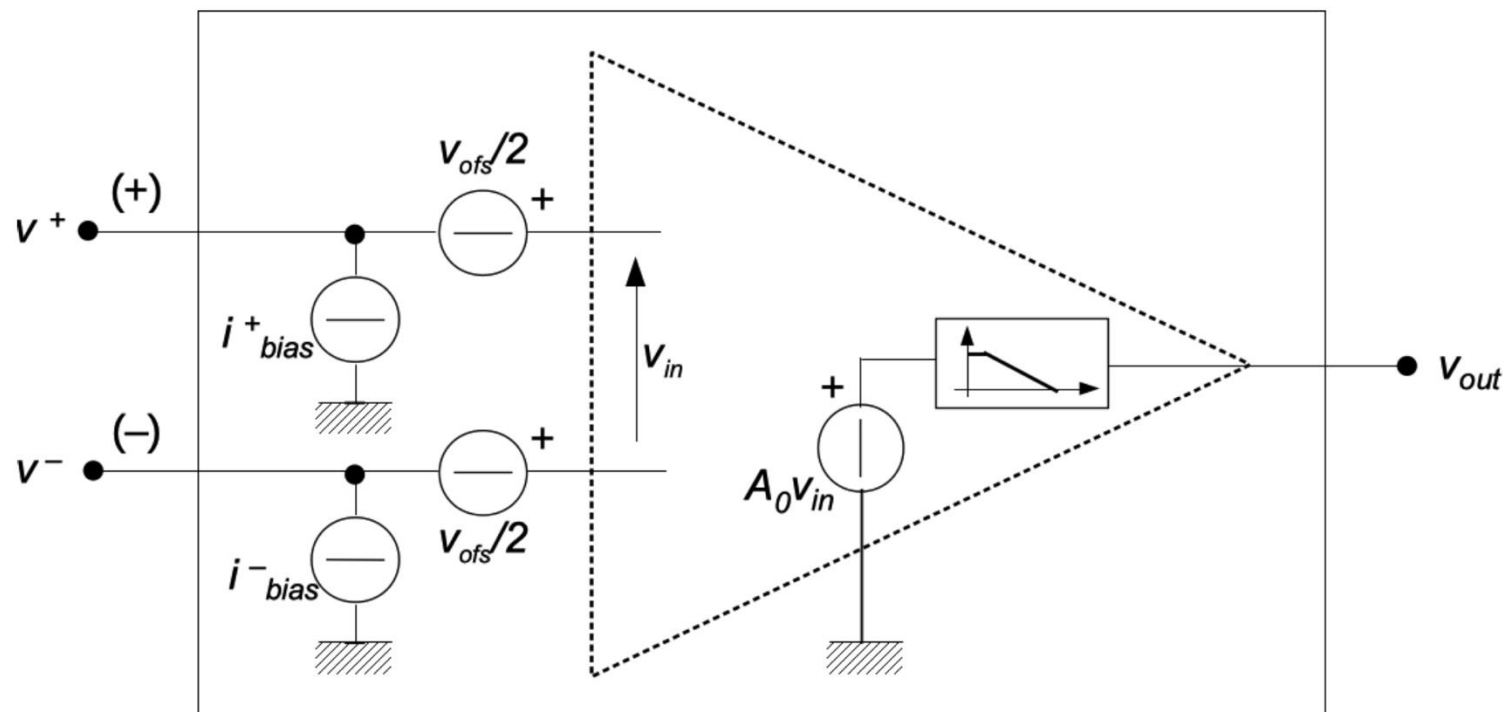- **Voltage sources** at the input → OpAmp **offset voltage**
- **Current sources** at the input → **Bias currents** through the input terminals
- Voltage-controlled **voltage source** → **Finite gain**
- **Frequency-dependent block** → Low-frequency pole → **Frequency response**



SPICE macromodel



Operational Amplifier Measurements

- **Extremely high gain**



Difficult to be measured due to the very large difference between input and output voltage levels



- **Open-loop gain**

Suitable feedback configurations



$$G_{ol}(f) = \frac{A_0}{1 + j2\pi f T_1}$$

Effects of the test circuit on the measured device

- A_0 DC gain
- T_1 low frequency pole time constant




Unit-gain bandwidth

- Voltage-follower configuration

$$\begin{aligned} G_{vf}(f) &= \frac{G_{ol}(f)}{1 + G_{ol}(f)} \cong \frac{1}{1 + j2\pi f \frac{T_1}{A_0}} = \\ &= \frac{1}{1 + j \frac{f}{f_T}} \\ f_T &= \frac{A_0}{2\pi T_1} = A_0 f_{ol} \end{aligned}$$

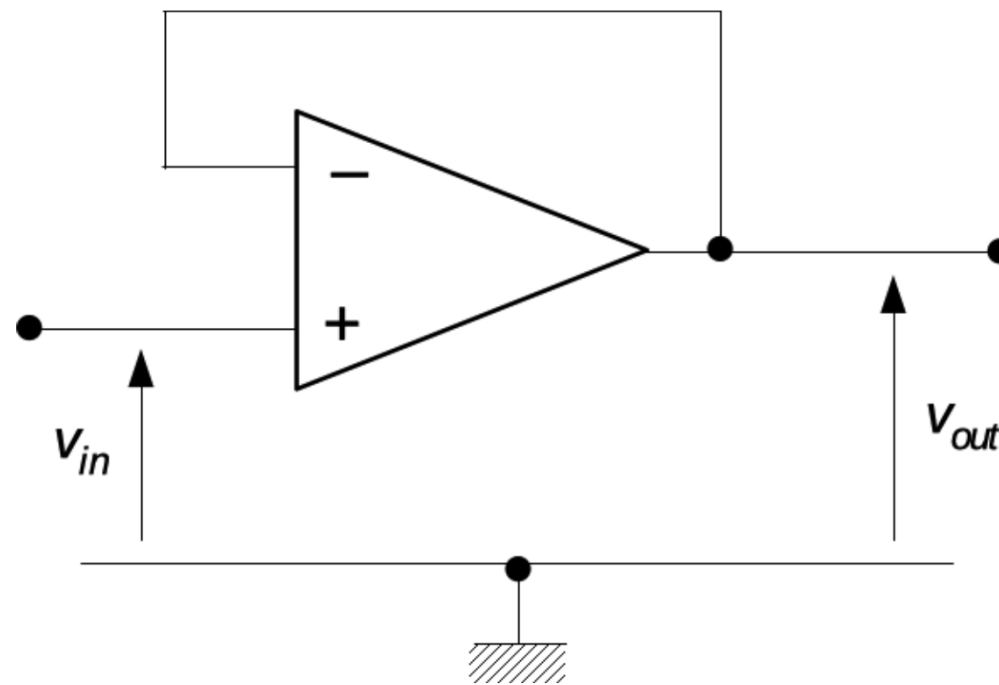
- f_{ol} unit-gain bandwidth
 - Typically, in the order of MHz





Unit-gain bandwidth measurement

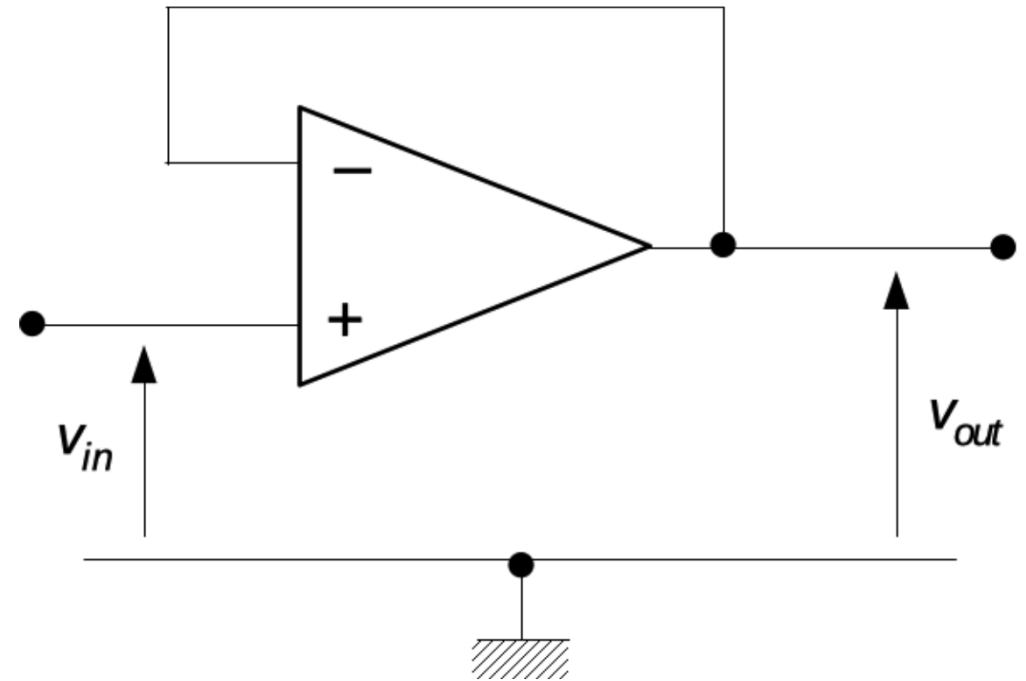- Frequency at which measured gain is 3 dB less than DC gain
- DC gain = 1
- Ratio of output to input voltage = $\frac{1}{\sqrt{2}} \cong 0.707$
- **Sinewave generator**
- **Two-channel oscilloscope** (voltage follower input and output)






Unit-gain bandwidth measurement

- Bias currents
- Voltage offsets



**Significant output voltage offset
(non-zero mean value)**

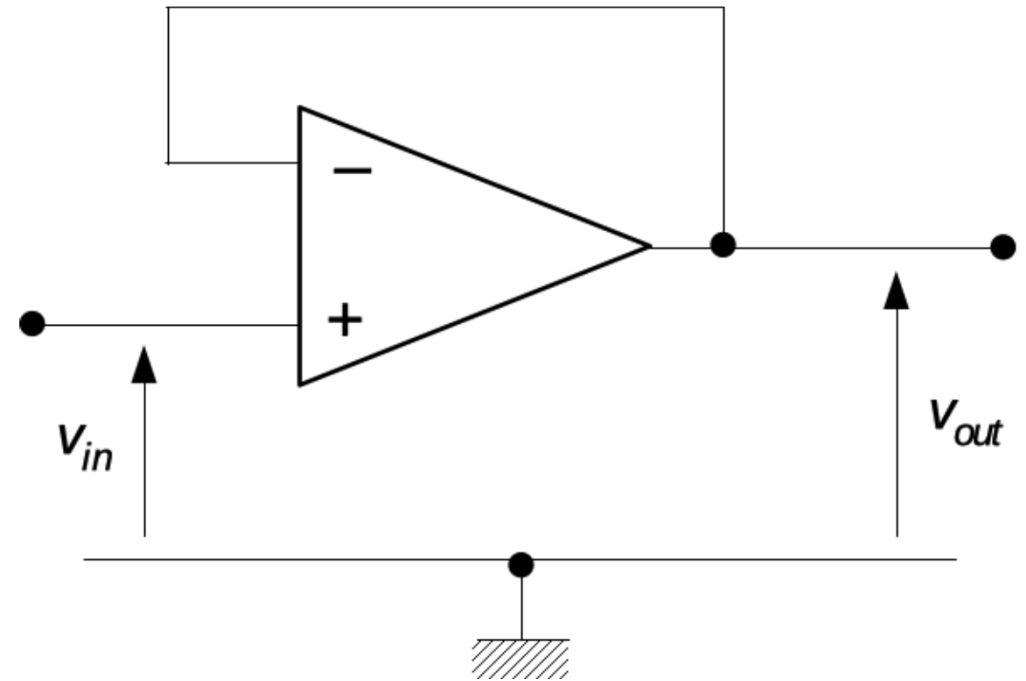- Peak-to-peak or RMS voltage
- AC coupling (both channels)





Open-loop gain

- Input-output measurement with sinewave input at different frequencies



High gain makes measurements hard


Input wave should be in the μV range



Feedback loop with an additional OpAmp




Open-loop gain measurement

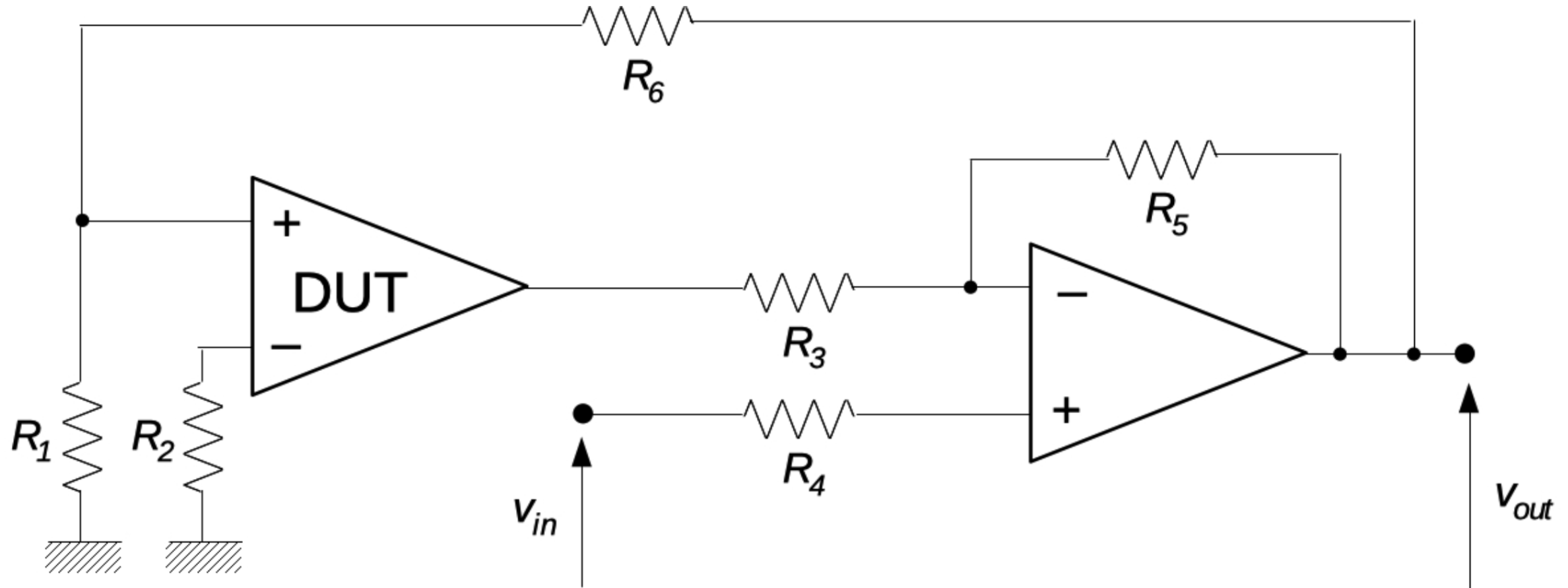



Open-loop gain measurement

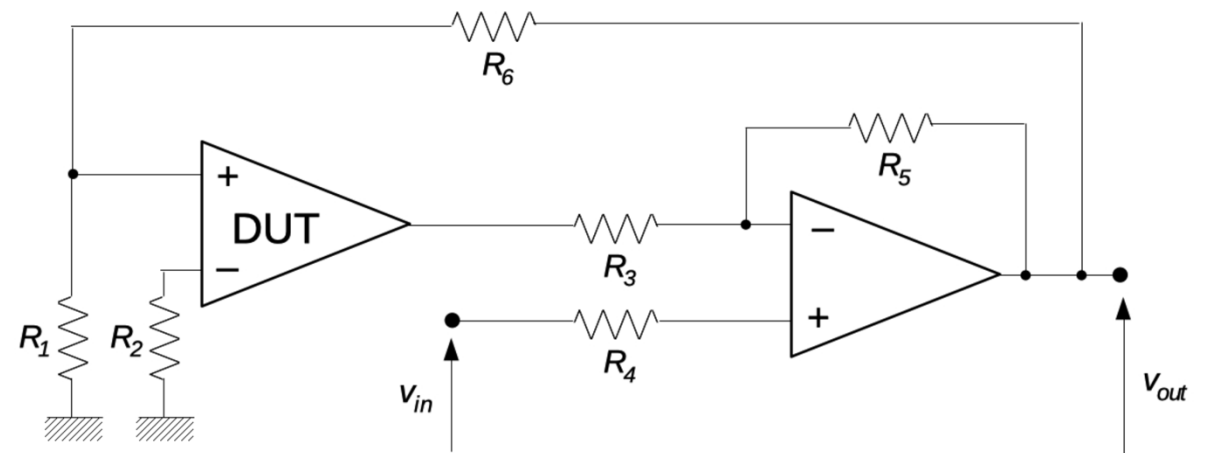
- v_{in} sent to the auxiliary OpAmp non-inverting input through R_4
- DUT output to the inverting input through R_3
- $R_3 = R_4$ to get a balanced differential input for the auxiliary OpAmp
- $R_1 = R_2$ to balance the effect of the DUT bias currents





Open-loop gain measurement

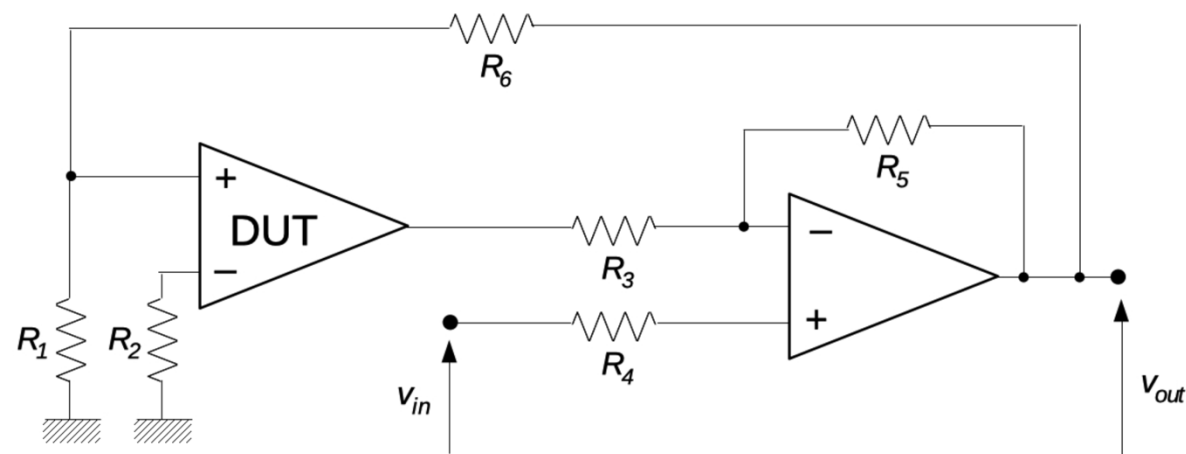
- The inner feedback loop provides the gain
- $R_5 \gg R_3$
- The outer loop acts as a voltage divider to bring a fraction of v_{out} to the non-inverting input of DUT
- $v_{DUTin} = v_{out} \frac{R_1}{R_1 + R_6}$
- $R_6 \gg R_1$





Open-loop gain measurement

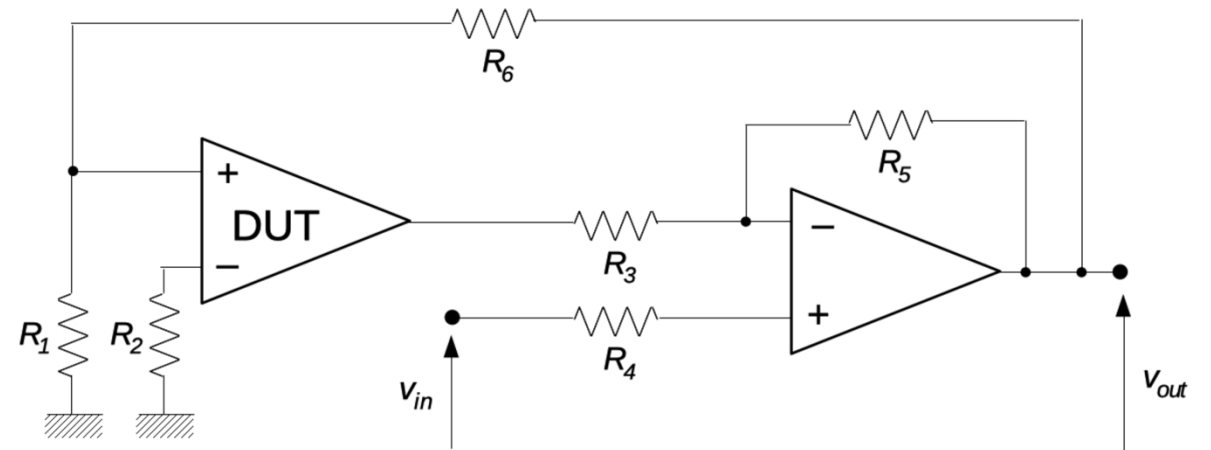- $v_{DUT_{out}} = v_{in}$
- DUT gain = $\frac{v_{DUT_{out}}}{v_{DUT_{in}}} = \frac{v_{in}}{v_{out} \frac{R_1}{R_1 + R_6}}$
- Actual R_1 and R_6 values should be **measured**



R_1	R_2	R_3	R_4	R_5	R_6
47 Ω	47 Ω	100 Ω	100 Ω	47 k Ω	47 k Ω



PROCEDURE

1. **Connect a power supply** to the test circuit and power it up
2. **Connect the waveform generator** to the test circuit and to an oscilloscope input channel, so that the test sinewave can be measured (using a ‘T’ coaxial connector). Set an appropriate waveform amplitude
3. Using a coaxial cable with suitable wire clips (or “banana” plugs), **acquire the test circuit output** and send it to an oscilloscope input channel
4. **Determine a set of frequencies** where the DUT gain is to be determined and repeat the measurement at each frequency



TIPS

- Low frequency pole



- No AC coupling (attenuation)

- Noisy v_{out} signal



- RMS(AC) measurement function instead of peak-to-peak
- Averaging acquisition mode (Stable trigger)



Gain and Phase Shift

Measurement outputs

- Amplitude of the test circuit input sinewave v_{in}
- Amplitude of the test circuit output sinewave v_{out}
- Delay τ of the output sinewave from the input sinewave

DUT GAIN

$$G[\text{dB}] = 20 \log_{10} \frac{v_{in}}{v_{out} \frac{R_1}{R_1 + R_6}}$$

DUT PHASE

$$\Delta\phi = -\tau \cdot 2\pi[\text{rad}] = -\tau \cdot 360[\text{degrees}]$$

- Test circuit input corresponds to the DUT output, while test circuit output provides the DUT input




Test circuit analysis

Limitations

- Deviations from nominal **resistance values**



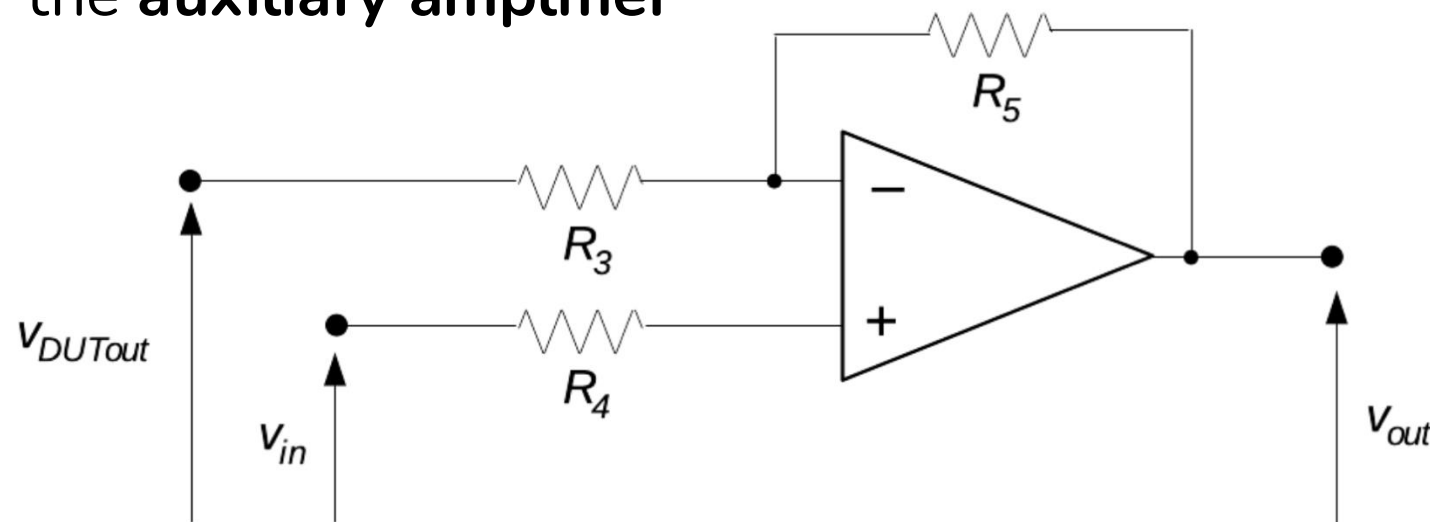
- tolerance limits are not critical, since the measured operational amplifier gain is quite large
- Behaviour of the **auxiliary amplifier**





Test circuit analysis

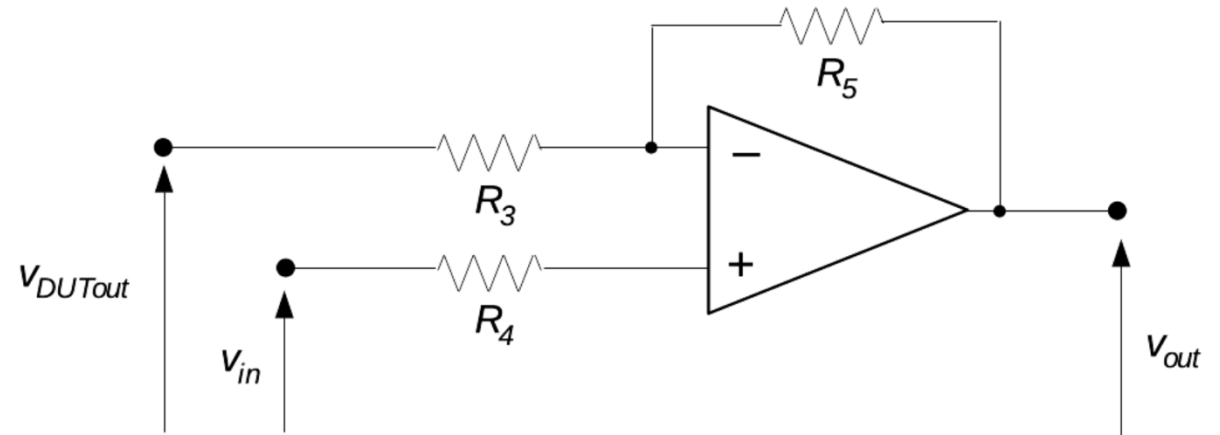- Behaviour of the **auxiliary amplifier**
- Input-output relationship:



$$v_{out} = \frac{R_5 + R_3}{R_3} \cdot \left(v_{in} - \frac{R_5}{R_5 + R_3} v_{DUTout} \right)$$


- Open-loop gain of the auxiliary amplifier:

$$f_{T_2} = \frac{A_{0,2}}{2\pi T_2}$$



Test circuit analysis

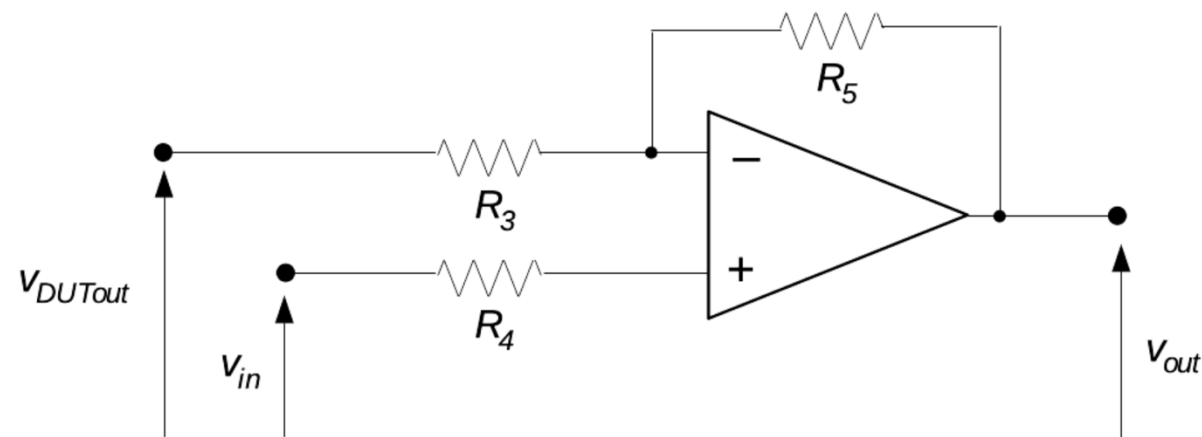- Behaviour of the **auxiliary amplifier**
- New input-output relationship:



$$v_{out} = \frac{1}{1 + j \frac{f}{f_T} \cdot \frac{R_5 + R_3}{R_3}} \cdot \left[\frac{R_5 + R_3}{R_3} \cdot \left(v_{in} - \frac{R_5}{R_5 + R_3} v_{DUTout} \right) \right]$$


- Test circuit amplifier is **band-limited**

$$f_{Aux} = \frac{f_{T2}}{\frac{R_5 + R_3}{R_3}} \text{ with } \frac{f_{T2}}{A_{0,2}} < f_{Aux} < f_{T2}$$



Test circuit analysis

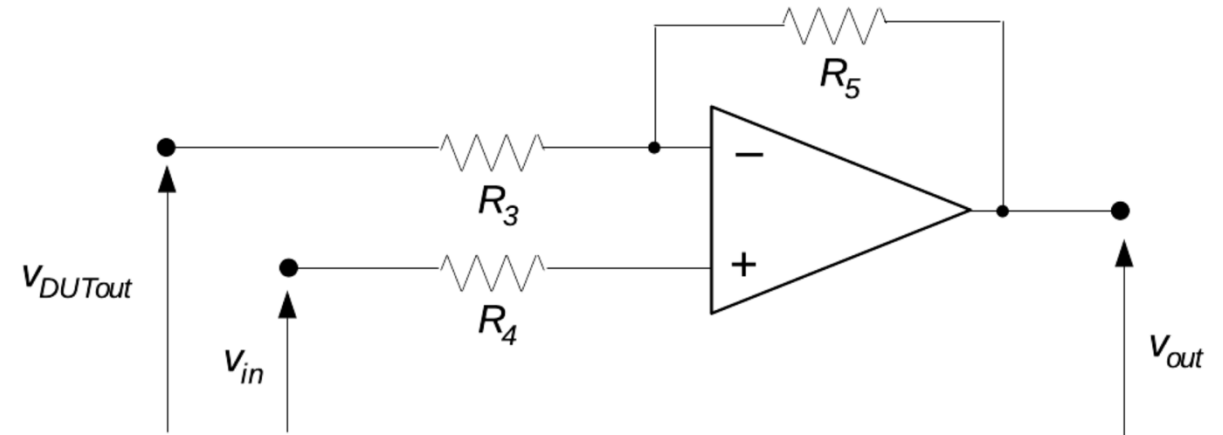- Numerical example:
- $f_{T_1} = f_{T_2} = 1 \text{ MHz}$
- $A_0 = 10^5$
- $\frac{R_5 + R_3}{R_3} \cong 5 \cdot 10^3$
- Low frequency pole at 10 Hz
- Auxiliary cut-off frequency at 2 kHz
- v_{out} is attenuated \rightarrow DUT gain increases





UNIVERSITÀ
DEGLI STUDI
DI PADOVA