



UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Signal integrity

Lecture #8

Electronic measurements


Alessandro Pozzebon



- Signals exchange → **pre-defined waveforms**
- **Digital signal:**
 - Alternation between two voltage levels
 - Very short switching intervals → Set-up time
 - Permanence in the levels for a suitable time → Hold time
- **Shape specifications:**
 - Rise and fall times
 - Pre-shoot
 - Overshoot




Waveform masks

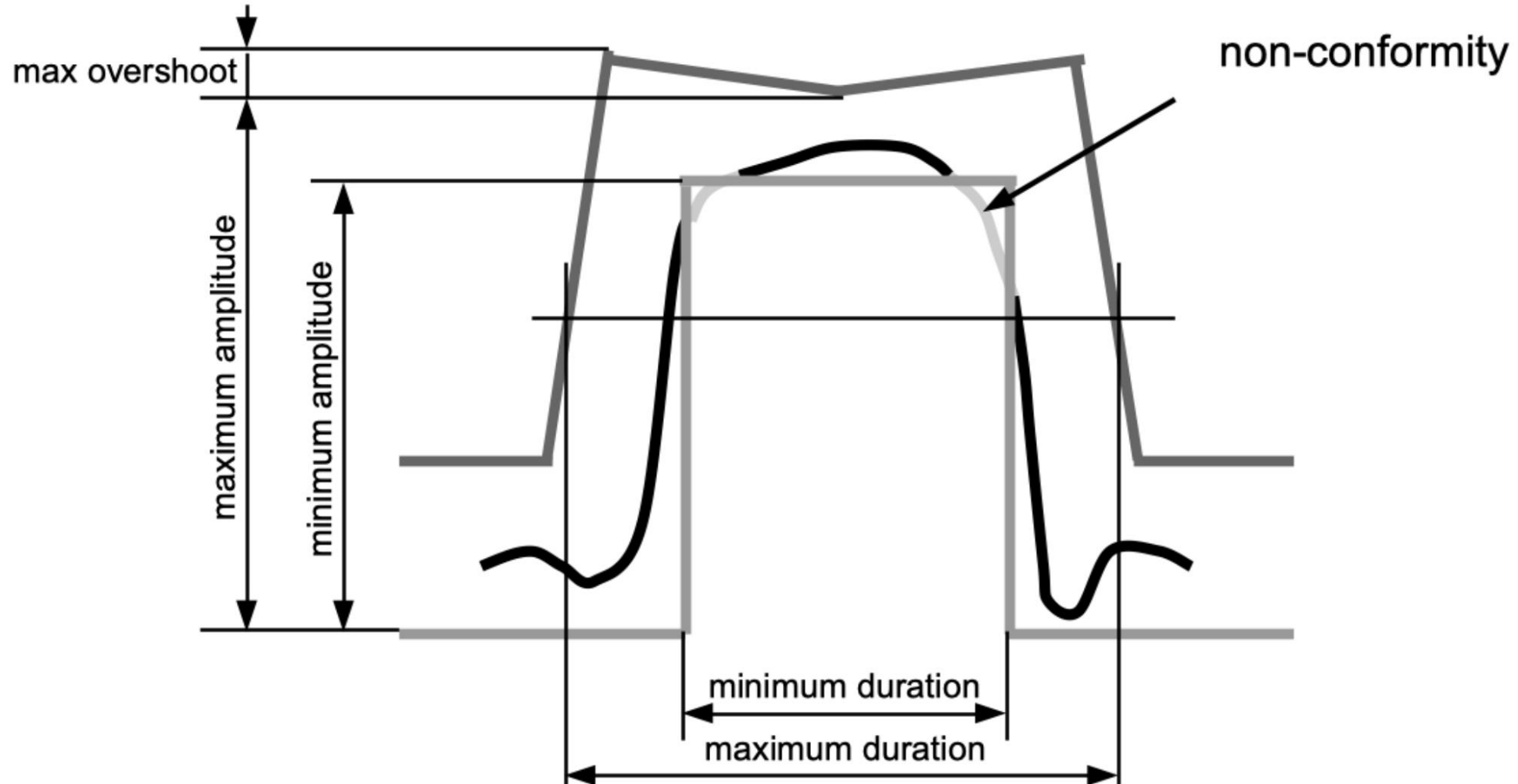



Signal integrity

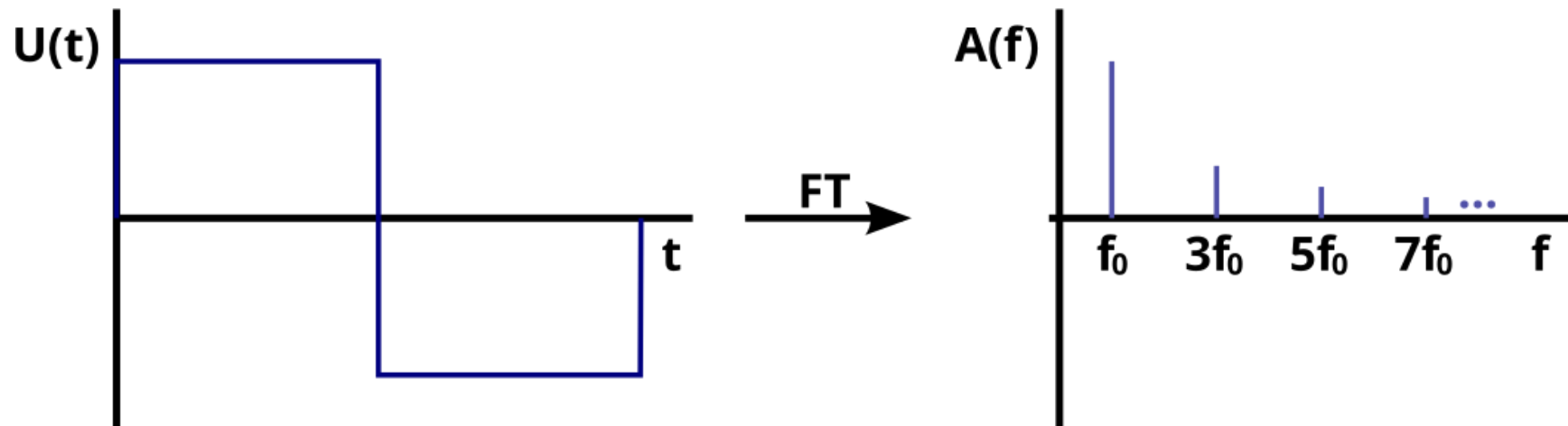- Example: ideal symmetric square wave
- $T = 200$ ns
- Fundamental frequency $f_s = 5$ MHz



- Oscilloscope with a 100 MHz bandwidth \rightarrow up to 19 harmonics within the bandwidth



Signal integrity

- **Real** symmetric square wave \rightarrow non-zero rise and fall times t_s
- **Trapezoidal** waveform
- **Time domain:** convolution in the between an “ideal” square wave and a rectangular pulse having length t_s
- **Frequency domain:** multiplication of the square wave spectrum and the spectrum $W(f)$ of a rectangular pulse:

$$W(s) = \frac{\sin \pi f t_s}{\pi f t_s}$$

Great attenuation at frequencies over $1/t_s$

- $t_s = 20 \text{ ns} \rightarrow$ Limiting frequency 50 MHz
- $t_s = 5 \text{ ns} \rightarrow$ Limiting frequency 200 MHz



Time Domain Reflectometry (TDR)

- Diagnostic technique employed when interconnections between components can be treated as **TRANSMISSION LINES**
- Analysis and troubleshooting of **high-speed digital systems**
- Voltage level transitions → **Transient** phenomena
- Poorly matched devices → Multiple **reflections**



Unintended changes in logic states


Delays in reaching stable voltage levels

PROPAGATION TIME



Time Domain Reflectometry (TDR)

- Microstrip line → Transmission line

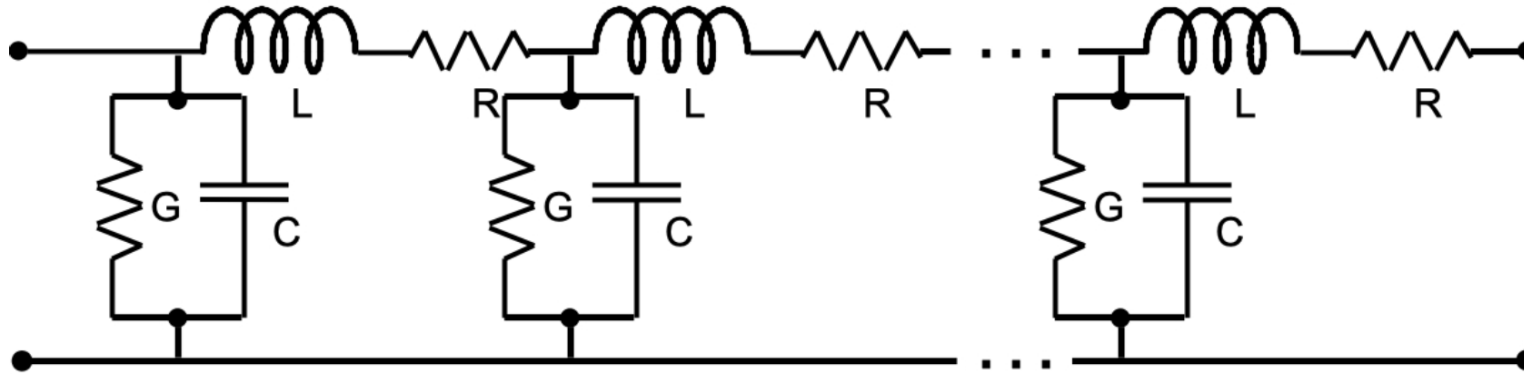

- Each segment of infinitesimal length
- Characteristic impedance

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

- R, L, C and G per unit length



Time Domain Reflectometry (TDR)

- Ideal behaviour → Delay
- Impedance mismatches → Reflections

Mismatched load at the opposite end of a line



Reflection




Time required to reach the measurement point from the reflection point
proportional to the distance

- Short, broadband test signals (Pulses or sharp edges)



UNIVERSITÀ
DEGLI STUDI
DI PADOVA


TDR measurement

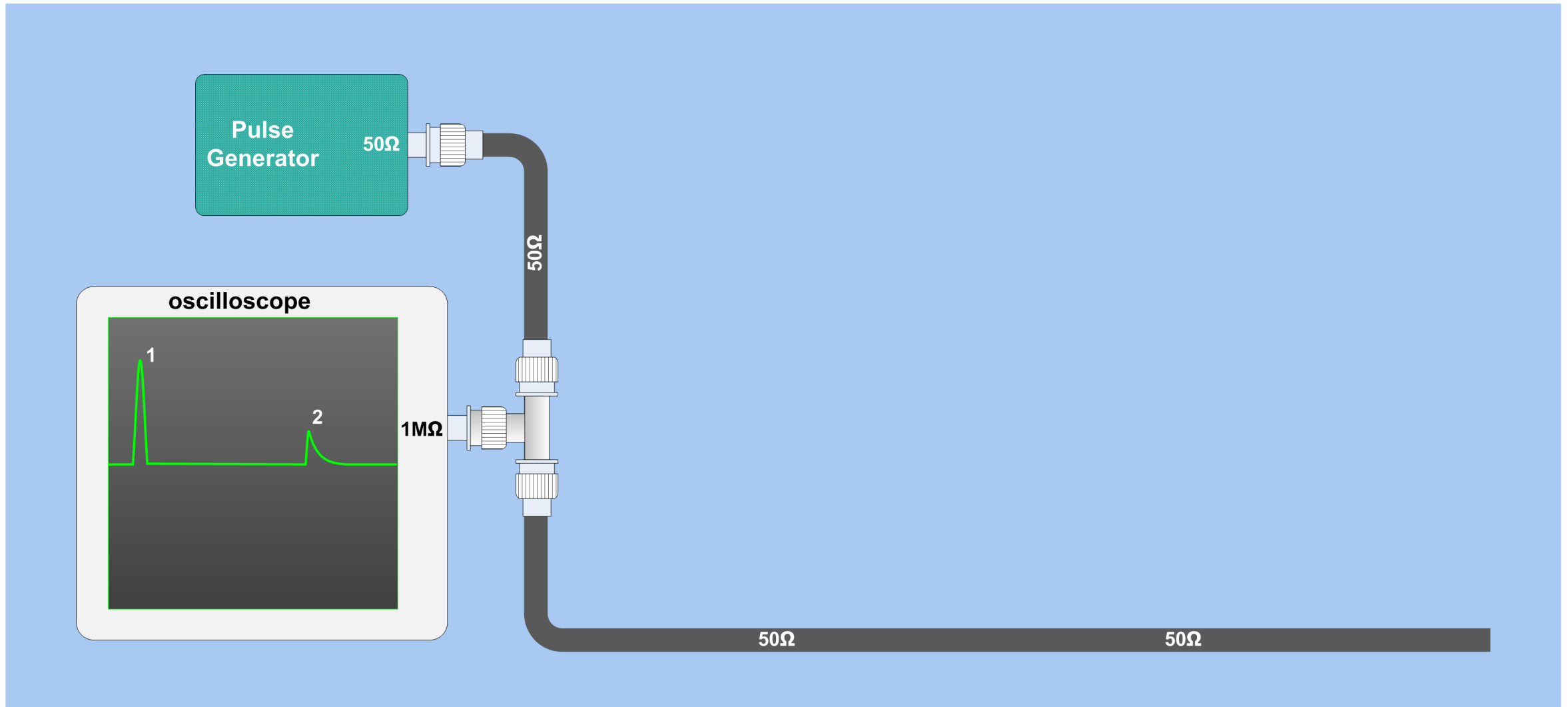



TDR measurement

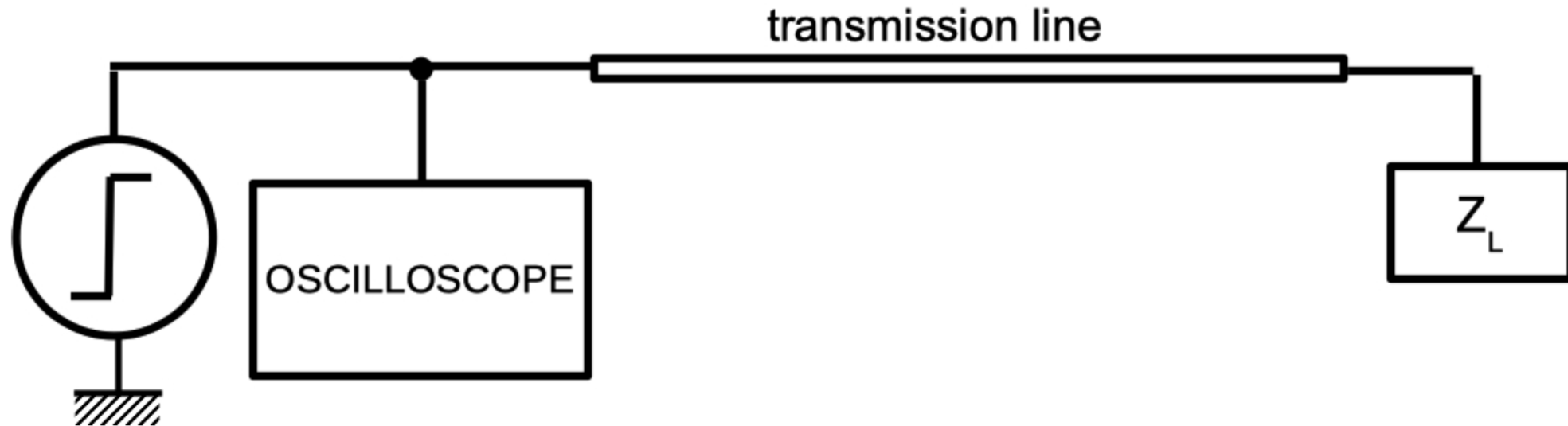- Instruments:
 - Oscilloscope
 - Broad band signal generator





TDR measurement

- The signal generator produces a test signal having a **very short length**
- The generator output impedance must be **matched** to the characteristic impedance of the transmission line under test
- **Only one end** of the transmission line needs to be accessed for measurement
- Although the observed trace shows the response of a whole transmission line, **individual reflection components** contributed by different points along the line can be separated in time, and originating points can be located
- Finite speed $v = \frac{c}{\sqrt{\epsilon_r}}$ where ϵ_r dielectric constant of the propagation medium
- **Coaxial cables** → polyethylene: $\epsilon_r \cong 2.3$
- **Microstrip lines** → partly in resin/fibreglass, partly in air



TDR measurement

- Test signal amplitude E_i
- Unmatched load impedance Z_L at the end of the line
- If $Z_L \neq Z_0 \rightarrow$ Partial or total reflection

- Reflection coefficient

$$\rho(\omega) \frac{E_r}{E_i} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

- x_d **distance** of the reflection point from the generator
- $\tau_d = x_d/v$ **time required** by the test signal to reach the reflection point
- $\Delta t = 2\tau$



TDR measurement


- **Lossless transmission** line of length l
- $R = 0$ and $G = 0$
- $Z_0 = \sqrt{L/C}$ is **purely resistive**
- If $R_L = Z_L$ purely resistive ρ is **real** and the **reflected wave is summed** to the incident
- $-1 \leq \rho \leq 1$
- A mismatched termination allows to estimate the **electrical length of the line**

$$l = (v \cdot \Delta t)/2$$



TDR measurement

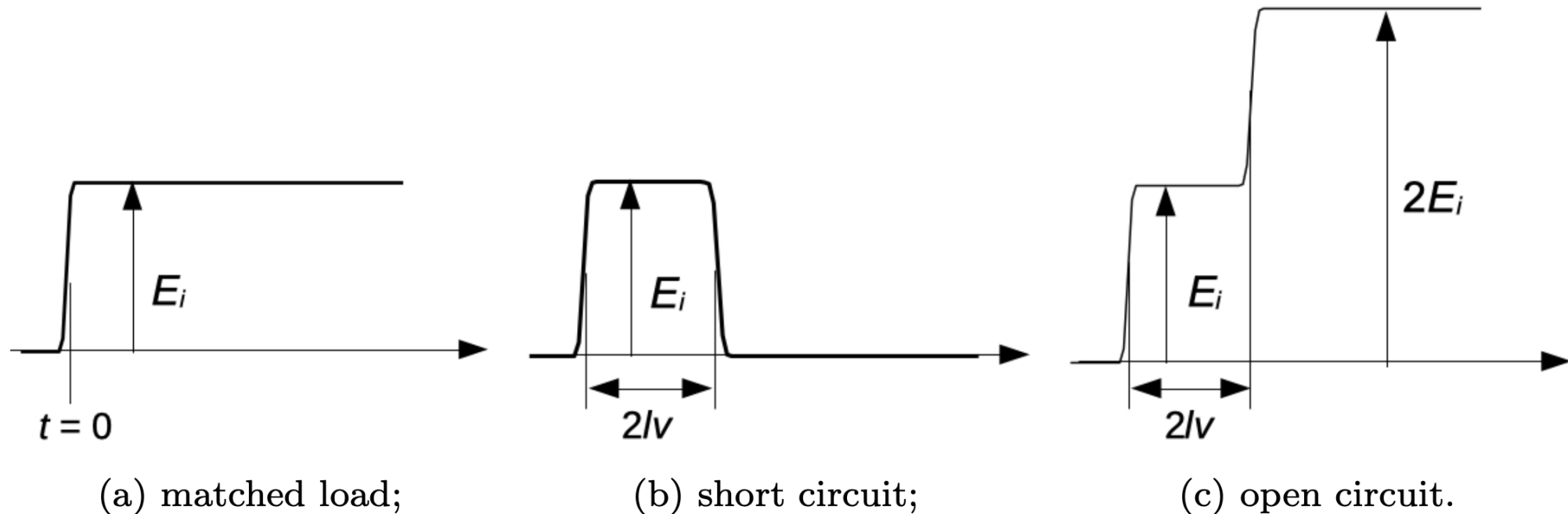- $R_L = Z_0 \Rightarrow \rho = 0 \Rightarrow E_r = 0 \Rightarrow E_r + E_i = E_i$
- $R_L = 0 \Rightarrow \rho = -1 \Rightarrow E_r = -E_i \Rightarrow E_r + E_i = 0$
- $R_L = \infty \Rightarrow \rho = 1 \Rightarrow E_r = E_i \Rightarrow E_r + E_i = 2E_i$






TDR measurement

- Resistive termination
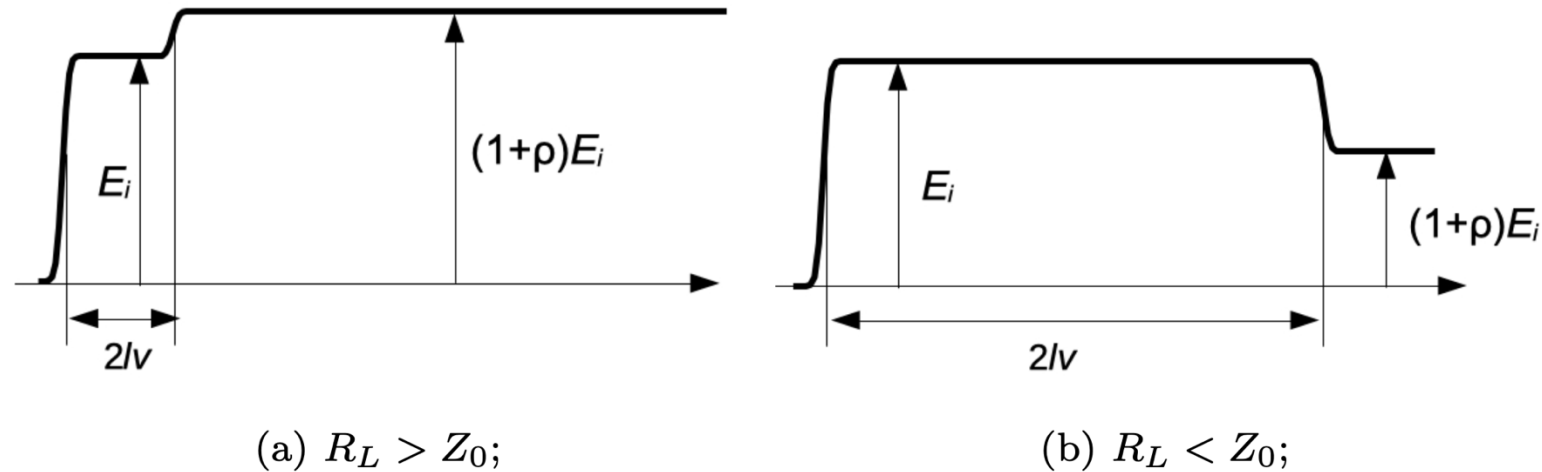
$$\frac{E_i + E_r}{E_i} = 1 + \rho \quad \text{where} \quad 1 + \rho = \frac{2R_L}{R_L + Z_0}$$




- Normalized load resistance $r_L = R_L/Z_0$, $V_1 = E_i$ and $V_2 = E_i + E_r$

$$\frac{V_2}{V_1} = 1 + \rho = \frac{2r_L}{r_L + 1} \quad \text{from which} \quad R_L = r_L \cdot Z_0 = \frac{V_2/V_1}{2 - V_2/V_1} \cdot Z_0$$




TDR accuracy analysis

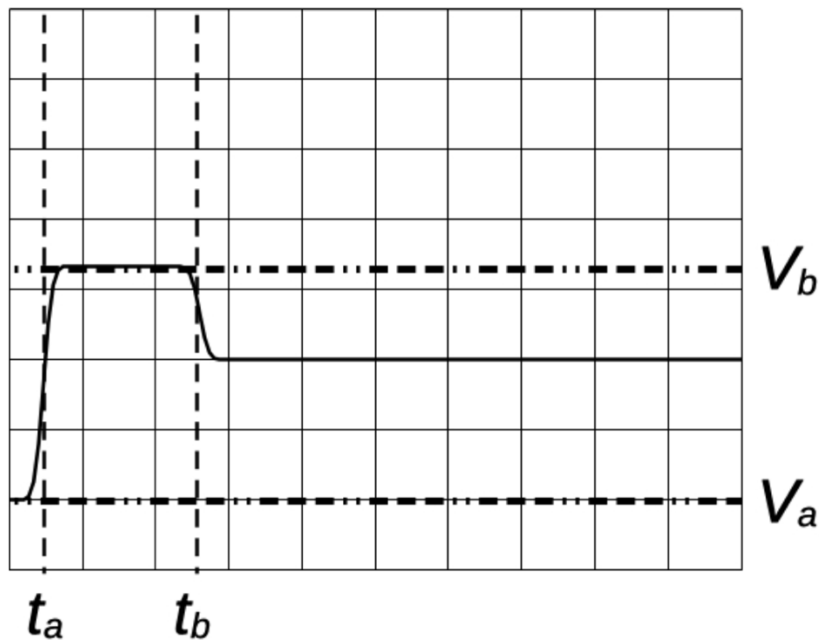- **Measurement accuracy** depending on specific points in the trace
- **Amplitude cursor positions** on the constant voltage levels



(a) amplitude cursors measuring E_i ;

$$E_i = V_b - V_a = V_1$$

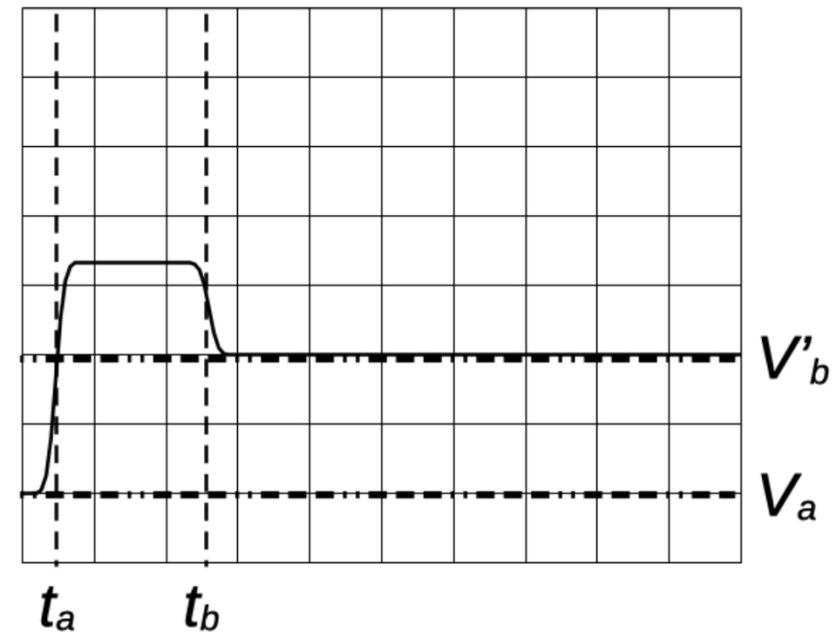

(b) amplitude cursors measuring $E_i + E_r$;

$$E_i + E_r = V'_b - V_a = V_2$$



TDR with reactive line termination

- Generic load impedance Z_L
- Fourier transform of an **incident step** $V_i(\omega) = E_i/(j\omega)$

$$V_r(\omega) = \frac{E_i}{j\omega} \cdot \frac{Z_L(\omega) - Z_0}{Z_L(\omega) + Z_0}$$

- After Δt the reflected wave is added to E_i :

$$\frac{E_i}{j\omega} \cdot [1 + \delta(\omega)] = \frac{E_i}{j\omega} \cdot \frac{Z_L(\omega)}{Z_L(\omega) + Z_0}$$



TDR with reactive line termination


- Capacitance C_L
- Waveform shape \rightarrow Inverse transform of:

$$\frac{E_i}{j\omega} + \frac{E_i}{j\omega} \cdot \frac{\frac{1}{j\omega C_L} - Z_0}{\frac{1}{j\omega C_L} + Z_0} = \frac{E_i}{j\omega} \cdot \frac{1}{1 + j\omega C_L Z_0}$$


- Junction between 2 cables with a connector introducing a series **inductance** L_C
- In general, **all possible load configurations** composed of either a series or a parallel of a resistance and a reactive quantity (capacitance or inductance) can be analyzed in this way



TDR with reactive line termination

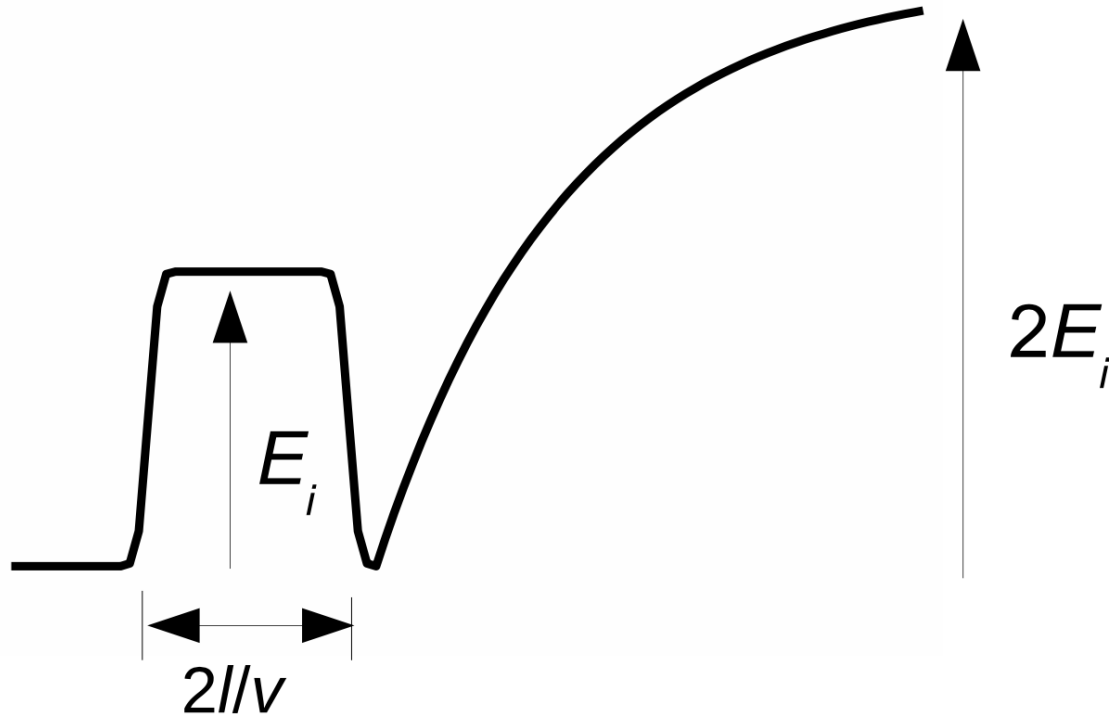

(a) capacitive load;

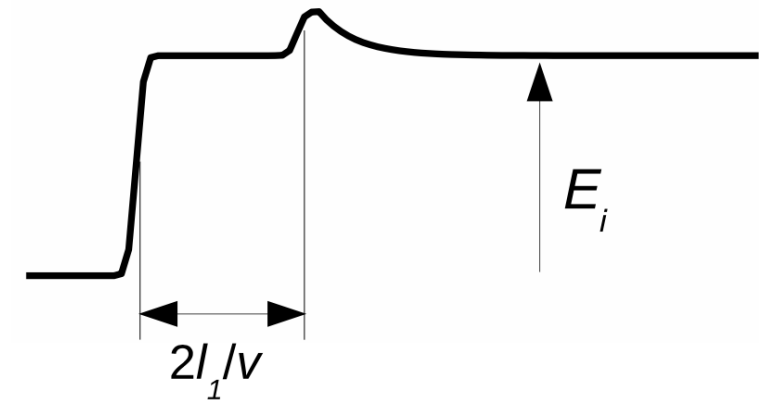

(b) effect of a junction where an inductive effect is introduced by the connector.



TDR systems specifications

- **Bandwidth** → Step as close as possible to the ideal behaviour
 - Short rise time
 - No overshoot
 - No oscillations
- **Test signal rise time** determines the minimum discernible separation
- **Propagation speed** of 15/20 ns/cm → sub-ns rise times for PCB analysis
- **Time resolution** → Sampling intervals of the same order of magnitude as the test signal rise time
- **Square wave** → Final steady state value to be reached in each half-period



Laboratory activity

- **Instruments:**
 - Keysight 33600A or Tektronix AFG 3101 **signal generator**
 - Coaxial cable
 - Keysight DSOX1102G (100 MHz) or MSOX3024T (200 MHz) **digital oscilloscope**
 - accessories and passive components
- Broad-band **signal generator**, providing either short pulses or steps with short rise time, whose output impedance should match the characteristic impedance of the transmission line under test (50 Ω)
- **Oscilloscope** with comparable bandwidth, connected to the line under test in parallel to the test signal generator



Laboratory activity

- Transmission line → **Long coaxial cable**
- Typical conditions → microstrip lines → Broad band instrumentation

TIME RESOLUTION

- Test signal: **SQUARE WAVE**
 - Any amplitude (ex. 1 V)
 - Period long enough to avoid superposition of the TDR responses from consecutive voltage steps (frequency below 10 kHz)
- Oscilloscope in **high impedance** (T-connector)
- Connection between the oscilloscope and the line under test as short as possible




Laboratory activity

- Measuring the length of a line
- Coil of coaxial cable
- One end connected to the T of the oscilloscope
- The opposite end open $\rightarrow Z_0 = \infty, \rho = 1$
- Measurement of the delay between the incident and reflected wavefront
- $l = (v \cdot \Delta t) / 2$
- $v = c / \sqrt{\epsilon_r} \rightarrow \epsilon_r = 2.3$ for polyethylene $\rightarrow v \cong 2 \times 10^8$ m/s



Laboratory activity

- Measuring the length of a line

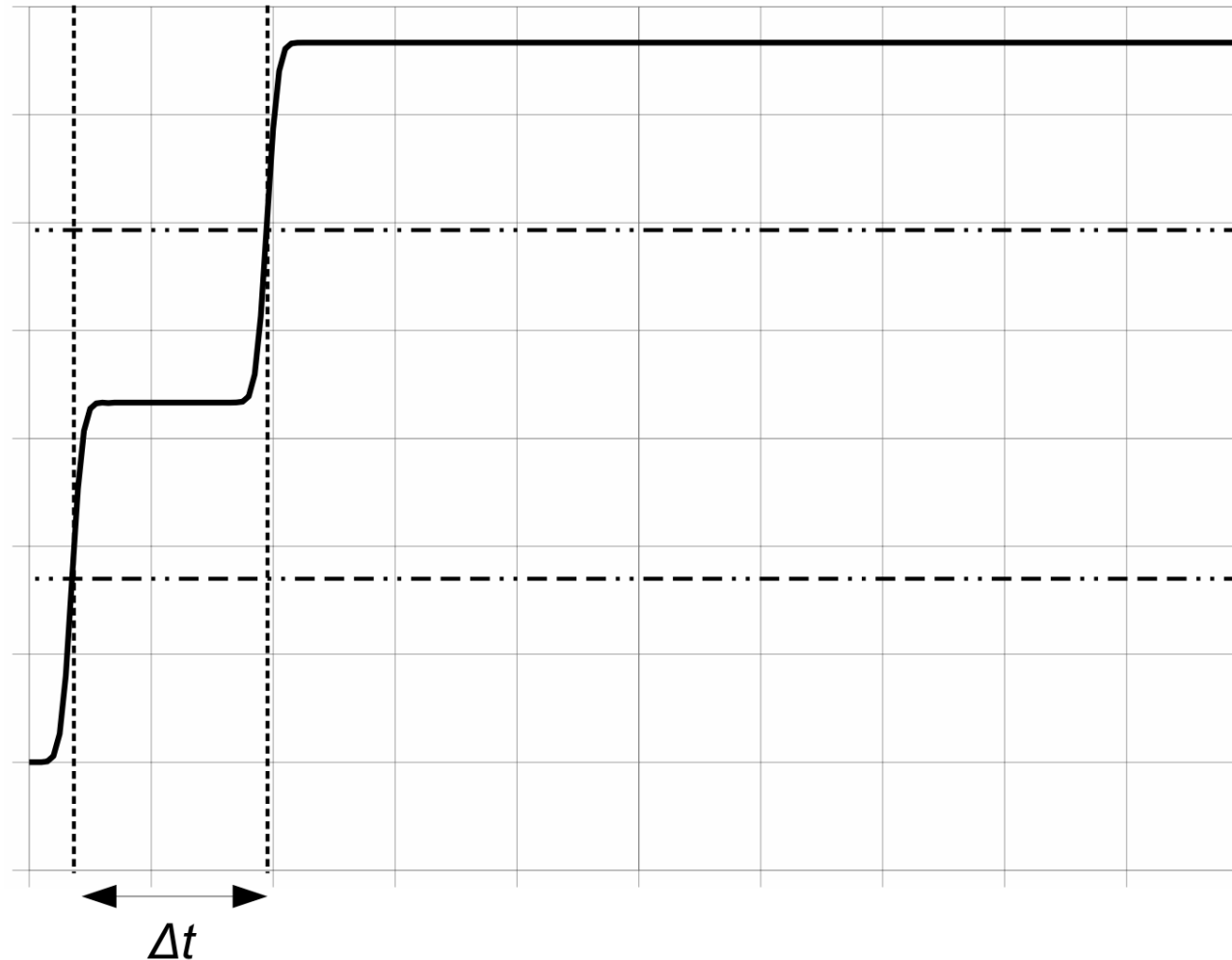




Laboratory activity

- **Verification of length measurement accuracy**
- **Incremental measurement:** a cable of known length is joined to the longer one
- Length difference is measured by TDR
- $\tau = \Delta t' - \Delta t$
- Time resolution Δ_t



Laboratory activity

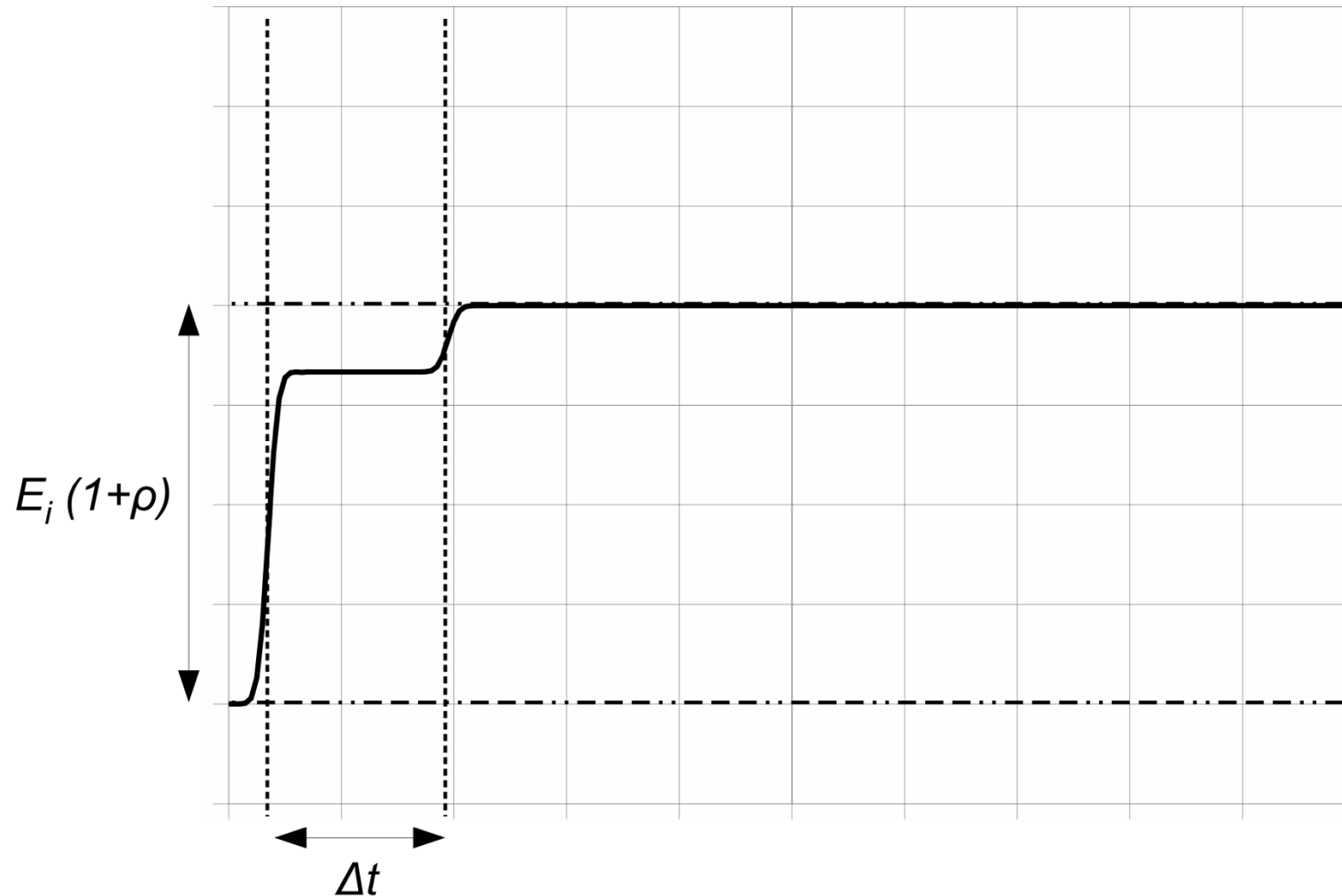- Line termination impedance: resistive load





Laboratory activity

- Line termination impedance: capacitive load

- $v(t) = 2E_i \left(1 - e^{-\frac{1}{Z_0 C_L}}\right)$


- Time to half-value $t_{\frac{1}{2}}$

- $e^{-\frac{1}{Z_0 C_L}} = \frac{1}{2}$ from which $Z_0 C_L = \frac{t_{\frac{1}{2}}}{\ln 2} \cong t_{\frac{1}{2}} \cdot 1.4$



Laboratory activity

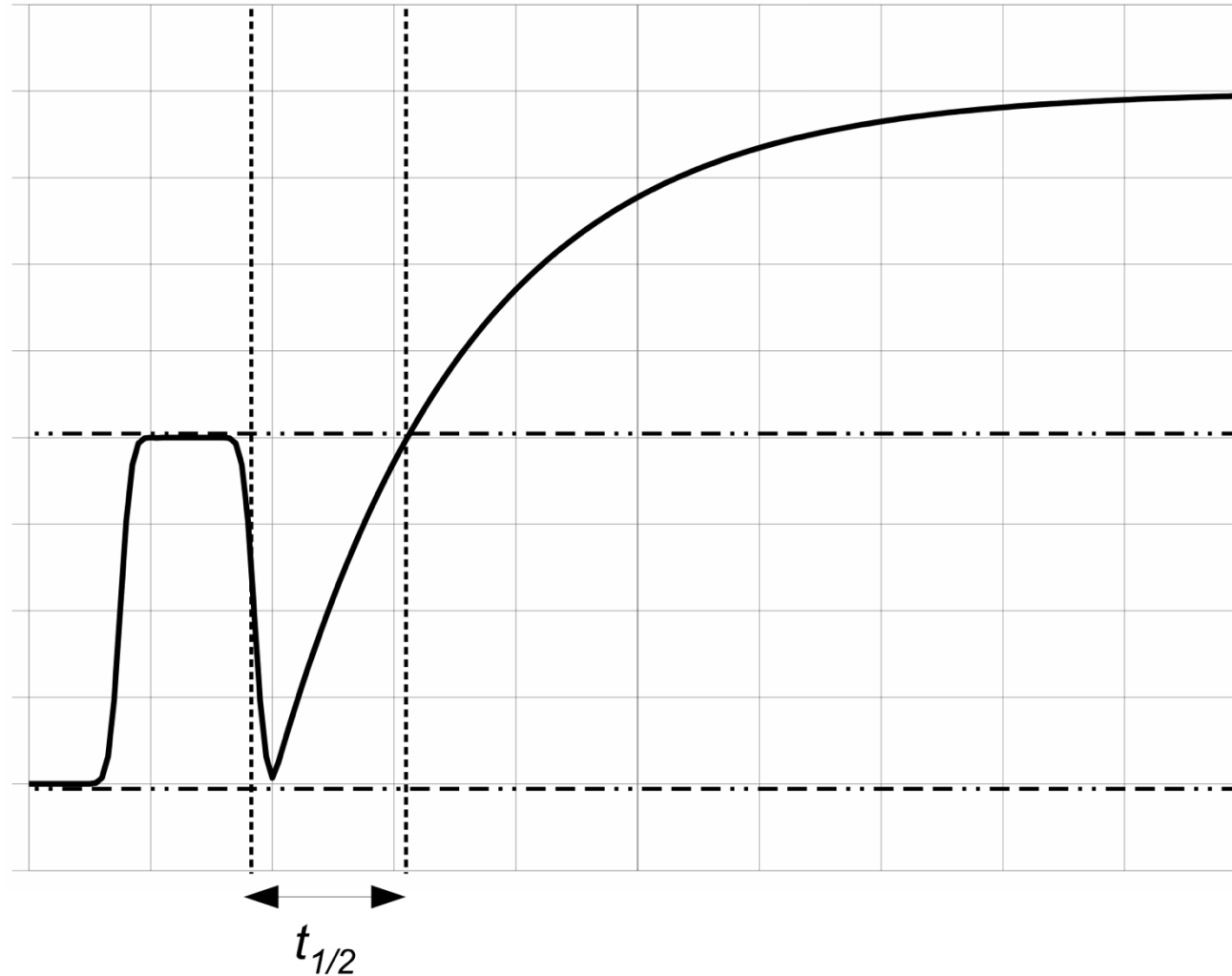- Line termination impedance: capacitive load





UNIVERSITÀ
DEGLI STUDI
DI PADOVA