

Lecture #14
Electronic measurements
Alessandro Pozzebon

- Measurement of time intervals
 - Measurement of periodic signals
 - Measurement of the delay between two signals
 - Phase shift measurement
 - Measurement of the rise and fall times of steep edges
- Measurement of frequencies
 - Characterization of signal generators, voltage-controlled oscillators, etc...
 - Analysis of signal sources associating the information content to frequency
- Measurements of time delay by means of ad-hoc sensors and transducers

• Identification of certain **reference points** on the analysed signal \rightarrow **Events**

- Measurement of the period → Events: beginning and ending of the period
- Measurement of the rise time → Events: instants at which the signal reaches conventionally defined amplitude values

Set of circuits which extract the events of interest from the input signals



Crossing of a given amplitude level



Measurement is made by direct comparison with the instrument's internal reference



Generation of time intervals of constant and known duration



Determination of elapsed time by counting them





Counter





Main components of a counter


- Input circuits
- Time and frequency reference
- Gate circuit
- Logic circuits and counting elements
- Control circuits
- Visualization tools

- At least two input channels, the use of which can be coordinated
- Each channel has its own independent input circuits

- **Signal conditioning circuit** → Similar to other measurement instruments
 - Amplification
 - Attenuation
 - Impedance matching



Normalization circuits

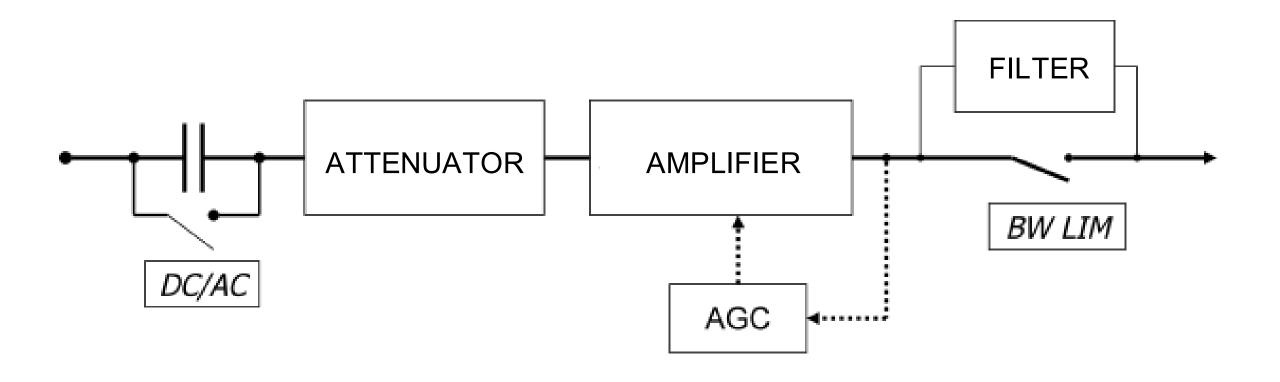

- AC/DC switch (Series capacitor): AC coupling
- Amplifiers and attenuators:
 - Extremely wide bandwidth
 - High gain
 - Stable over time and temperature changes
 - Low noise level
 - Uniformity of behaviour
- Low pass filter (BW LIM): when measuring signals at frequencies significantly lower than the maximum one, it can reduce the effects of broadband noise

• Shaping circuit: provides a signal that retains the time information of the input signal while being different in form \rightarrow Comparator with hysteresis



- Trigger: there is a switching edge any time the input signal reaches a threshold voltage
- The information concerning the events of interest is associated with the switching of a signal

- Maximum frequency of the counter → switching speed of the trigger
- The most important condition to be fulfilled in this case is the permanence


- Rise time measurements: the ability to precisely establish the threshold level also becomes important \rightarrow The set level needs to be verified from the outside
- Counters often have an output on which the DC voltage of the trigger level is present

Comparator without hysteresis → Impact of noise → Spurious switching



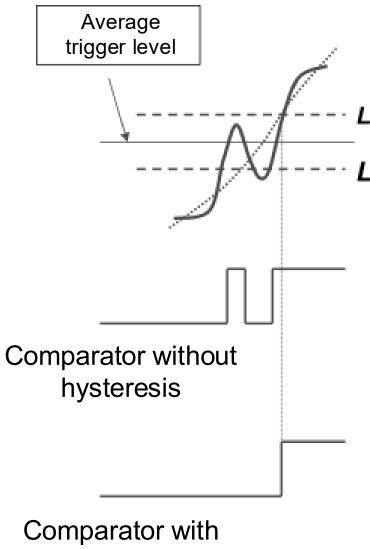Introduction of a hysteresis into the input-output characteristic of the comparator






hysteresis

- The peak-to-peak amplitude of the input signal must be greater than the amplitude of the hysteresis band
- Command adjusting hysteresis → Sensitivity command
- **Sensitivity**: rms value of a sinusoidal signal whose peak-to-peak amplitude is equal to the difference between the two thresholds:

sensitivity =
$$\frac{L^+ - L^-}{2 \cdot \sqrt{2}}$$

Signal shaping circuit

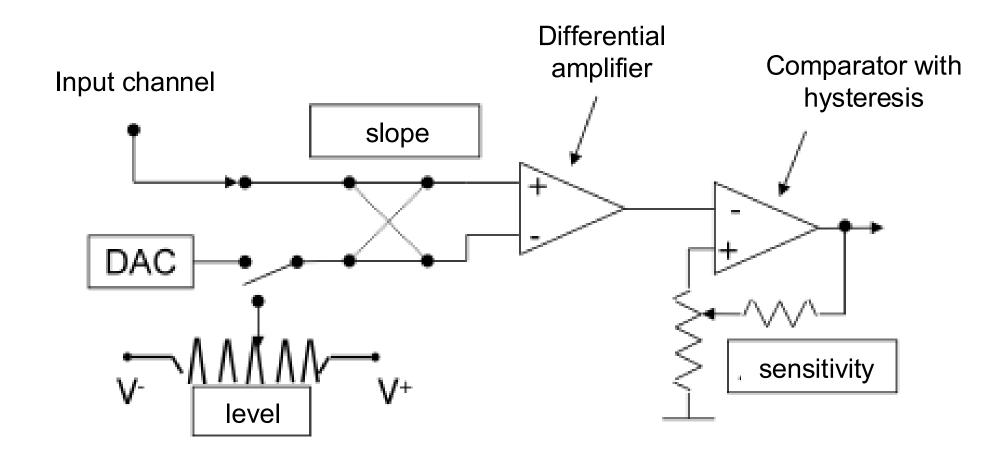



Frequency reference and time base

- Time base: sets the fundamental limits of accuracy
- Quartz cristal resonant element: oscillation frequency F_R between 1 and 10 MHz
- Minimization of temperature influence (oven oscillators)
- Avoiding loading effects → Buffer (impedance separator)
- Sinusoid → Converted in a square wave

- Factors of uncertainty:
 - Fluctuations in the supply voltage
 - Short-term variations
 - Variations over time




 10^{-6}

- Enables the counting of events:
 - Taken from the input signal
 - Provided, at constant intervals, by the internal reference
- Start signal: opening of the gate
- Stop signal: closing of the gate




- Time interval $T_{ON} \rightarrow$ Gate time
- Two inputs:
 - One for the signal to be sent to the counter
 - One for the command signal

Gate circuit

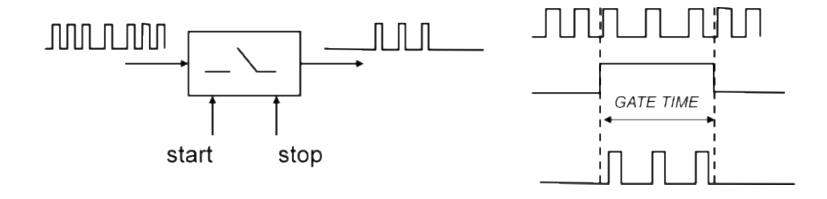

- The **rising edge** of the command signal enables the passage through the gate of the pulses to be counted
- The subsequent falling edge terminates the time interval during which the gate is enabled
- AND logic gate

Gate circuit

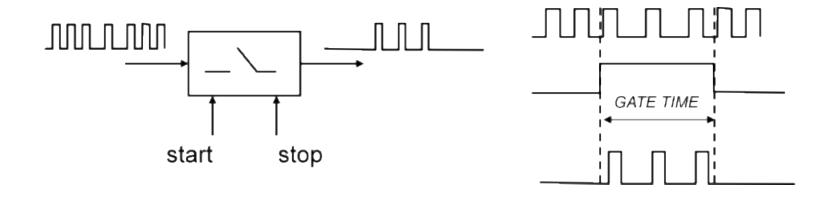

- The gate places limits on the maximum frequency at which the counter can be used
- In order not to cause counting errors when the signal has a frequency F, the switching times of the gate must be less than 1/(2F)
- **Response time** to Start and Stop commands as short as possible and equal for both commands

Counting circuits

- This block counts the events between the Start and Stop signals
- Binary counter → Simple structure → High speeds
- Impulses counting
- Initialization command to be sent to the counter → Block reset
- Limits on the frequency of the input signal


Control circuits

- They select the mode and type of the measurement:
 - Periodic, intermittent, continuous
 - Period, frequency, etc...
- They control the opening and closing of the gate
- They also control the displaying of the result and the resetting of the counter in the instrument
- They also enable the **transfer** of the obtained count to an auxiliary memory register to allow the display of the result

- Devices for the **visual presentation** of the numerical result of the measurement:
 - LEDs
 - Liquid Crystal
 - 7-segment displays
- 3 to 8 decimal digits
- Resolution obtainable with a given instrument varies according to the type of measurement and the way in which the instrument itself is set up

Events counting

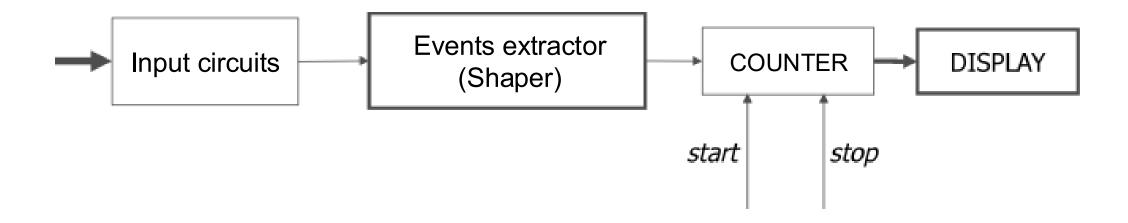
- The input signal is transformed into a succession of pulses to be sent to the counting block
- Signals of Start and Stop can be supplied either manually via the front panel of the instrument, or by means of external signal generators
- The output is a number



Reciprocal counting

- Two distinct counters:
 - One used to count the events associated with the external signal
 - One counting the pulses coming from the internal time reference
- The gates of the two counters are controlled in a coordinated manner by a single circuit:
 - Same gate time T_{ON}
- In this instrument, the operator, in addition to selecting the type of measurement desired, only sets the measurement time $T_{\it ON}$
 - The most suitable measurement mode is chosen by the instrument itself based on the characteristics of the input signal

Reciprocal counting

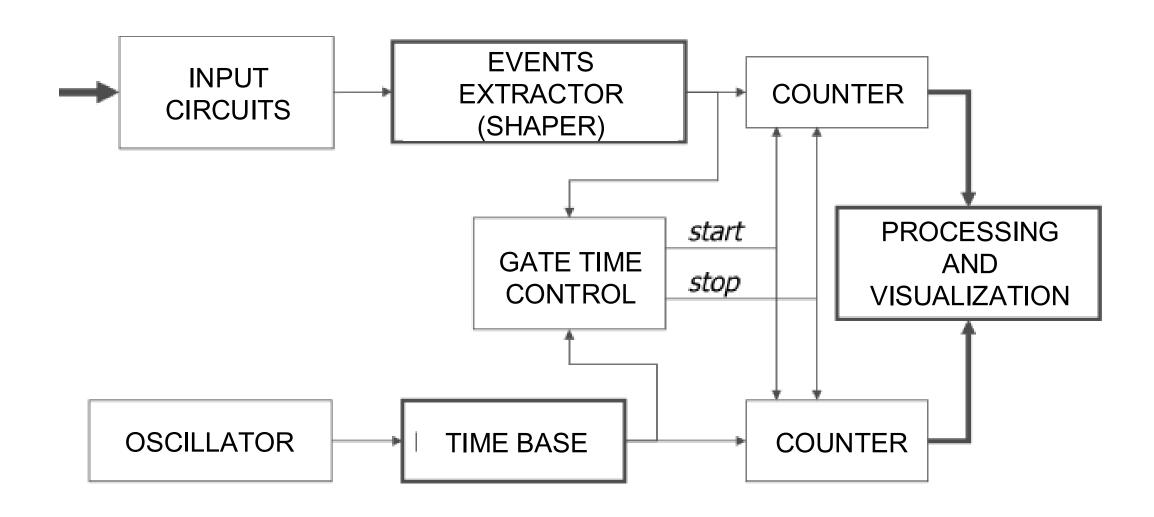

Reciprocal counting

- Selection of the type of measurement
- Selection of the gate time T_{ON}
- **Time counter** → Time base
- Events counter → Input signal
- If $F_X < F_R \rightarrow \text{Time meter}$
- If $F_X > F_R \rightarrow$ Frequency meter

Measurement with internal time reference


- Internal time reference \rightarrow Periodic signal of period T_R
- How many time units, of duration T_R , the unknown interval corresponds to
- Start and stop commands, determining the gate time are derived from the input signal

Periodic signal → one event every period

- If start corresponds to one of these events and the Stop to the one immediately following $\rightarrow T_{ON} = T_x$
- If the Stop is given at a distance of M periods $\to T_{ON} = MT_x$ $T_{ON} = MT_x = N_x \cdot T_R$

Measurement with internal time reference

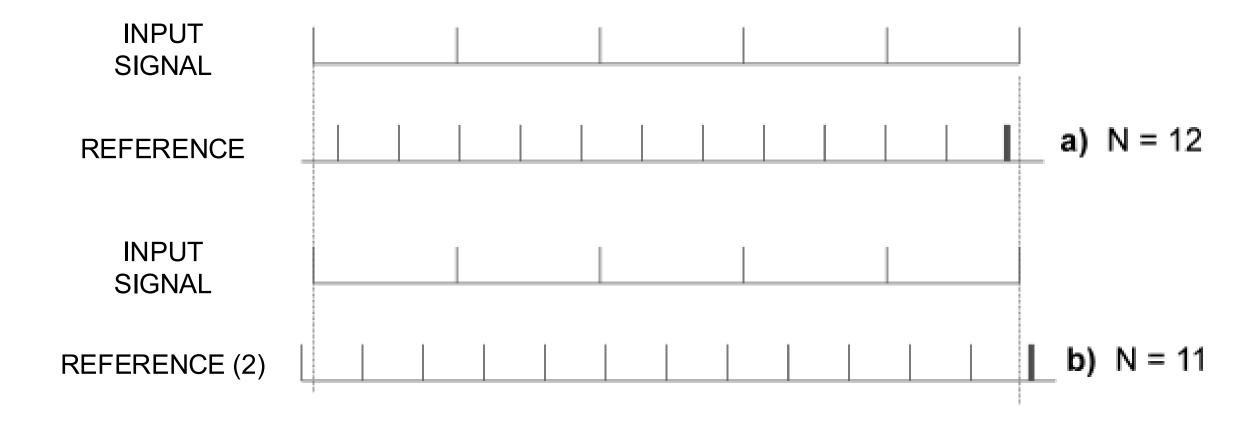Uncertainty in the counting equal to the resolution of the counter, equal to ±1 units of its least significant digit



Measurement with internal time reference

$$MT_{x} = (N_{x} \pm 1) \cdot T_{R}$$

$$T_{x} = \frac{N_{x}}{M} T_{R} \pm \frac{T_{R}}{M}$$

$$F_{x} = \frac{1}{T_{x}} = \frac{M}{N_{x}} F_{R} \pm \frac{M}{N_{x}^{2}} F_{R}$$

- As M increases, the resolution improves
- As M increases, the time required for the measurement also increases
- Resolution:

$$\frac{\Delta_{\mathcal{X}}}{T_{\mathcal{X}}} = \frac{T_R}{MT_{\mathcal{X}}} = \frac{T_R}{T_{ON}} = \frac{1}{N_{\mathcal{X}}}$$

Measurement with internal frequency reference

- F_x number of periods per time unit time interval
- The shaping circuit obtains an event at each period of the input signal and the instrument counts the number of events that occur in the known time interval T_{ON}
- $T_{ON} = K \cdot T_R = (N_x \pm 1)T_x$

$$F_{\chi} = \frac{N_{\chi}}{K} F_R \pm \frac{F_R}{K}$$

$$T_{\chi} = \frac{1}{F_{\chi}} = \frac{K}{N_{\chi}} T_R \pm \frac{K}{N_{\chi}^2} T_R$$

$$\Delta_F = \frac{F_R}{K} = \frac{1}{KT_R}$$

Study of the resolution

- Internal period reference vs internal frequency reference
- Time reference

$$\frac{\Delta_{x}}{T_{x}} = \frac{T_{R}}{MT_{x}} = \frac{T_{R}}{T_{ON}}$$

Frequency reference


$$\frac{\Delta_F}{F_X} = \frac{F_R}{KF_X} = \frac{1}{F_X} \cdot \frac{1}{T_{ON}}$$

• Time reference: no dependance on F_{χ}

Study of the resolution

Equal gate time

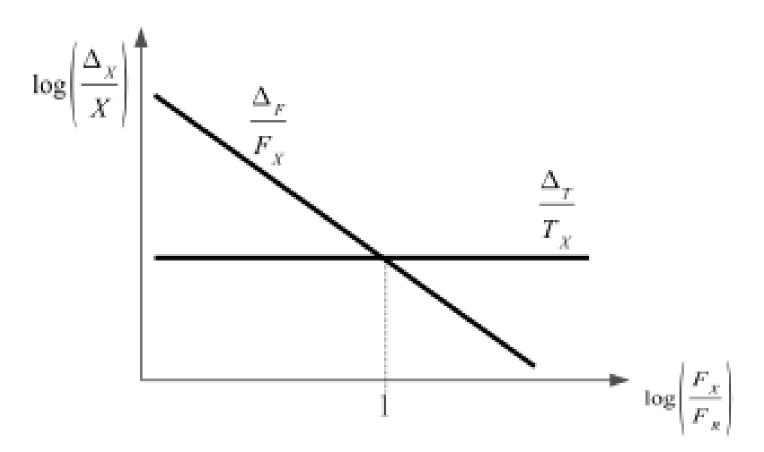
$$\frac{\Delta_{\mathcal{X}}}{T_{\mathcal{X}}} \le \frac{\Delta_{F}}{F_{X}} \Longrightarrow \frac{T_{R}}{T_{ON}} \le \frac{1}{F_{\mathcal{X}}} \cdot \frac{1}{T_{ON}} \Longrightarrow F_{\mathcal{X}} \le F_{S}$$






Sources of uncertainty

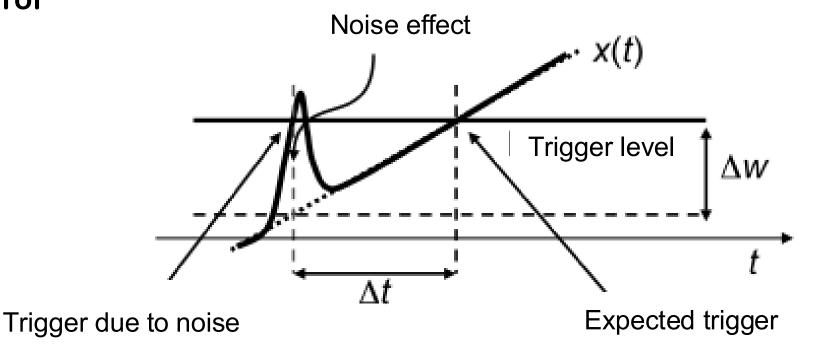- Resolution (Start and Stop signals synchronization)
- Time base stability
 - Long use
 - Influence quantities
- Trigger error






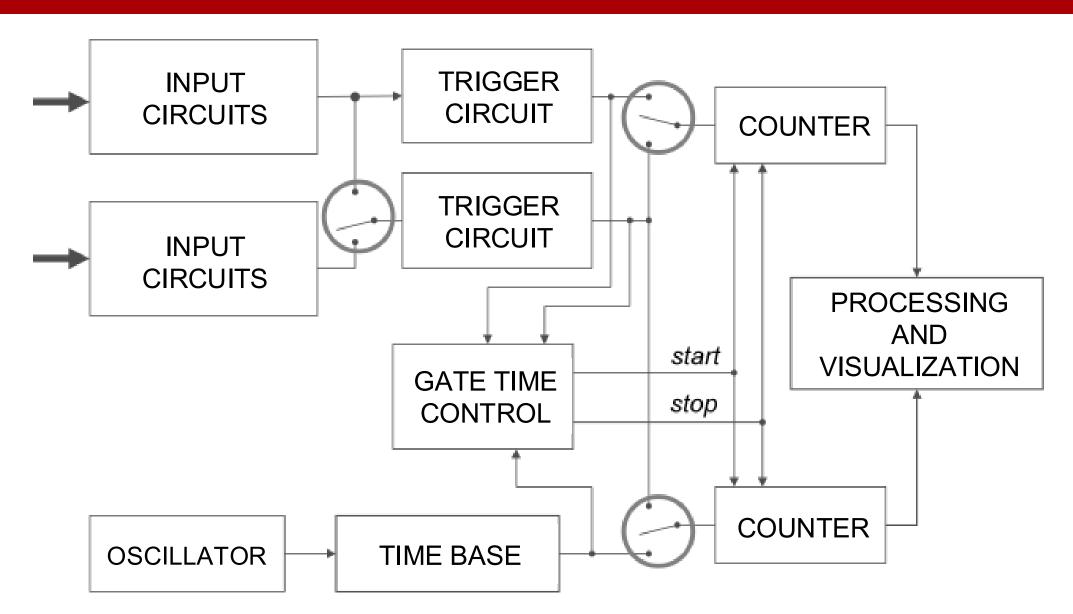Reciprocal counter with two input channels



Reciprocal counter with two input channels

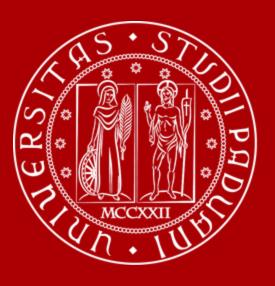- Measurement of the ratio of two frequencies
- Measurement of the duration of a time interval
- Measurement of the average duration of a time interval



UNIVERSITÀ DEGLI STUDI DI PADOVA