



UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Digital circuit test – An introduction

Lecture #16

Electronic measurements


Claudio Narduzzi, Alessandro Pozzebon



UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Modelling digital devices

Computer Aided Design (CAD)

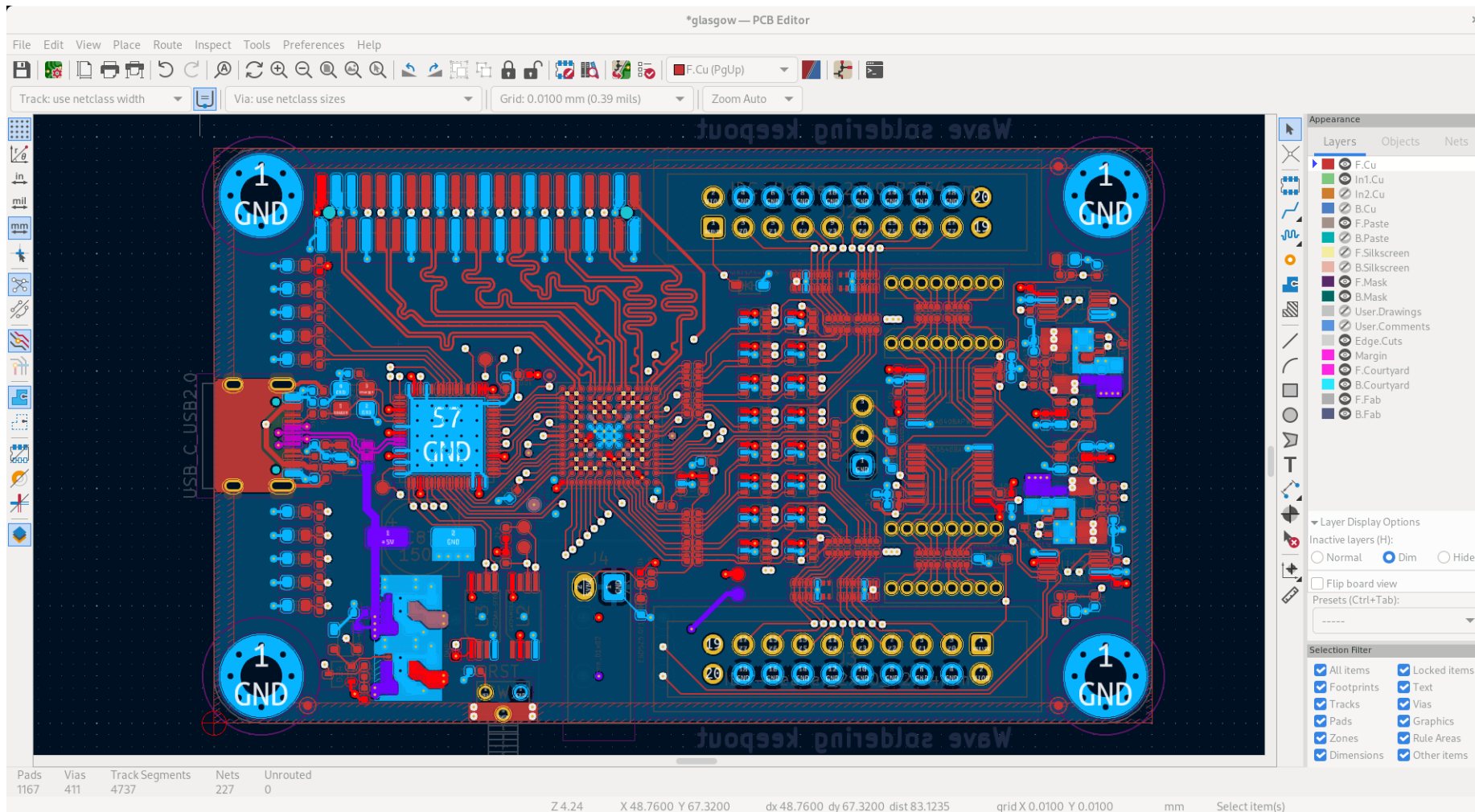



Modelling digital devices

- **Models** → Different levels of abstraction
 - Behavioural models
 - Structural models
- **System level models** → Device architecture
- Different subsystems with different tasks
- **Behavioural model** → Interacting processes
- **Structural model** → Integrated components (processors, memory units, the organization of data and control busses, etc...)



Modelling digital devices

- **Algorithms** → Description of the way the system processes data and produces an output
- **Data** → Variables → Registers
- **Algorithm steps** → transfers of processed data among registers



Register-transfer (RT) model



Modelling digital devices

- **Logic level models** → Basic representation by means of binary variables
- **Behavioural model** → Boolean equations
- **Structural model** → Logic gates and memory elements




Primary approach in the characterization of digital electronic devices

- Signal representation:
 - **Analog:** function $x(t)$
 - **Digital:** $[0, 1]$ values



 Transfer characteristic of a logic inverter






Modelling digital devices

- **Internal circuits timing** → Clock → Square wave
- **Rising or falling edges** determine the instants when digital memory elements are allowed to update their values → Active edges
- **Combinational logic networks** → Truth tables
- **Synchronous sequential state machines** → State diagrams
- Verification of **correct logic behaviour** → measurement instrument uses the circuit clock
- Analysis of **response times** → Measurement instrument uses an internal high-speed time reference → Timing analysis (**Timing diagrams**)



Timing diagram

 

T = toggle



- **Physical-level defects → Logic faults**
 - Digital components like EEPROM, PLD or FPGA, are **programmed only when employed in a specific device**. Component-level verification cannot ensure a proper system functionality check
 - An electronic product goes through **several assembly stages** (component positioning on PCB, soldering, etc...) that may introduce defects
 - Electronic components may be subjected to **thermal, mechanical, chemical and electrical stress**



Digital testing → identification of the logic faults induced by defects



Fault models

- **Fault model:** translates the possible effects of a physical-level defect into the description of a **faulty logic-level behaviour**
- **Logic fault** → Device logic function is altered
 - Combinational logic network → Modification in the **input-output logic behaviour**
 - Sequential machine → Modification in the **state diagram**
- **Timing faults** → critical variations in the device **timing diagrams**




Stuck-at faults

- In some circuit node, switching between the two logic levels **becomes impossible for some reason**
- The logic level of one specific line is thus forced to just one value → **Stuck-at**
- Functional verification: check that **all inputs and outputs can freely change** their logic state in response to suitable test stimuli



Stuck-at faults

- Example: NAND gate

 


a	b	y
0	0	1
0	1	1
1	0	1
1	1	0



Stuck-at faults

 - Gate output behaviour
 - $a = 1, b = 1$
 - One of the other three combinations
- Gate input behaviour
 - $a = 1, b = 0$
 - $a = 0, b = 1$



a	b	y
0	0	1
0	1	1
1	0	1
1	1	0




Test vectors



Test vectors

 - **Test Vector:** any combination of input logic values employed in the test of a logic network, associated with the indication of the expected correct response



- **NAND gate**

- 6 stuck-at single faults (stuck-at 0 and stuck-at 1)
- Minimum number of test vectors required for a complete test = 3

a	b	y
0	0	1
0	1	1
1	0	1
1	1	0

test vector no.	a	b	y	\bar{y}	detectable faults		
1	0	1	1	0	a stuck-at-1	y stuck-at-0	
2	1	0	1	0	b stuck-at-1	y stuck-at-0	
3	1	1	0	1	a stuck-at-0	b stuck-at-0	y stuck-at-1



Test vectors

test vector no.	a	b	y	\bar{y}	detectable faults		
1	0	1	1	0	a stuck-at-1	y stuck-at-0	
2	1	0	1	0	b stuck-at-1	y stuck-at-0	
3	1	1	0	1	a stuck-at-0	b stuck-at-0	y stuck-at-1

- $a = 1, b = 1, y = 1 \rightarrow$ a fault condition is detected (**Fault detection**), but it is not possible to establish where the fault occurred (**Fault location**)
- Minimum number of test vectors N_{tv} :

$$n + 1 \leq N_{tv} \leq 2^n$$

with n inputs



Test vectors

$$n + 1 \leq N_{tv} \leq 2^n$$

- The number of test vectors **increases with the number of inputs**
- The actual complexity **depends on the specific Boolean function**, as well as on how that function is implemented by a logic gate network
- **Different combinations of logic gates** can be used to implement a given Boolean function




Whenever possible, a designer should favour easily testable circuit structures



Test vectors

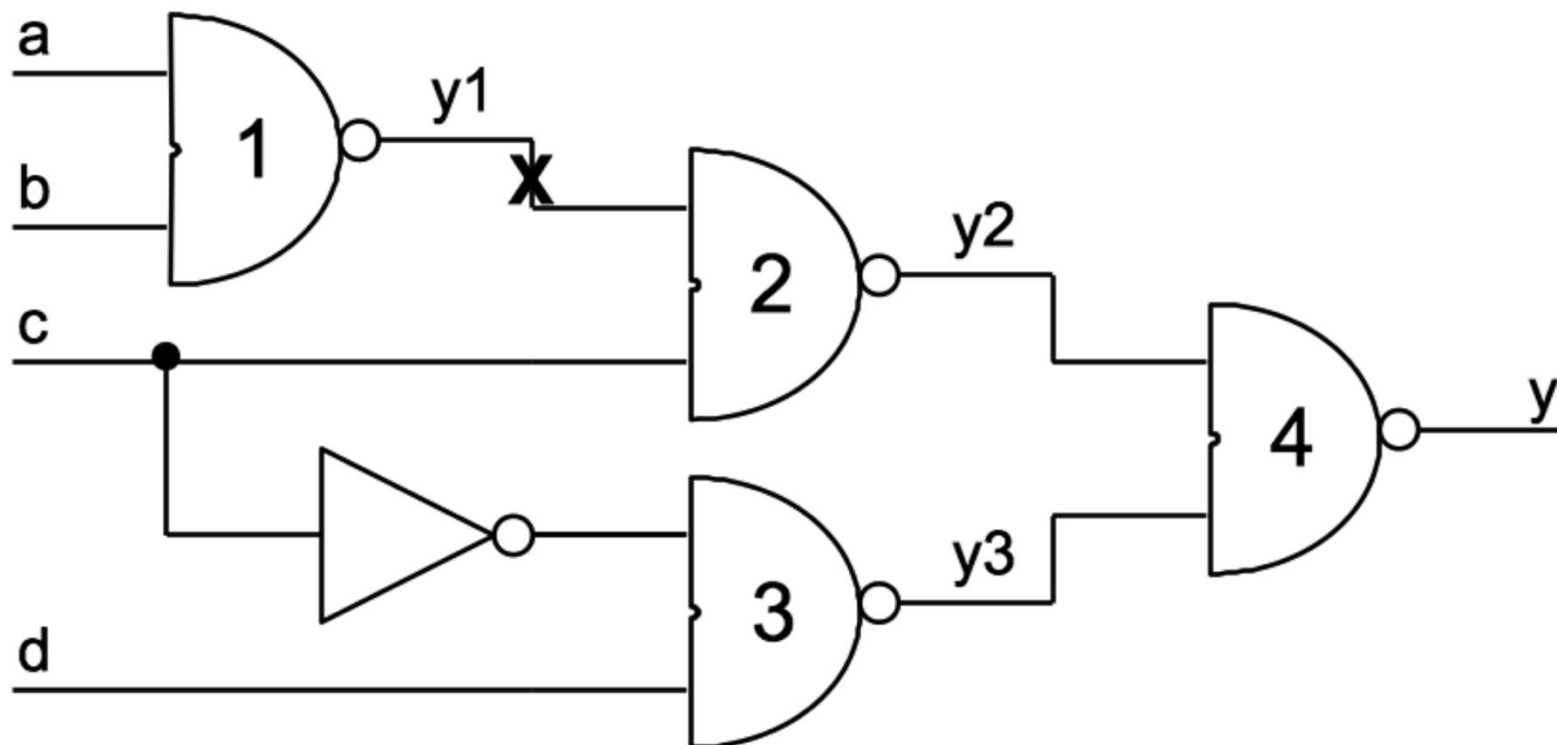- Verification of lines that are **not directly accessible** from the network input/output terminals




a	b	c	d	y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0



Test vectors

- **Input c** → **Enable input** that allows to select as the network output y , the logic NAND of the two inputs a and b , or the value of logic variable d
- Test vectors for the NAND gate allow the verification of gate no. 1 (a and b), but **the output is not accessible** unless input $c = 1$
- Setting $c = 1$ allows the gate no. 1 output value to propagate through NAND gate no. 2
- Care needs to be taken to define some of the test inputs so that **the response of logic gates at intermediate levels can be observed**

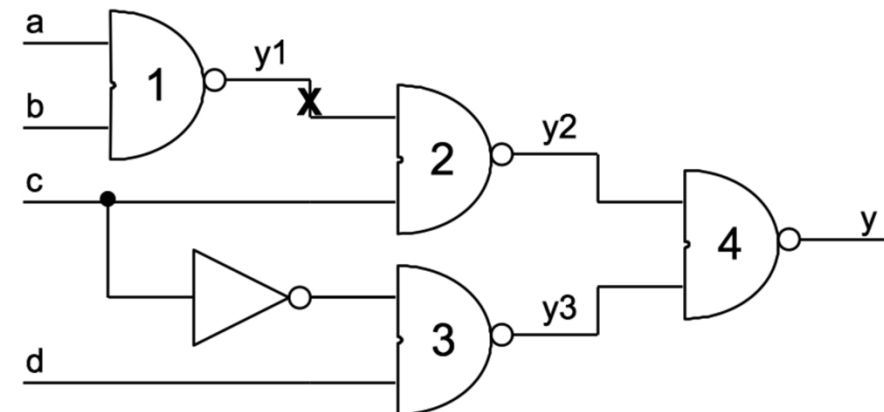



Test vectors

test vector no.	a	b	c	d	y	\bar{y}	detectable faults
1	X	\bar{X}	0	0	0	1	d s-a-1 $y1$ s-a-0 $y2$ s-a-0 $y3$ s-a-0 y s-a-1
2	X	\bar{X}	0	1	1	0	c s-a-1 d s-a-0 $y3$ s-a-1 y s-a-0
3	0	1	1	1	1	0	a s-a-1 c s-a-0 $y1$ s-a-0 $y2$ s-a-1 y s-a-0
4	1	0	1	1	1	0	b s-a-1 c s-a-0 $y1$ s-a-0 $y2$ s-a-1 y s-a-0
5	1	1	1	1	0	1	a s-a-0 b s-a-0 c s-a-0 $y1$ s-a-1 $y2$ s-a-0 $y3$ s-a-0 y s-a-1





Test vectors

- Test vectors are defined under the assumption that a **single** fault may occur
 - The full path bringing the input stimulus to the logic gate concerned is enabled (**Path sensitization**)
 - The full path that propagates the test response to an observable output is enabled (**Fault propagation**)
- A single vector can detect **more than one single fault condition**
- Generation of test vectors is usually the task of **automatic test pattern generation (ATPG)** tools
- Often the test vector set produced by an ATPG is not designed to cover all possible faults, but to provide a **sufficiently high level of fault coverage** (for instance, 90%)

Test vectors

  - Better test efficiency is obtained by a **combination of test techniques**
- Observation of the **thermal image** of an assembled printed circuit board





Sequential state machines


- **Sequential State Machines:**
 - A number of **states**
 - A set of state **transition rules**
- **Clock** circuit for timing
- **Machine states** → Contents of memory elements
- **State transitions** → Triggered by clock active edges → Outputs of combinational logic functions



State transition functions define the values that will be stored in the memory elements at the next clock edge



Sequential state machines

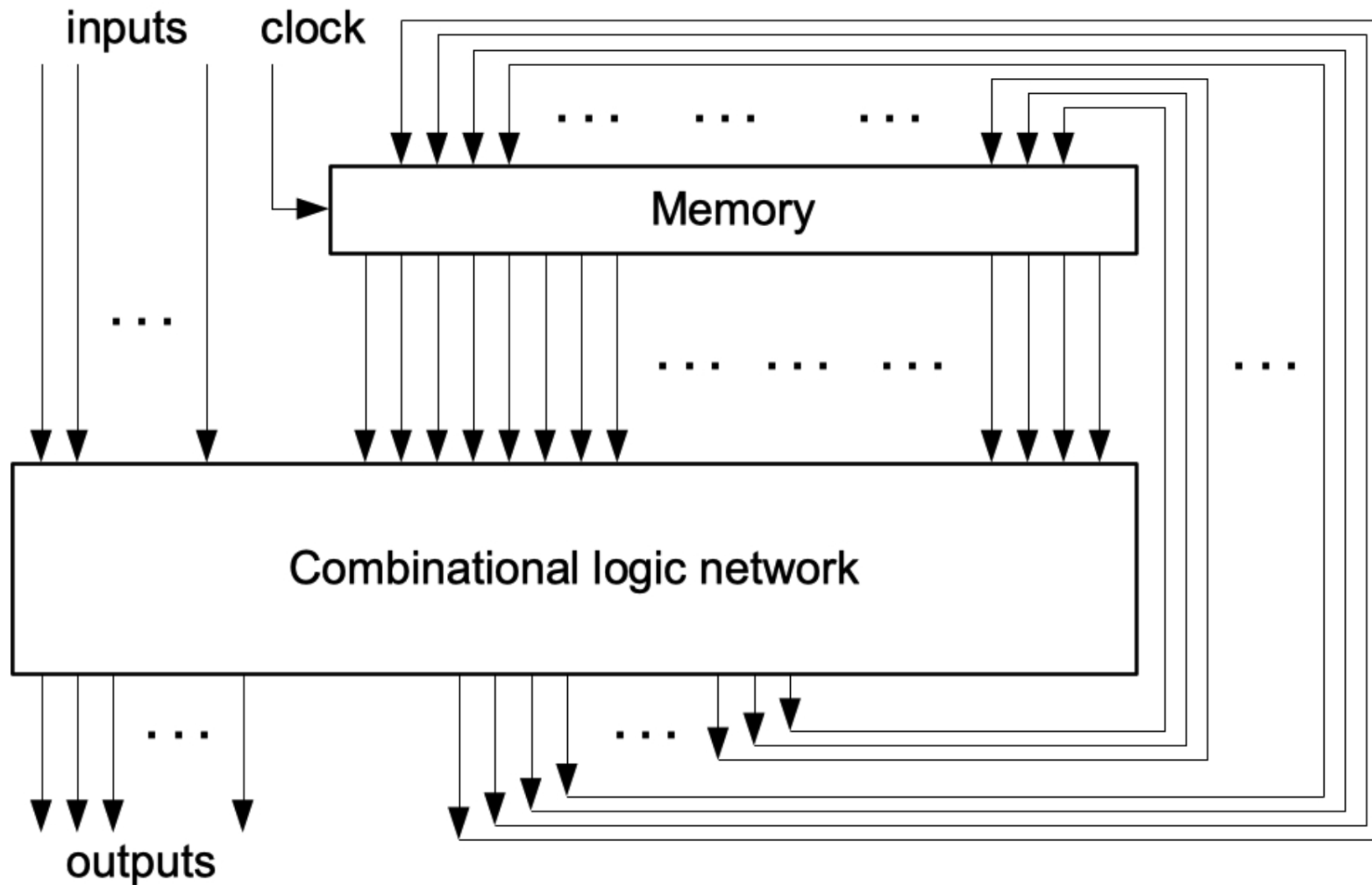



Sequential state machines

- Verification of a sequential machine presents far **more complex problems** than a purely combinational network
- **Input and output lines** are considered the only test points



Tests should also take into account all possible states of the machine

Internal variables

- m memory cells
- 2^m different states



The correctness has to be verified for each state



Sequential state machines

- n inputs
- 2^n input combinations
- $2^m \times 2^n$ test vectors
- **Difficulties:**
 - An extremely high number of combinations
 - The difficulty to preset the sequential machine to a known state before a test starts, since reaching a specific state usually implies the application of a suitable sequence of inputs



Printed Circuit Boards

- **Testing of PCBs**

- Test stimuli and the corresponding system responses can only be observed at the board input/output connectors




The **number of test points** remains extremely limited compared to system complexity

- Design of **additional test points** to provide access to selected signals, internal to the board
- **Partitioning of the system functions** into more easily testable subsystems



UNIVERSITÀ
DEGLI STUDI
DI PADOVA


Sequential state machines

 



UNIVERSITÀ
DEGLI STUDI
DI PADOVA

Sequential state machines

 



Printed Circuit Boards

- Dedicated test probes
- In-circuit testing → Automatic test systems
- **Test fixture:** interface between the test machine and the system under test
 - **Power supply** for the system under test
 - **Access to the test points** represented by system connectors
 - **Connections** to the internal test points → **Bed of nails**
- **Nails:** telescopic, spring-loaded pins whose position in the test fixture matches exactly that of test points in the system under test
- Each test fixture is **specific to a certain system under test**



Boundary scan

- **Boundary scan or Scan Path:** standardized testing technique
- **JTAG:** Joint Test Action Group → IEEE 1149.1 Standard
- Testing of complex and VLSI (Very large scale integration) lcs
- Progressive decrease in the accessibility
- **Microcontroller:** several thousand logic gates and just a few tens input/output lines






Boundary scan

- **Dedicated additional circuits** to facilitate the observation of internal states in a device and its initialization to a desired state → Activated exclusively during testing
- JTAG standard supports the realization of those test circuits and defines the system architecture for their use
- **Boundary Scan Cell (BSC):** memory cell → elementary JTAG circuit
- Associated to each input and output line in a logic network



Boundary scan

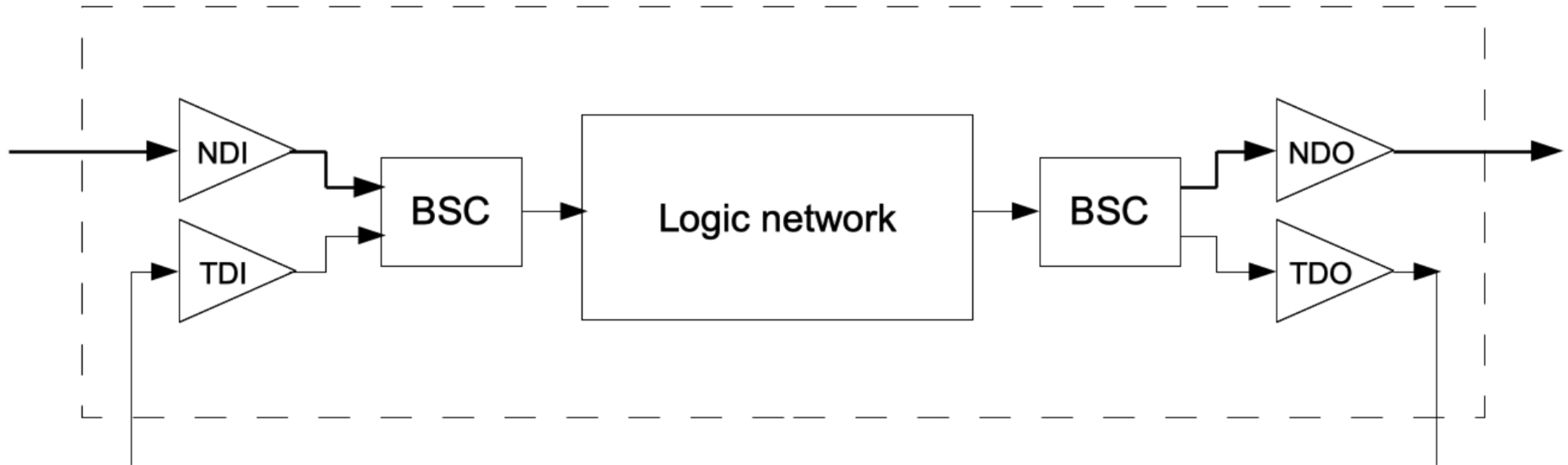




Boundary scan

- Device in **normal operation** → BSC is “transparent” to the exchange of data and does not affect the IC in any way
 - **Normal Data Input (NDI)**
 - **Normal Data Output (NDO)**
- **Test mode** activation → BSC disconnects the internal logic network from NDI and NDO lines, replacing them with test lines
 - **Test Data Input (TDI)**
 - **Test Data Output (TDO)**
- A test input can thus be sent to the logic network through TDI, and the response is observable on line TDO




Boundary scan register

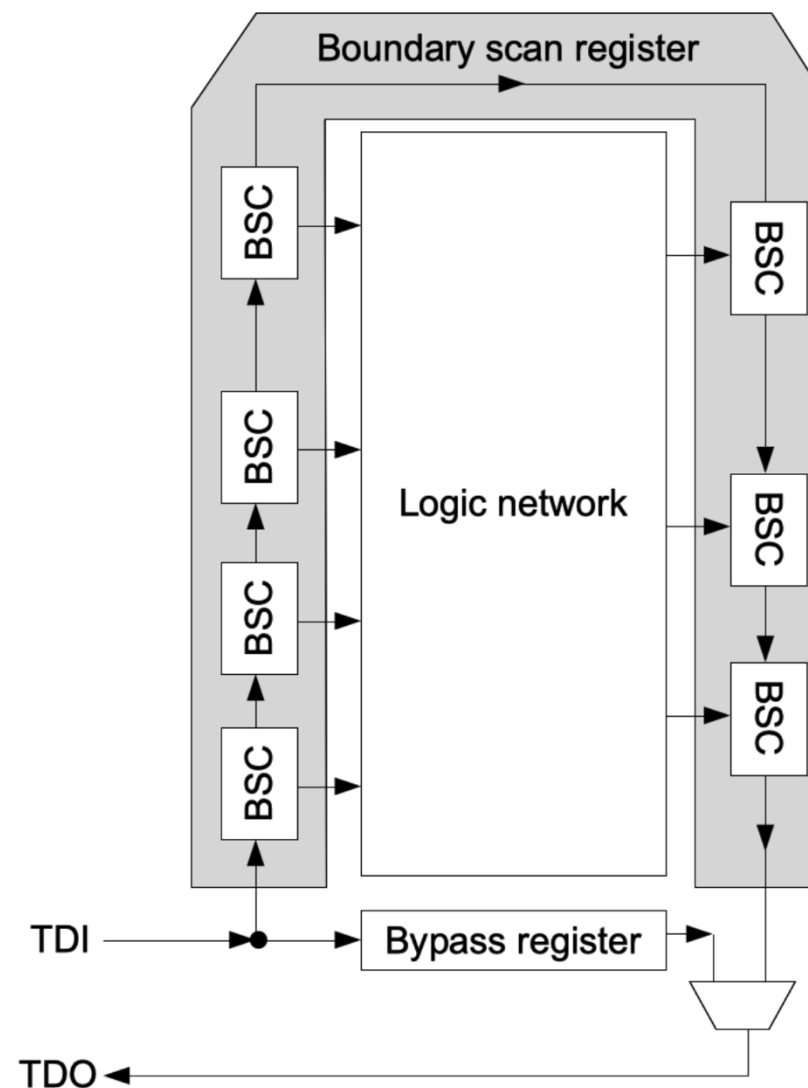- BSC cells within a device are interconnected to form a register, called boundary scan register (BSR)
- During the actual test, all the component input and output lines are operated in parallel
- Four test lines are defined by the JTAG standard and form the **test access port (TAP)**:
 - TDI
 - TDO
 - TCK: test clock
 - TMS: test mode select






Boundary scan register

 



Boundary scan register

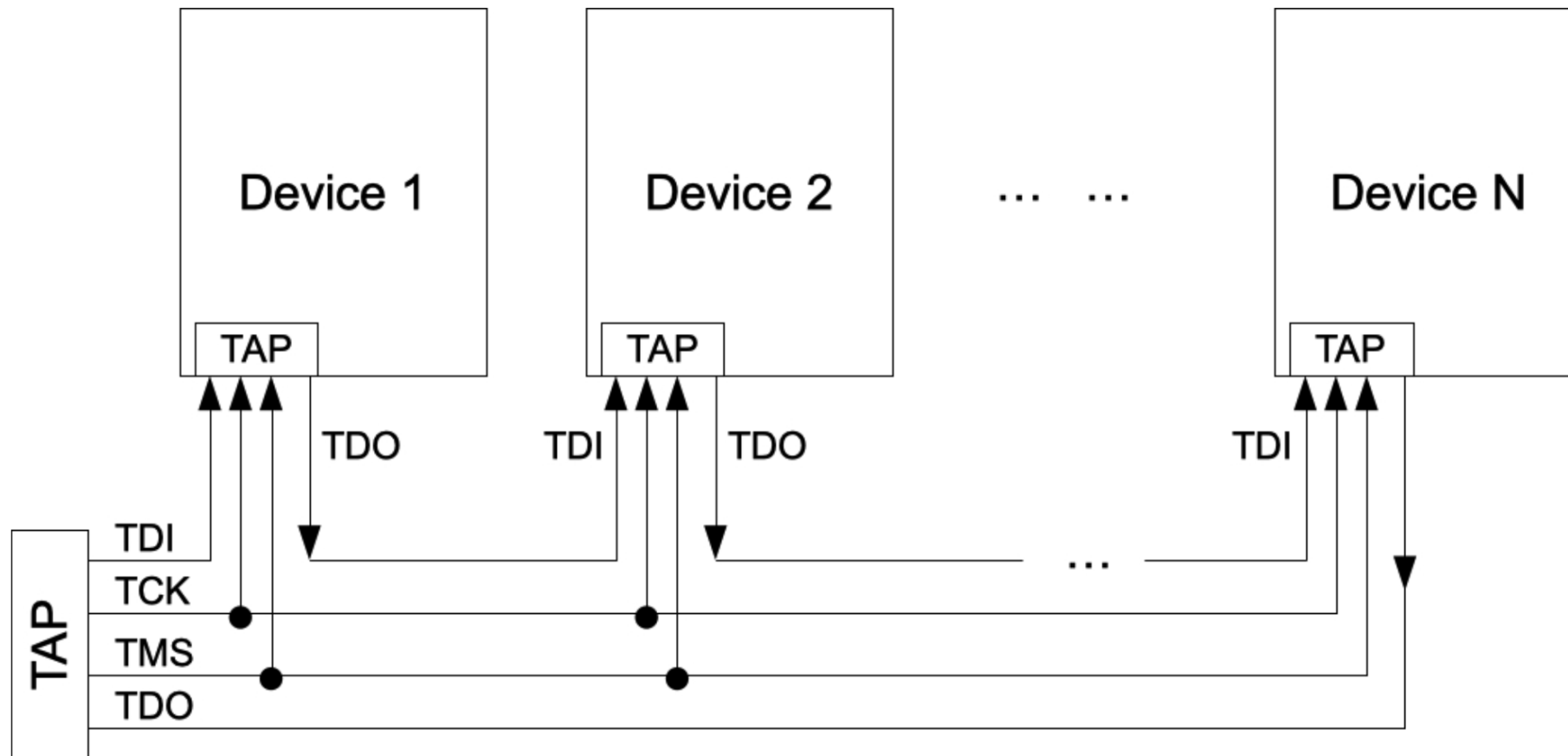- In a system, all JTAG-compatible components are serially linked to form a daisy chain





UNIVERSITÀ
DEGLI STUDI
DI PADOVA